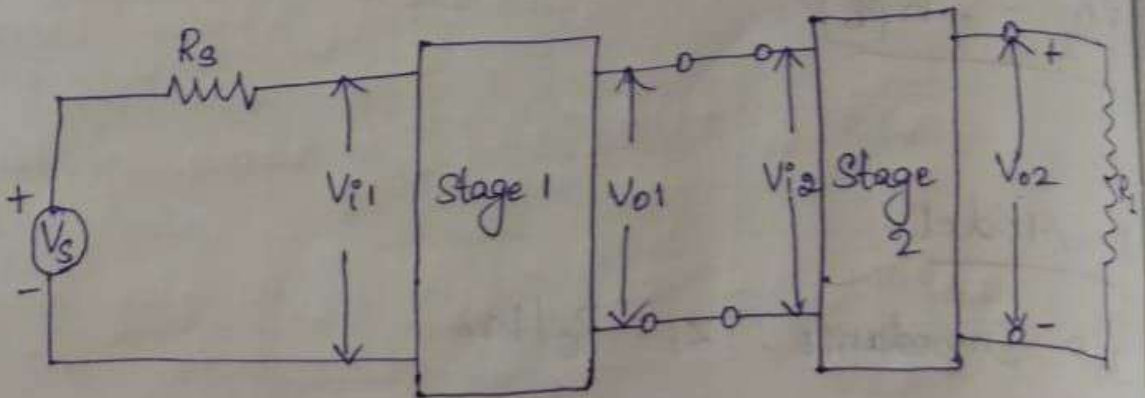



Two stage Cascaded Amplifier :





$$A_v = \frac{V_{o2}}{V_{i1}} = \frac{V_{o2}}{V_{i2}} \cdot \frac{V_{i2}}{V_{i1}}$$

$$V_{o1} = V_{i2}$$
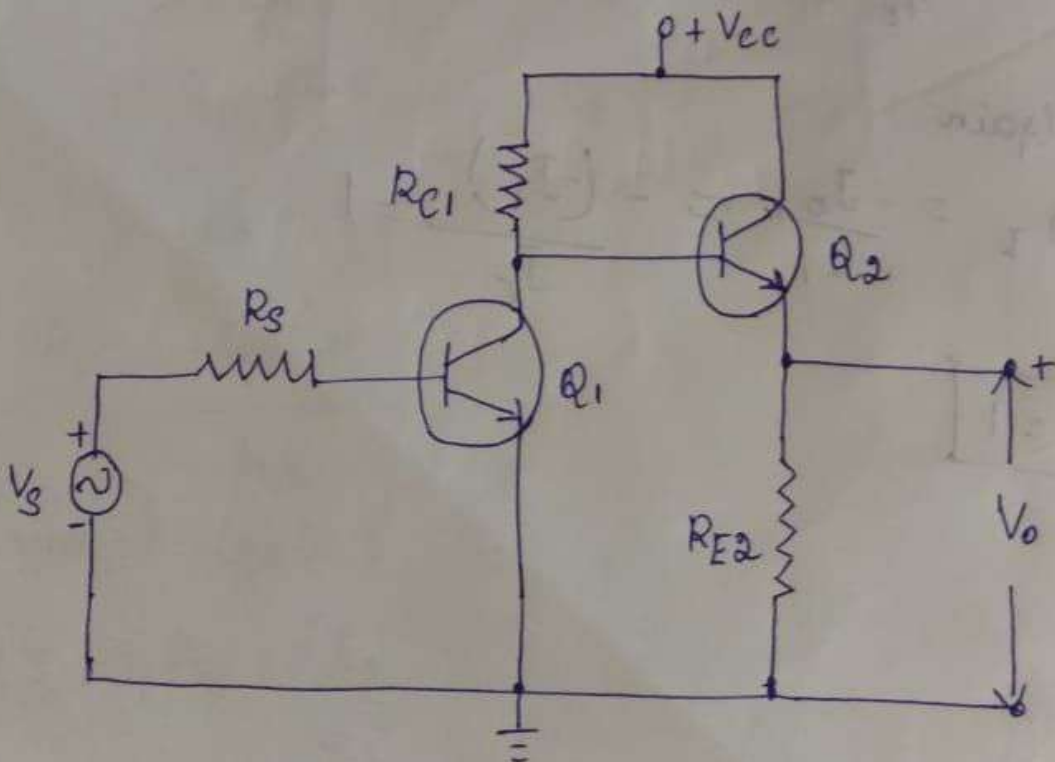
$$A_v = \frac{V_{o2}}{V_{i2}} \cdot \frac{V_{o1}}{V_{i1}} = A_{v2} A_{v1}$$



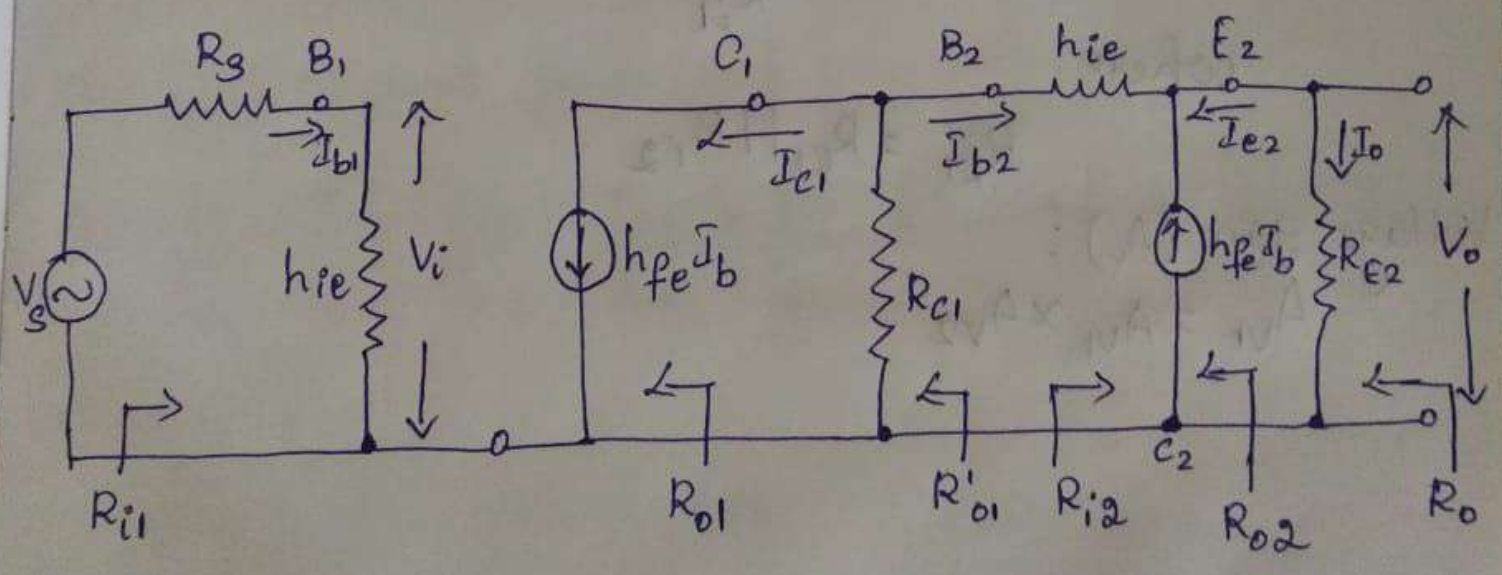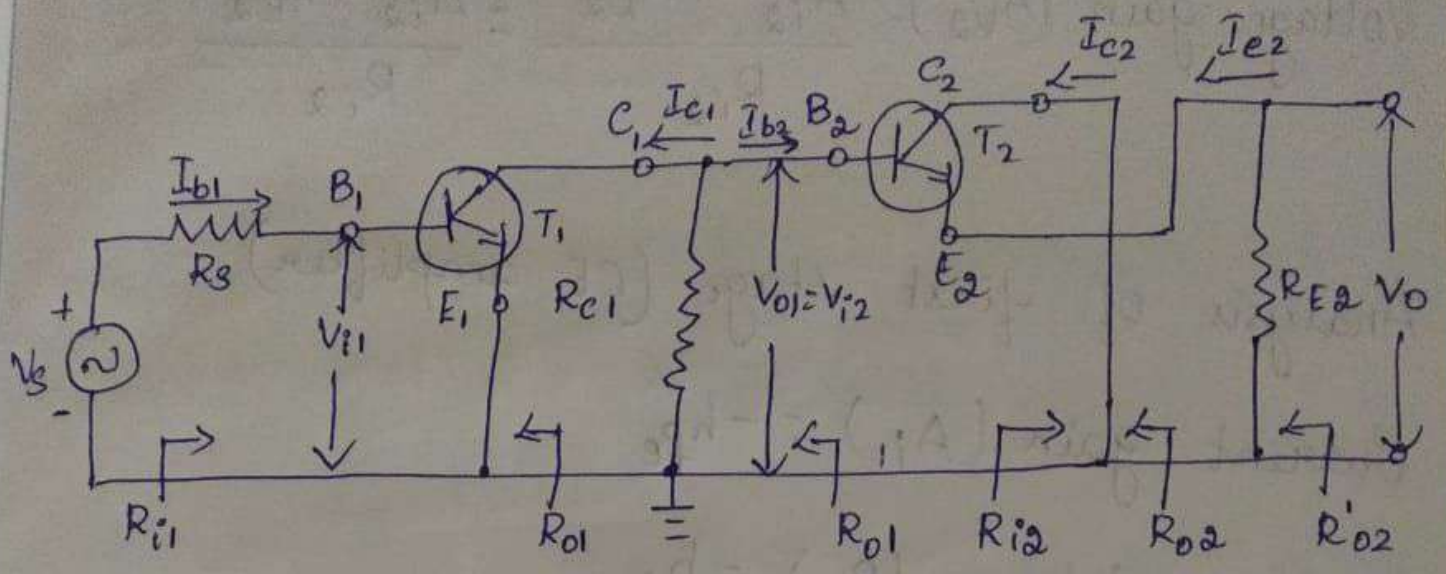

Analysis of second stage (CE amplifier):

$$\text{Current gain } (A_{i2}) = 1 + h_{fe}$$

$$\text{Input resistance } (R_{i2}) = h_{ie} + (1 + h_{fe}) R_{E2}$$

$$\text{Voltage gain } (A_{V2}) = \frac{A_{i2} \times R_{L2}}{R_{i2}} = \frac{A_{i2} \times R_{E2}}{R_{i2}}$$

Analysis of first stage (CE amplifier):

$$\text{Current gain } (A_{i1}) = -h_{fe}$$

$$\text{Input resistance } (R_{i1}) = h_{ie}$$

$$\text{Voltage gain } (A_{V1}) = \frac{A_{i1} \times R_{L1}}{R_{i1}}$$

where,

$$R_{L1} = R_{C1} \parallel R_{i2}$$

Voltage gain (A_V):


$$A_V = A_{V1} \times A_{V2}$$

$$\text{Overall voltage gain } (A_{Vs}) = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s}$$

$$V_i = V_s \times \frac{R_{i1}}{R_s + R_{i1}}$$

$$A_{Vs} = \frac{V_o}{V_i} \times \frac{R_{i1}}{R_s + R_{i1}}$$
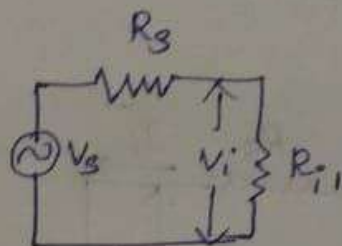
$$= A_v \times \frac{R_{i1}}{R_s + R_{i1}}$$



Output resistance (R_o) = ∞


$$R'_{o1} = R_{o1} \parallel R_{c1}$$

$$R_{o2} = \frac{R_s + h_{ie}}{1 + h_{fe}} = \frac{R'_{o1} + h_{ie}}{1 + h_{fe}}$$

$$R_o = R_{o2} \parallel R_{E2}$$

Overall current gain (A_i):
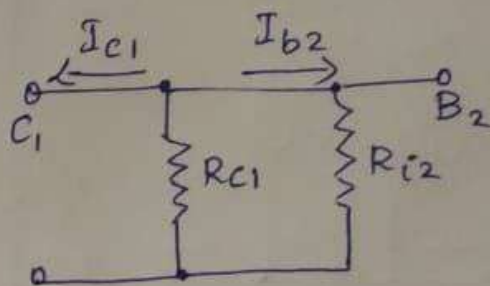
$$A_i = \frac{I_o}{I_{b1}} = \frac{I_o}{I_{e2}} \times \frac{I_{e2}}{I_{b2}} \times \frac{I_{b2}}{I_{c1}} \times \frac{I_{c1}}{I_{b1}}$$




Where,

$$\frac{I_o}{I_{e2}} = -1, \quad \frac{I_{e2}}{I_{b2}} = -A_{i2}$$

$$\frac{I_{b2}}{I_{c1}} = -\frac{R_{c1}}{R_{i2} + R_{c1}}$$

$$\frac{I_{c1}}{I_{b1}} = A_{i1}$$

n-stage Cascaded Amplifier:

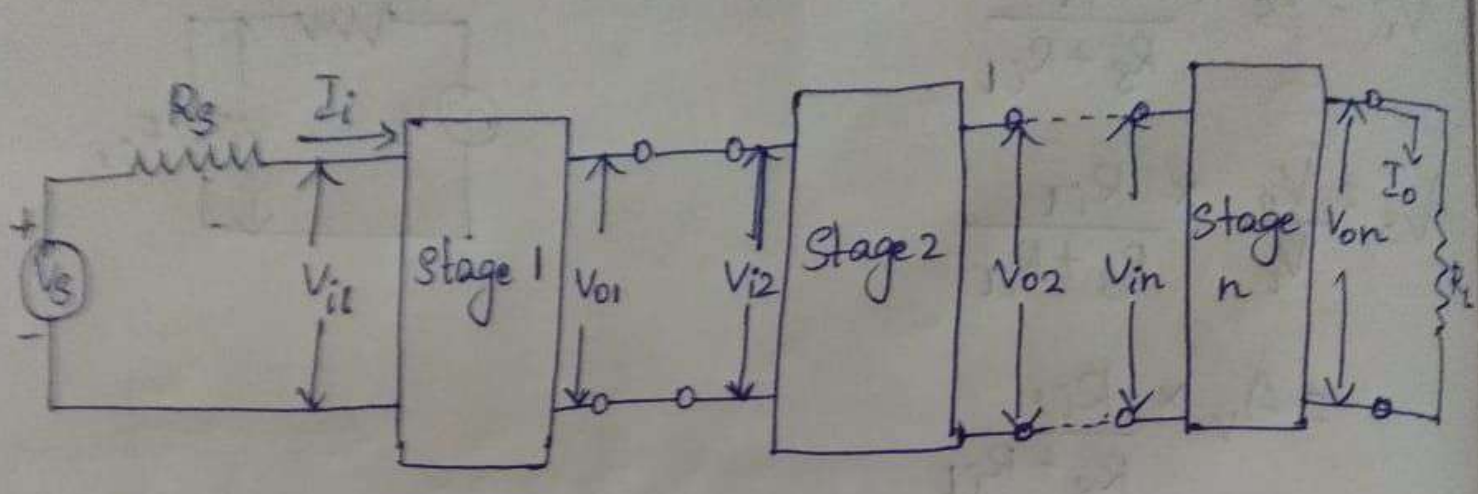

$$A_v = A_{v1} \times A_{v2} \times \dots \times A_{vn}$$

The voltage gain of the k^{th} stage is,

$$A_{vk} = \frac{A_{ik} R_{Lk}}{R_{ik}}$$