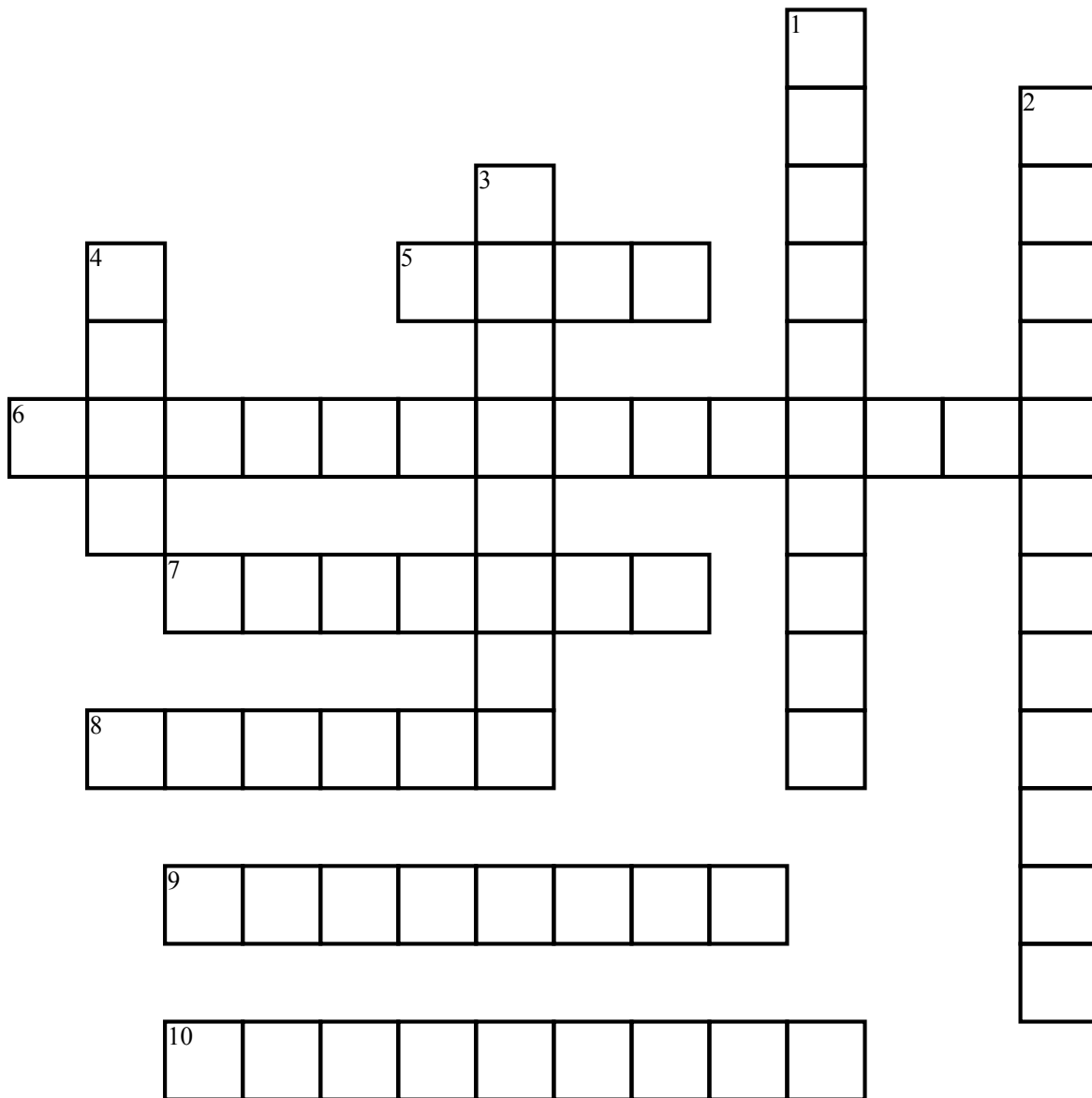


Name: \_\_\_\_\_

Date: \_\_\_\_\_

# COMPONENTS OF A CIRCUIT



## Across

5. to provide electrical energy
6. Connects the components together.
7. To measure current strength.
8. converts electrical energy into sound energy
9. a resistors whose resistance can be adjusted higher or lower.
10. to measure voltage or potential difference

## Down

1. stops the flow of current
2. allows the flow of current
3. A component that opposes or inhibits electrical current in a circuit.
4. to convert electrical energy into light energy