



# **SNS COLLEGE OF TECHNOLOGY**

(An Autonomous Institution)

Re-accredited by NAAC with 'A+' Grade

Approved by AICTE, New Delhi, Recognized by UGC & Affiliated by Anna University, Chennai  
Coimbatore-641035

## **DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING**

**19EET301 / POWER ELECTRONICS AND DRIVES**

**III YEAR / V SEMESTER**

**UNIT – IV : PART B - DC DRIVES**



**THYRISTOR CONVERTER  
FED DC DRIVE – 1Q, 2Q  
OPERATION**



# TOPIC OUTLINE


What we'll discuss?



- Single phase 1Q drive
- Single phase 2Q drive
- Three phase 2 Q drive
  - A case study video



# SINGLE PHASE 1 Q DRIVE

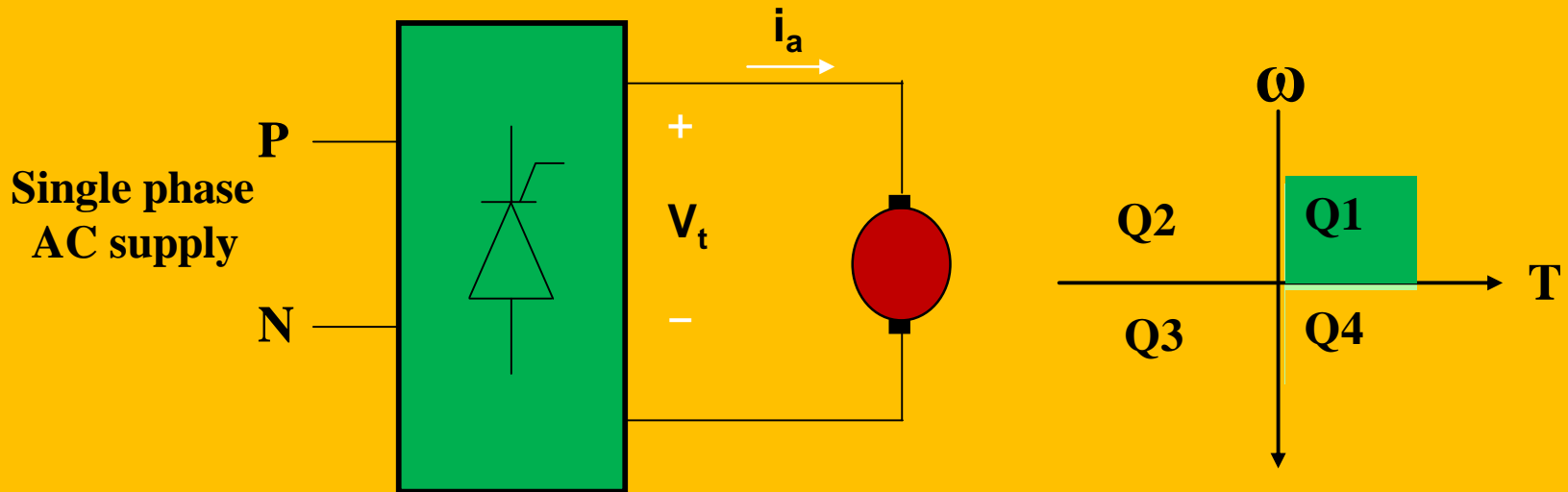


## BLOCK DIAGRAM & QUADRANT OF OPERATION




# SINGLE PHASE 1 Q DRIVE

**CIRCUIT  
DIAGRAM**

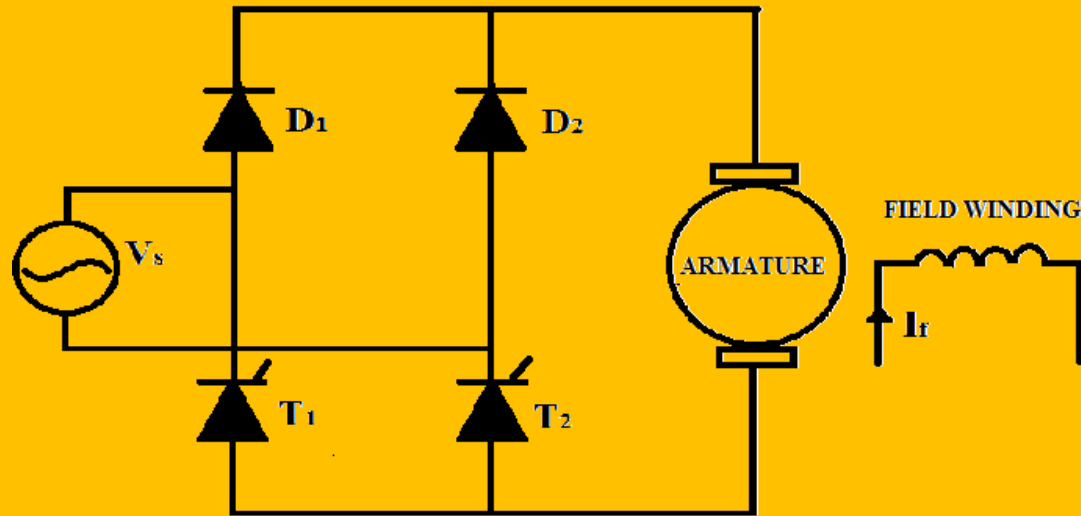

**WAVEFORM**

**Input Voltage,  $V_s$**

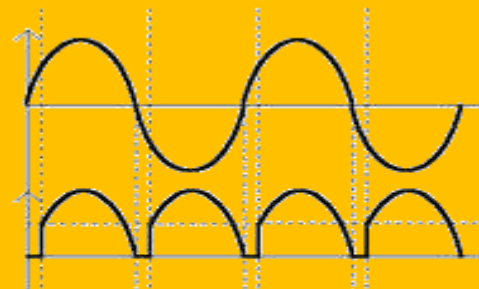

**Output Voltage,  $V_a$**



# SINGLE PHASE 1 Q DRIVE

**A CASE STUDY VIDEO  
OF  
FAN DRIVE**



# SINGLE PHASE 1 Q DRIVE

## CALCULATION OF OUTPUT VOLTAGE

The circuit – single phase half controlled converter fed DC drive– 1 Quadrant drive

**INPUT VOLTAGE:** 230 V AC is RMS value.

**OUTPUT VOLTAGE:**  $V_a = \frac{230\sqrt{2}}{\pi} (1 + \cos \alpha)$  is Average value.

**Switch position is Low :** Assume  $\alpha = 170^\circ$ , then  $V_a = \left[ \frac{(230\sqrt{2})}{\pi} \right] (1 + \cos 170^\circ)$   
 $V_a = 61 \text{ V}$


**Switch position is Med :** Assume  $\alpha = 75^\circ$ , then  $V_a = \left[ \frac{(230\sqrt{2})}{\pi} \right] (1 + \cos 75^\circ)$   
 $V_a = 129 \text{ V}$

**Switch position is High :** Assume  $\alpha = 10^\circ$ , then  $V_a = \left[ \frac{(230\sqrt{2})}{\pi} \right] (1 + \cos 10^\circ)$   
 $V_a = 204 \text{ V}$

**Greater the voltage, higher the speed of motor.**




# SINGLE PHASE 2 Q DRIVE

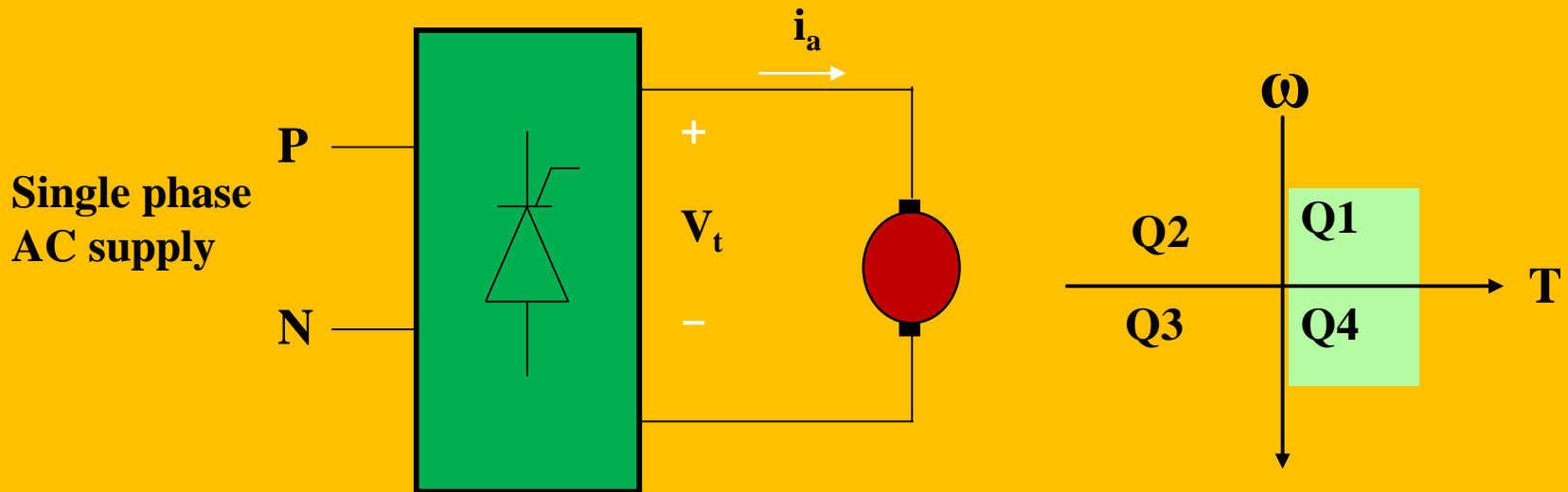

## BLOCK DIAGRAM & QUADRANT OF OPERATION



# SINGLE PHASE 2 Q DRIVE

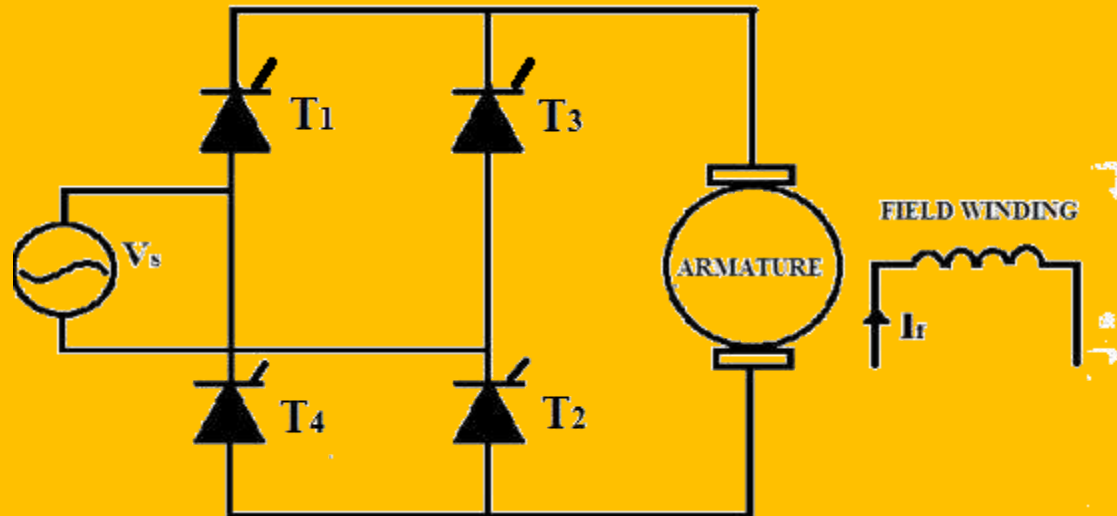


**CIRCUIT DIAGRAM**





# SINGLE PHASE 2 Q DRIVE

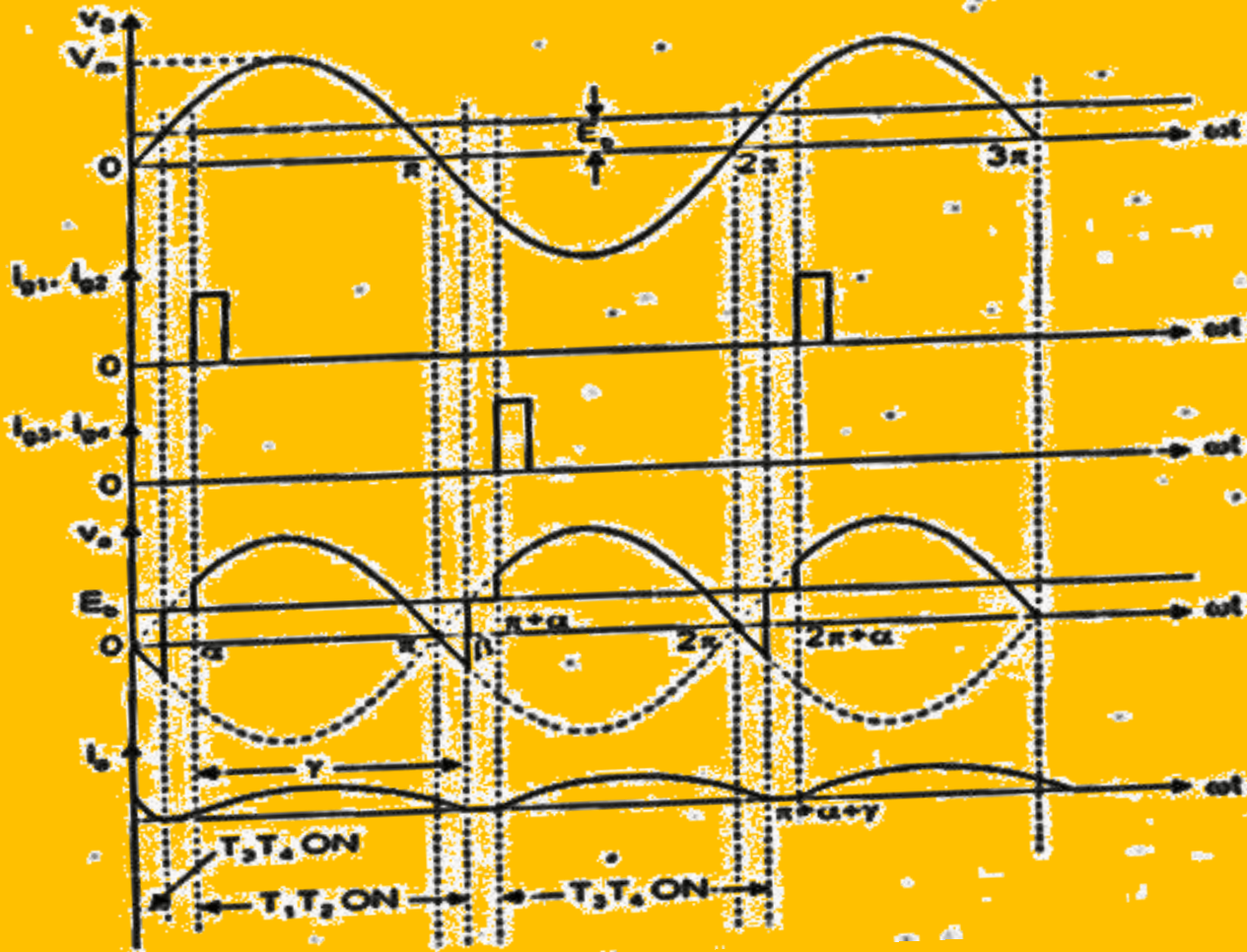

**INPUT /  
OUTPUT  
WAVEFORMS**



# SINGLE PHASE 2 Q DRIVE

**Back EMF,  $E_b$  :  $V_a - I_a R_a$**

**Speed,  $N$  :  $E_b / \Phi$**

**Let,**

**$V_i$ , Input Voltage (AC) = 220 V (RMS value),  $I_a = 150$  A,  $R_a = 0.06 \Omega$ ,  $\Phi = 0.2$  (K)**

$$V_a, \text{ Output Voltage (DC)} = \frac{2V_m}{\pi} \cos \alpha$$

**(i) If  $\alpha = 30$ , then**  $V_a = \{ [2 * 220 \sqrt{2}] / \pi \} \cos 30 = 172 \text{ V}$


$E_b = 163 \text{ V}$

Therefore speed,  $N = 163 / 0.2 = \mathbf{815 \text{ RPM}}$

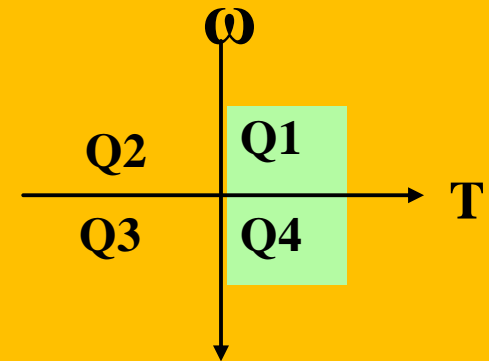**(ii) If  $\alpha = 160$ , then**  $V_a = -186 \text{ V}$

$E_b = -195 \text{ V}$



Therefore speed,  $N = -195 / 0.2 = \mathbf{-975 \text{ RPM}}$





# THREE PHASE 2 Q DRIVE


Three phase  
AC supply

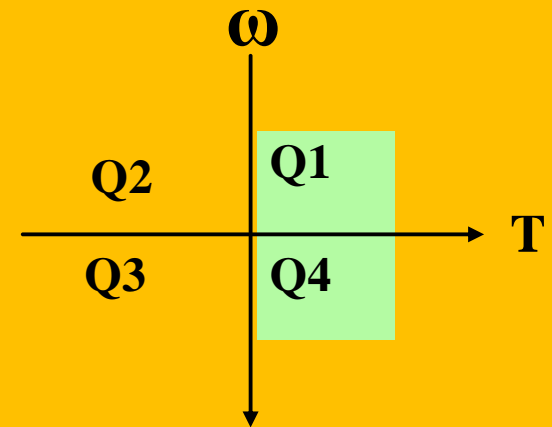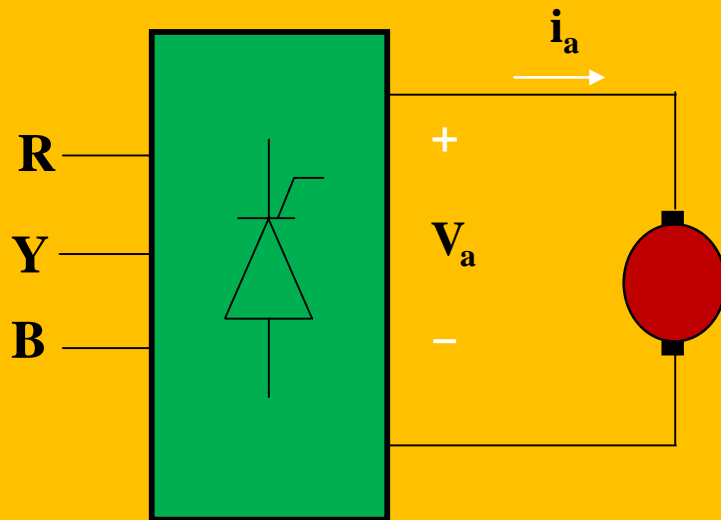

**BLOCK DIAGRAM & QUADRANT OF OPERATION**



# THREE PHASE 2 Q DRIVE

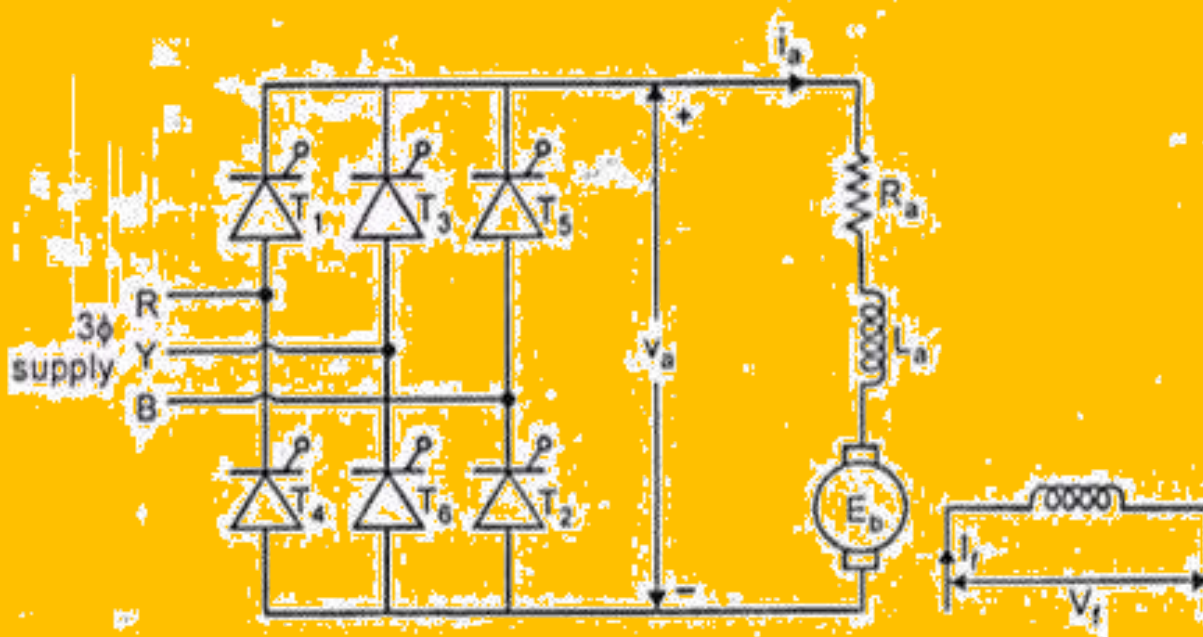

**CIRCUIT DIAGRAM OF SEPARATELY EXCITED DC MOTOR DRIVE**



# Evaluation Time

Summarize the  
content...



**Assignment:**

Draw the thyristor fed circuit diagram  
for DC Series Motor

Thanking You.