



# **SNS COLLEGE OF TECHNOLOGY**

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



## **Department of Electrical and Electronics Engineering**

### **23EET101 / BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING**

### **I YEAR / I SEMESTER**

### **UNIT-I:AC CIRCUITS**

### **NODAL ANALYSIS**

15/9/2023

BEEE/S.SHARMILA,AP/EEE

1



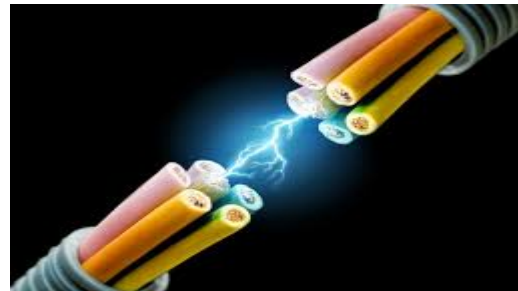
# TOPIC OUTLINE



Electricity  
?

- Voltage, Current, Resistance
- Nature of Current
- Ohms Law



15/9/2023

BEEE/S.SHARMILA,AP/EEE



2


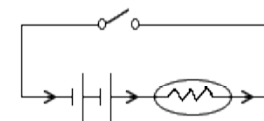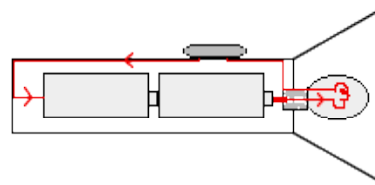
## Basic Elements of a Circuit



- An electric circuit provides a complete path for current to flow
- A basic circuit must include:
  - Power Source (battery)
  - Complete Path (wires)
  - Load (resistor, light, motor, etc.)
- Many circuits also include:
  - Control Devices (switch, etc.)
  - Protective Devices (fuse, circuit breaker, etc)





## Types of Circuits



Circuits with multiple loads can be placed into one of three categories: Series, Parallel, & Series-Parallel



- These are based on paths of current flow through the circuit


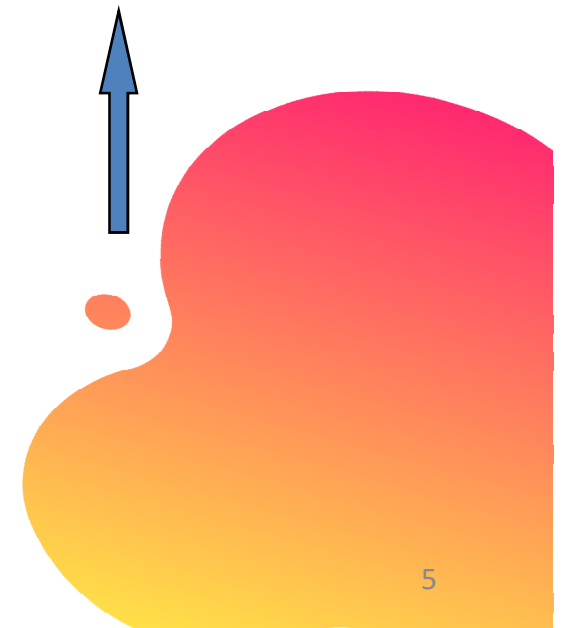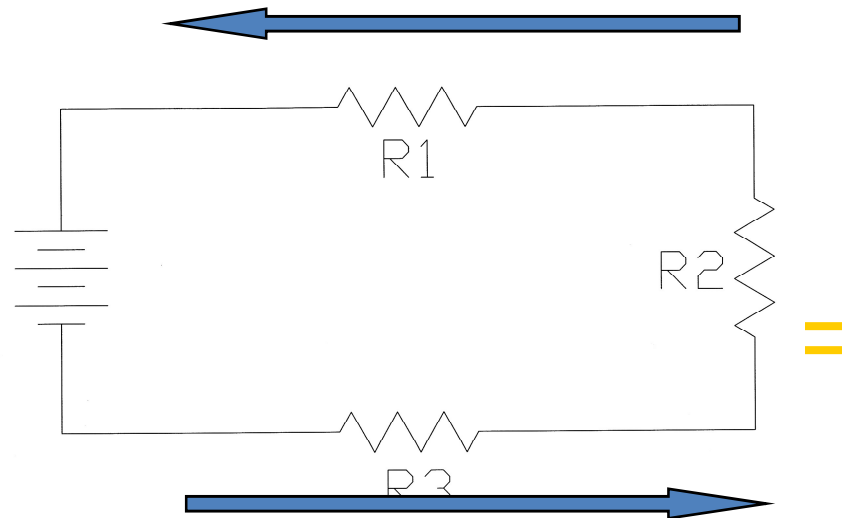
## Series Circuits




- Only allow current to flow through one path from – to + through the loads
- Current only has one way to go from one side of the power source to the other




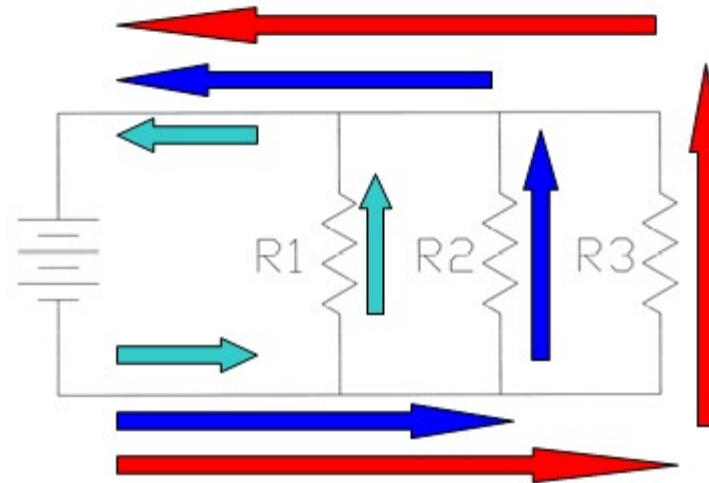
## Parallel Circuits

- Allows current to take Multiple Paths from – to + through the loads.  
Current can follow different routes from the source, through the loads, and back to the source





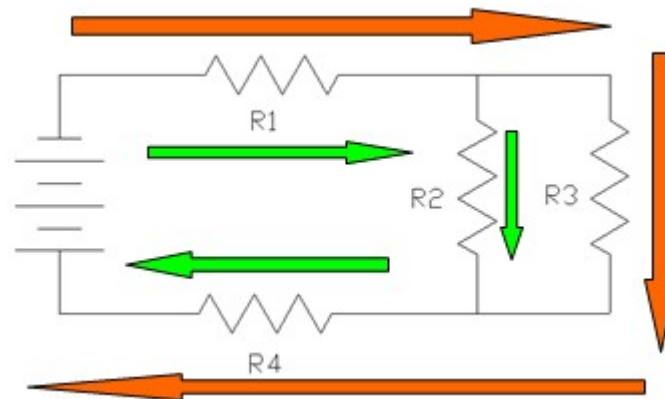
## Series-Parallel Circuits



- Contains areas of both Series & Parallel circuits
- Some sections allow multiple paths for current flow
- Other areas only allow one path for current flow
- Must have at least three loads



15/9/2023

BEEE/S.SHARMILA,AP/EEE





## Resistance Calculations

- Because some circuits allow current to follow multiple paths, current divides among these paths
- This reduces the total current of these sections
- Therefore, different resistance formulas must be used for different circuits





## Series Circuit Calculations

- Only allow current to follow one path
- Total resistance is equal to the sum of all the individual resistances
- Formula  $R_t = R_1 + R_2 + R_3 \dots$

$$R_1 = 10\Omega$$


$$R_2 = 20\Omega$$

$$R_3 = 30\Omega$$

$$R_t = R_1 + R_2 + R_3$$

$$R_t = 10\Omega + 20\Omega + 30\Omega$$

$$R_t = 60\Omega$$

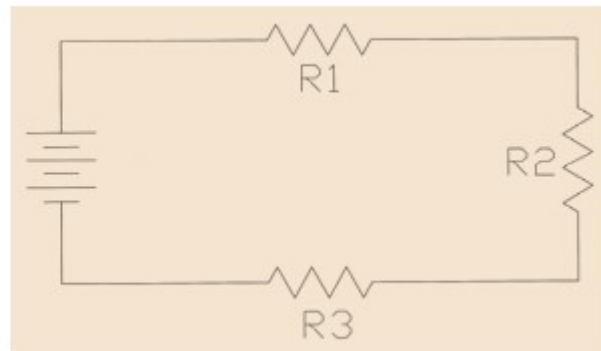

ECED - Dr.D.Revathi ,AP/EEE  
BEEE/S.SHARMILA,AP/EEE





## Parallel Circuit Calculations



- Allow current to follow Multiple Paths
- Current divides among paths
- Total resistance is always less than smallest resistor
- Resistance Formula:  $R_t = 1 / [(1/R_1) + (1/R_2) + (1/R_3) \dots]$

- This is Known as the Reciprocal Formula

$$R_1 = 10\Omega \quad R_2 = 20\Omega \quad R_3 = 30\Omega$$


$$R_t = 1 / [(1/R_1) + (1/R_2) + (1/R_3)]$$

$$R_t = 1 / [(1/10) + (1/20) + (1/30)]$$

$$R_t = 1 / [.1 + .05 + .033]$$

$$R_t = 1 / .183$$

$$R_t = 5.45\Omega$$

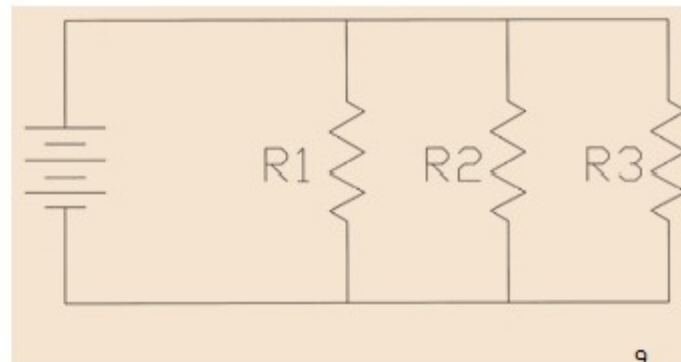



## Parallel Circuit Calculations (Only Two Resistors)




If only Two resistors are in parallel, then another formula can also be used to calculate total resistance

This formula is:  $R_t = (R_1 \times R_2) / (R_1 + R_2)$

Total resistance is always less than smallest resistor
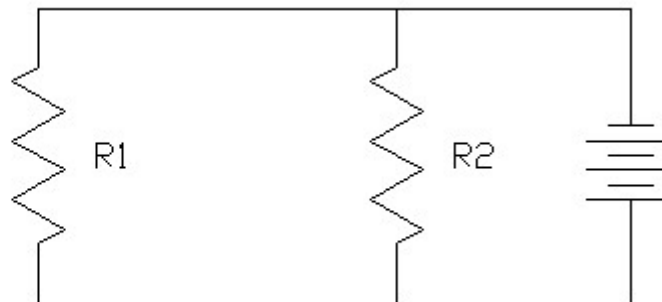
$$\begin{aligned}R_1 &= 20\Omega & R_2 &= 20\Omega \\R_t &= (R_1 \times R_2) / (R_1 + R_2) \\R_t &= (20 \times 20) / (20 + 20) \\R_t &= 400 / 40 \\R_t &= 10\Omega\end{aligned}$$





## Parallel Circuit Calculations (All Resistors Are the Same)



If all of the resistors in the circuit are equal, then this formula may be used:

$$R_t = R / N \quad (N = \text{Number of resistors/ loads})$$


Total resistance is always less than smallest resistor

$$R_1 = 30\Omega \quad R_2 = 30\Omega \quad R_2 = 30\Omega$$

$$R_t = R / N$$

$$R_t = 30 / 3$$

$$R_t = 10\Omega$$

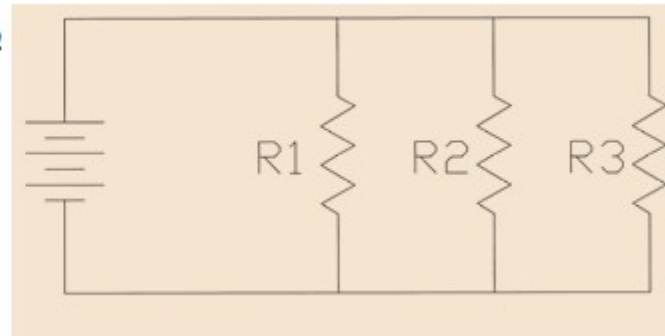



## Series-Parallel Circuit Calculations



- Contain series & parallel elements
- Must use series & parallel formulas
- First determine Parallel R-value, then add to series sections

$$R1 = 10\Omega \quad R2 = 10\Omega \quad R3 = 10\Omega \quad R4 = 10\Omega$$

$$Rt = (R1 \times R2) / (R1 + R2)$$

$$Rt = (10 \times 10) / (10 + 10)$$


$$Rt = 100 / 20$$

$$Rt = 5\Omega$$

$$Rt = R1 + R2 + R3$$

$$Rt = 10\Omega + 5\Omega + 10\Omega$$

$$Rt = 25\Omega$$

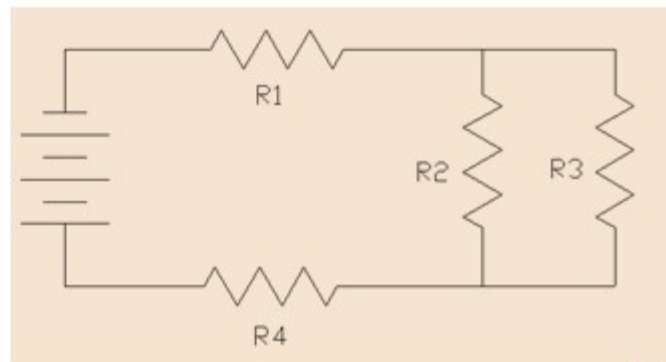


12





# Resistance Formula Flow Chart
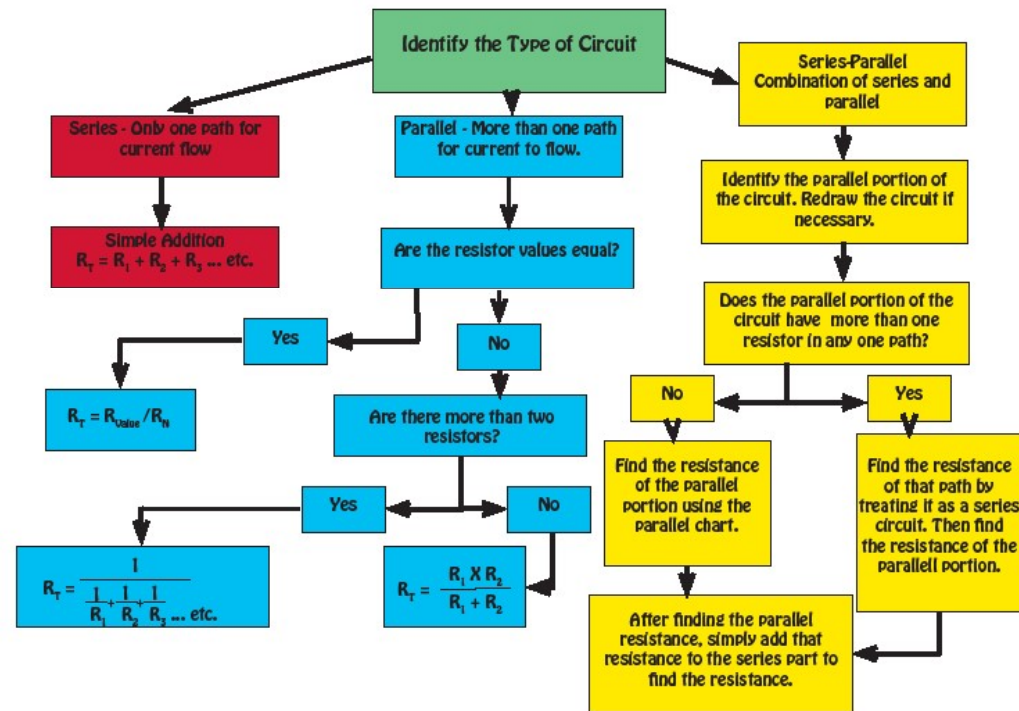
## Calculating Total Resistance Flow Chart





## Practice #1



- What kind of circuit is it?
- Series Circuit
- What Formula can be used?
- $R_t = R_1 + R_2 + R_3$
- What is the total resistance?

$$R_1 = 30\Omega$$


$$R_2 = 50\Omega$$

$$R_3 = 70\Omega$$

$$R_t = R_1 + R_2 + R_3$$

$$R_t = 30\Omega + 50\Omega + 70\Omega$$

$$\mathbf{R_t = 150\Omega}$$

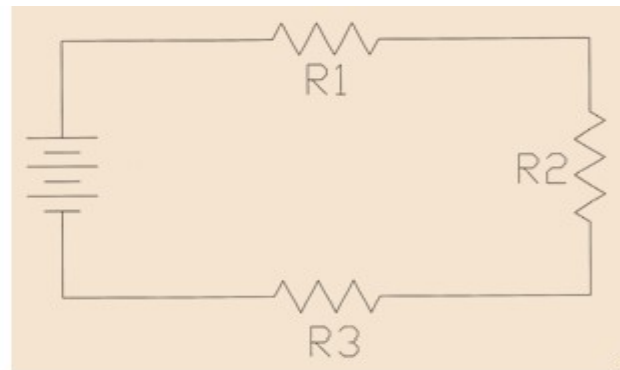

14

15/9/2023



15



## Practice #2



- **What kind of circuit is it?**

Parallel Circuit

- **What Formula can be used?**

$$R_t = 1 / [(1/R_1) + (1/R_2) + (1/R_3) \dots]$$

or ...  $R_t = (R_1 \times R_2) / (R_1 + R_2)$

- **What is the total resistance?**


$$R_1 = 10\Omega \quad R_2 = 20\Omega$$

$$R_t = (R_1 \times R_2) / (R_1 + R_2)$$

$$R_t = (10 \times 20) / (10 + 20)$$

$$R_t = 200 / 30$$

$$\mathbf{R_t = 6.67\Omega}$$

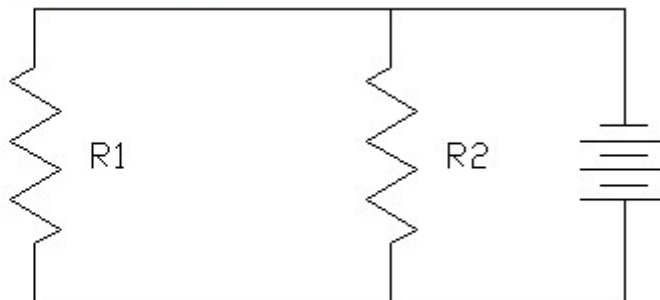





## Practice #3



- **What kind of circuit is it?**  
Series-parallel
- **What Formula can be used?**  
 $R_t = (R_1 \times R_2) / (R_1 + R_2)$  &  $R_t = R_1 + R_2 + R_3$
- **What is the total resistance?**

$$R_1 = 5\Omega \quad R_2 = 4\Omega \quad R_3 = 6\Omega \quad R_4 = 5\Omega$$


$$R_t = (R_1 \times R_2) / (R_1 + R_2)$$

$$R_t = (4 \times 6) / (4 + 6)$$

$$R_t = 24 / 10$$

$$R_t = 2.4\Omega$$

$$R_t = R_1 + R_2 + R_3$$

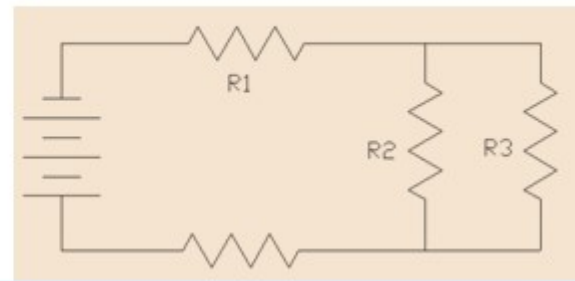



# RECAP...


15/9/2023

BEEE/S.SHARMILA,AP/EEE





# RECAP...

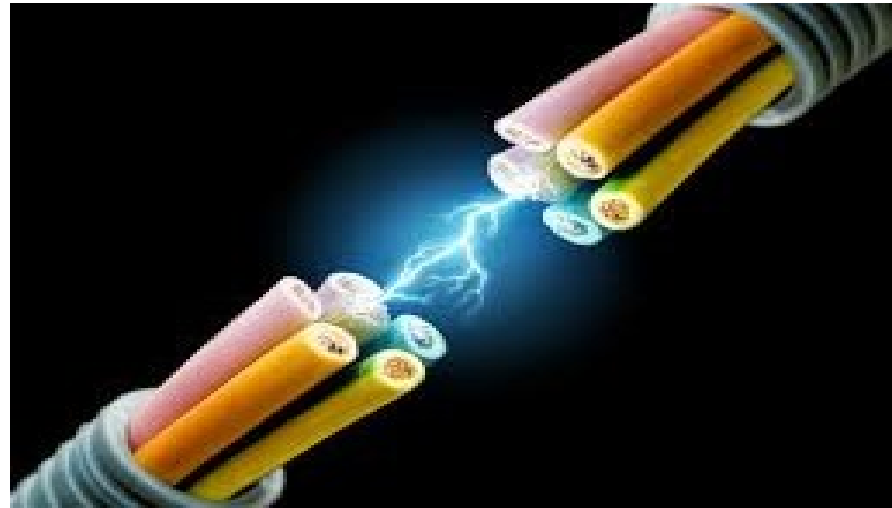

# ...THANK YOU

