



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB201 –ANALOG ELECTRONIC CIRCUITS

II Year B.E.ECE - III Semester

TOPIC– LC OSCILLATORS



OSCILLATOR (RECAP)




➤ Oscillators convert a DC input (the supply voltage) into an AC output (the waveform), which can have a wide range of different wave shapes and frequencies

To operate as an oscillator, it must have the following three characteristics.


- Some form of Amplification
- Positive Feedback (regeneration)
- A Frequency determine feedback network

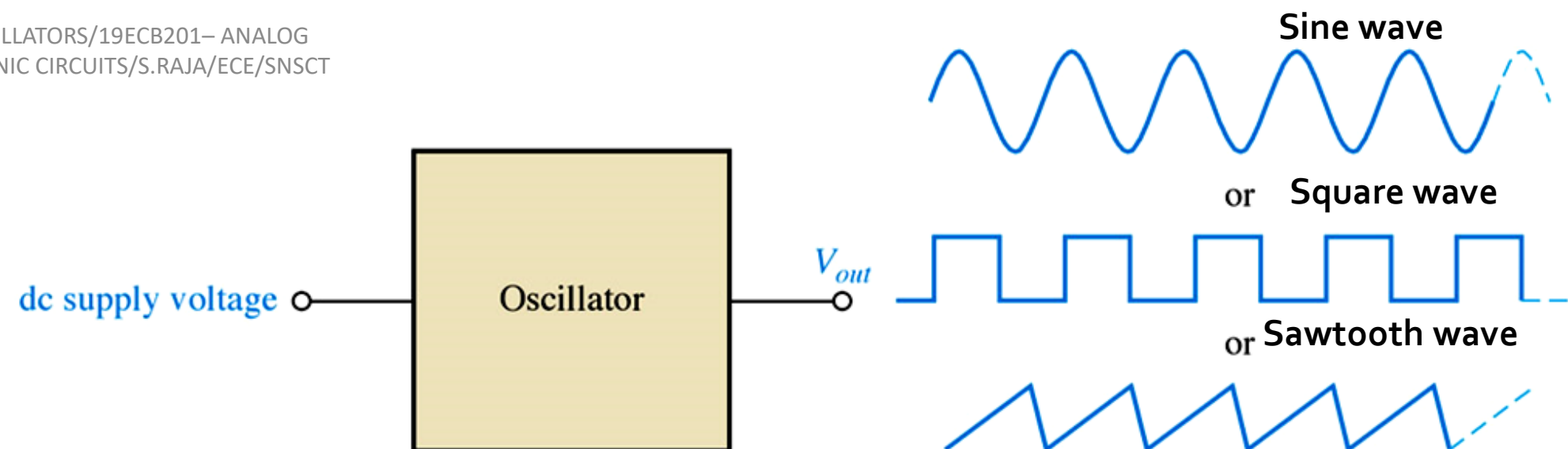LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT





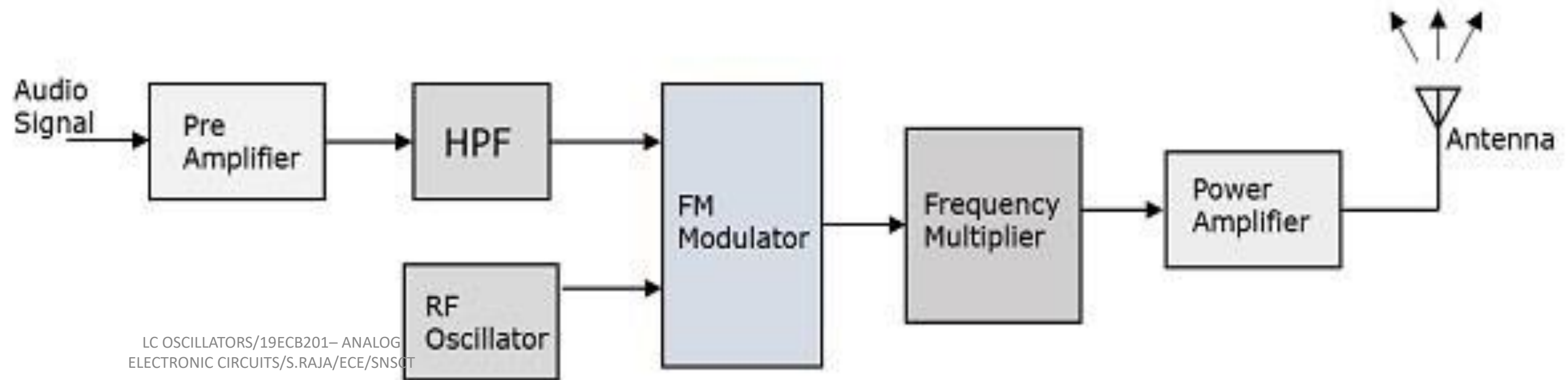
Application of Oscillators (FM Transmitter)



LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT



CLASSIFICATION OF OSCILLATORS

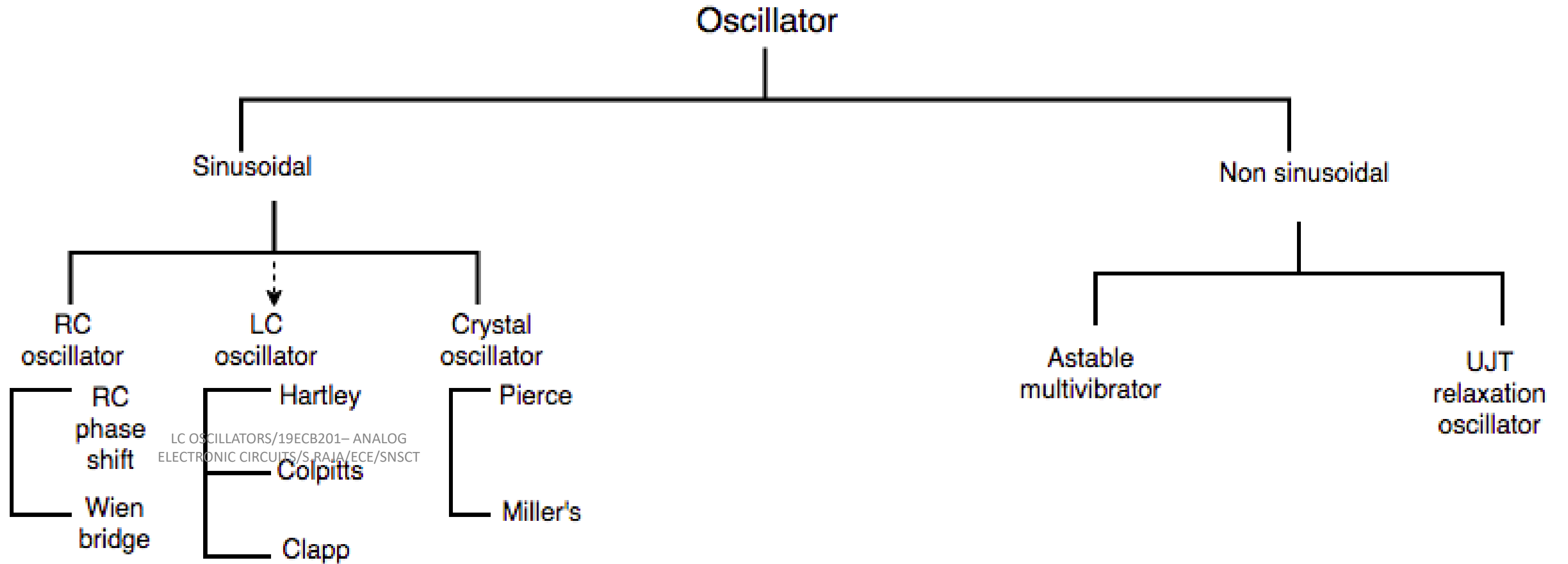




LC OSCILLATORS



- The oscillators which use the elements L and C to produce the oscillations are called LC oscillators
- These oscillators are used for high frequency range from 200 kHz up to few GHz.

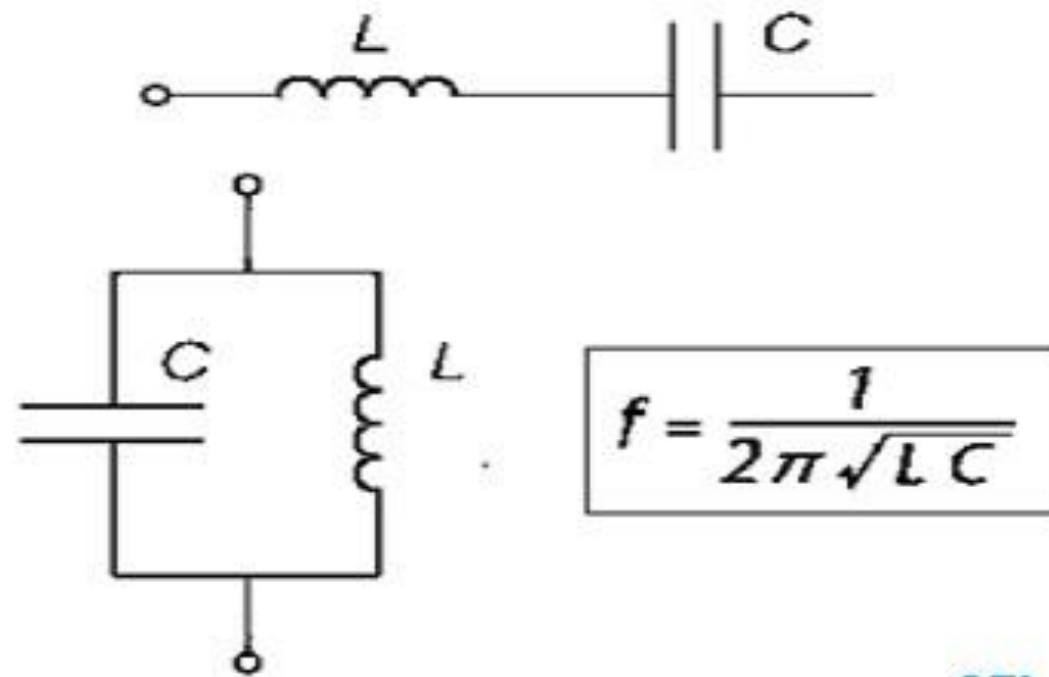LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT





Why LC oscillators?




- **Why LC oscillator is better than RC oscillator?**
- LC oscillators are preferred at higher frequencies because of their high-Quality factor and a wider range of frequencies.
- LC oscillators offer greater stability, and produce sinusoidal waveforms with fewer harmonics.
- LC circuit is used for generating high frequency because as the frequency goes higher and higher, physical size of LC also becomes smaller.
- LC oscillators can be designed using OP-AMP and Transistors.

12/3/2023

LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT



Tank circuit

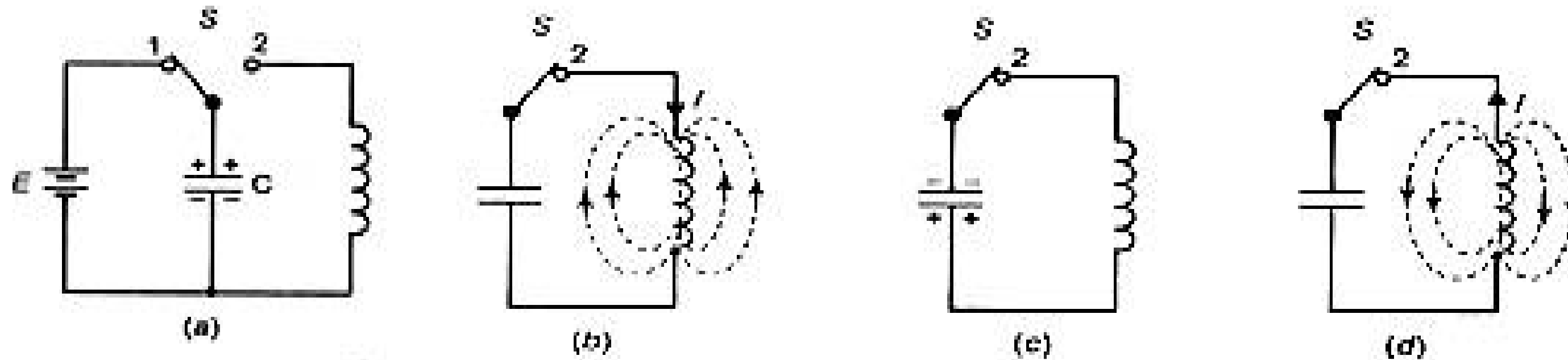


LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT

➤ The capacitor stores energy in the form of an electrostatic field and which produces a potential (static voltage) across its plates, while the inductive coil stores its energy in the form of an electromagnetic field.



Tank circuit

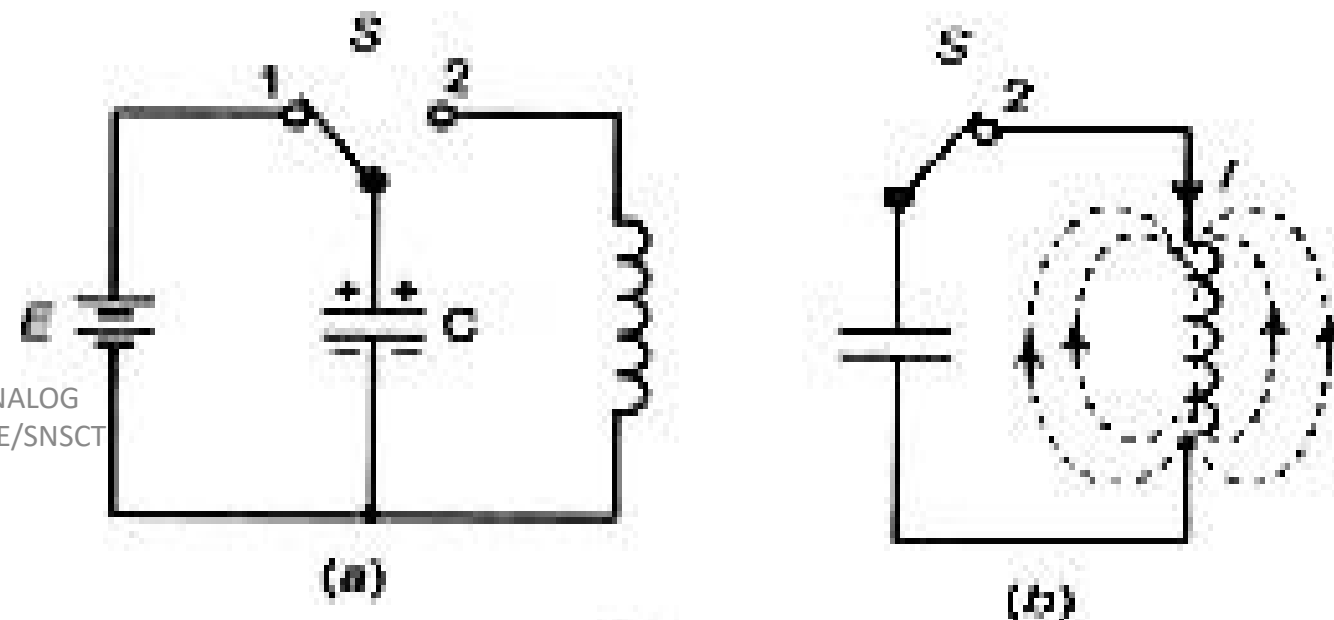- The capacitor is charged up to the DC supply voltage, V by putting the switch in position 1.
- When the capacitor is fully charged the switch changes to position 2.



LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT





Tank circuit



- The charged capacitor is now connected in parallel across the inductive coil so the capacitor begins to discharge itself through the coil.
- The voltage across C starts falling as the current through the coil begins to rise. This rising current sets up an electromagnetic field around the coil which resists this flow of current.



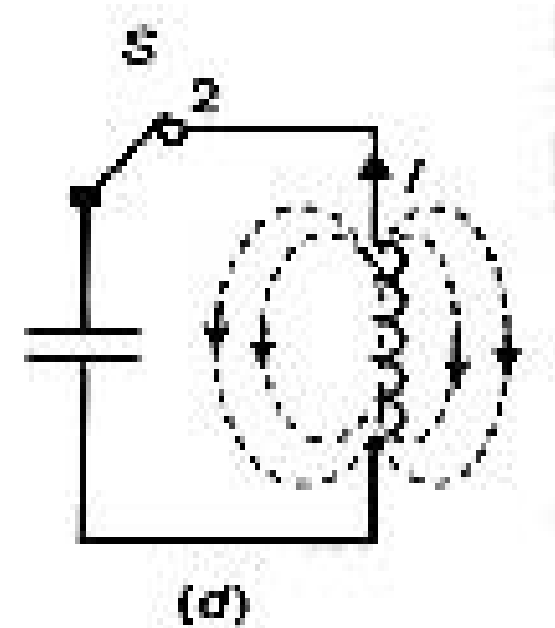
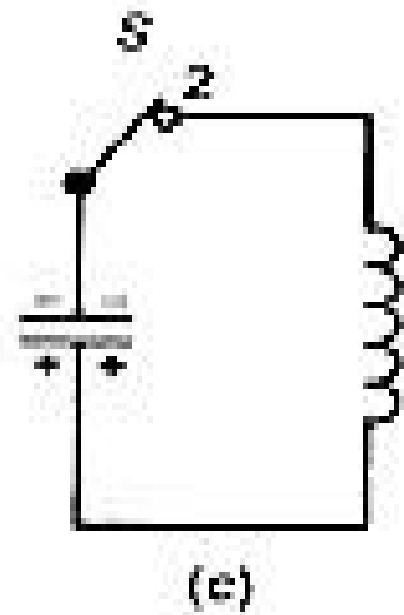
LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT





Tank circuit

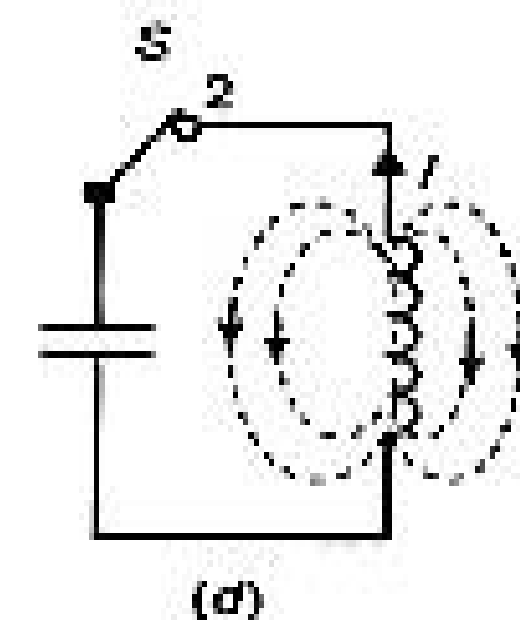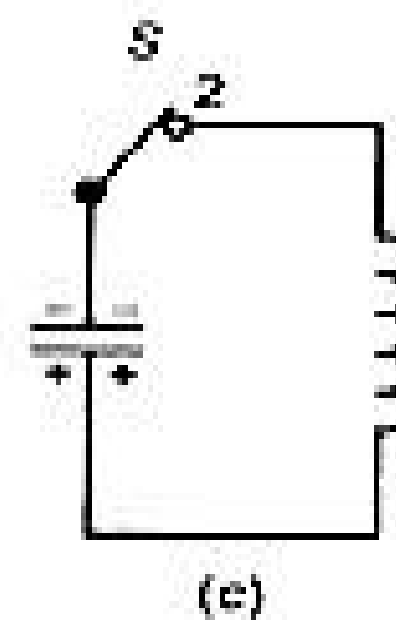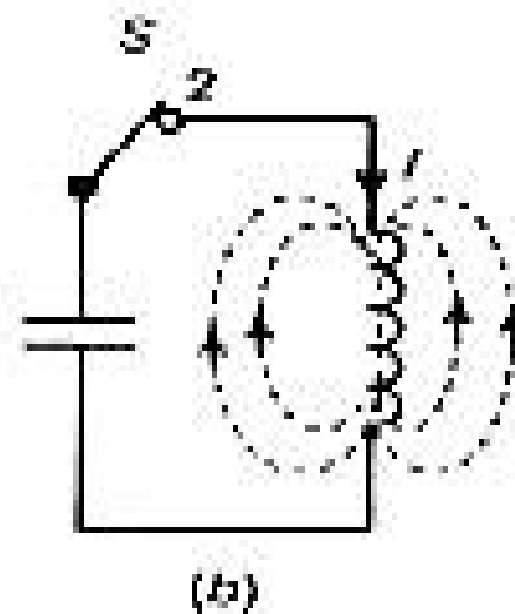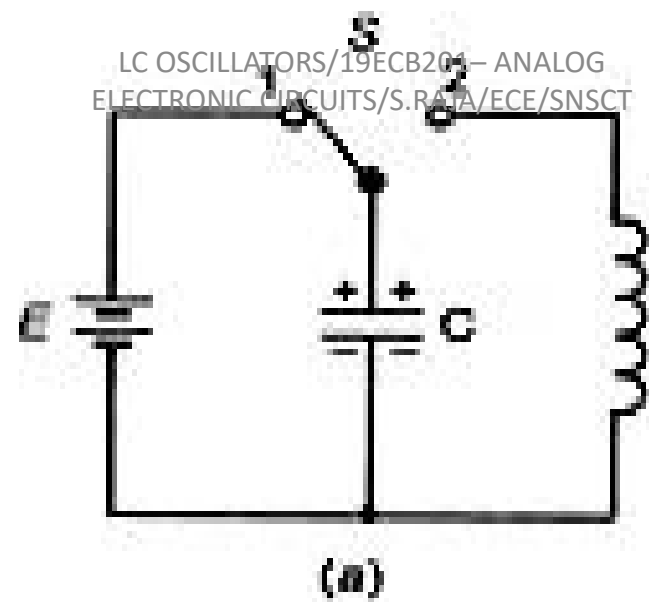- When the capacitor, C is completely discharged the energy that was originally stored in the capacitor, C as an electrostatic field is now stored in the inductive coil, L as an electromagnetic field around the coils windings.
- As there is now no external voltage in the circuit to maintain the current within the coil, it starts to fall as the electromagnetic field begins to collapse.






Tuned circuit



- A back emf is induced in the coil ($e = -L \frac{di}{dt}$) keeping the current flowing in the original direction.
- This current now charges up the capacitor, c with the opposite polarity to its original charge.
- Capacitor continues to charge up until the current reduces to zero and the electromagnetic field of the coil has collapsed completely.
- The capacitor now starts to discharge again back through the coil and the whole process so repeated.
- The polarity of the voltage changes as the energy is passed back and forth between the capacitor and inductor producing an AC type sinusoidal voltage and current waveform.



Tank circuit working

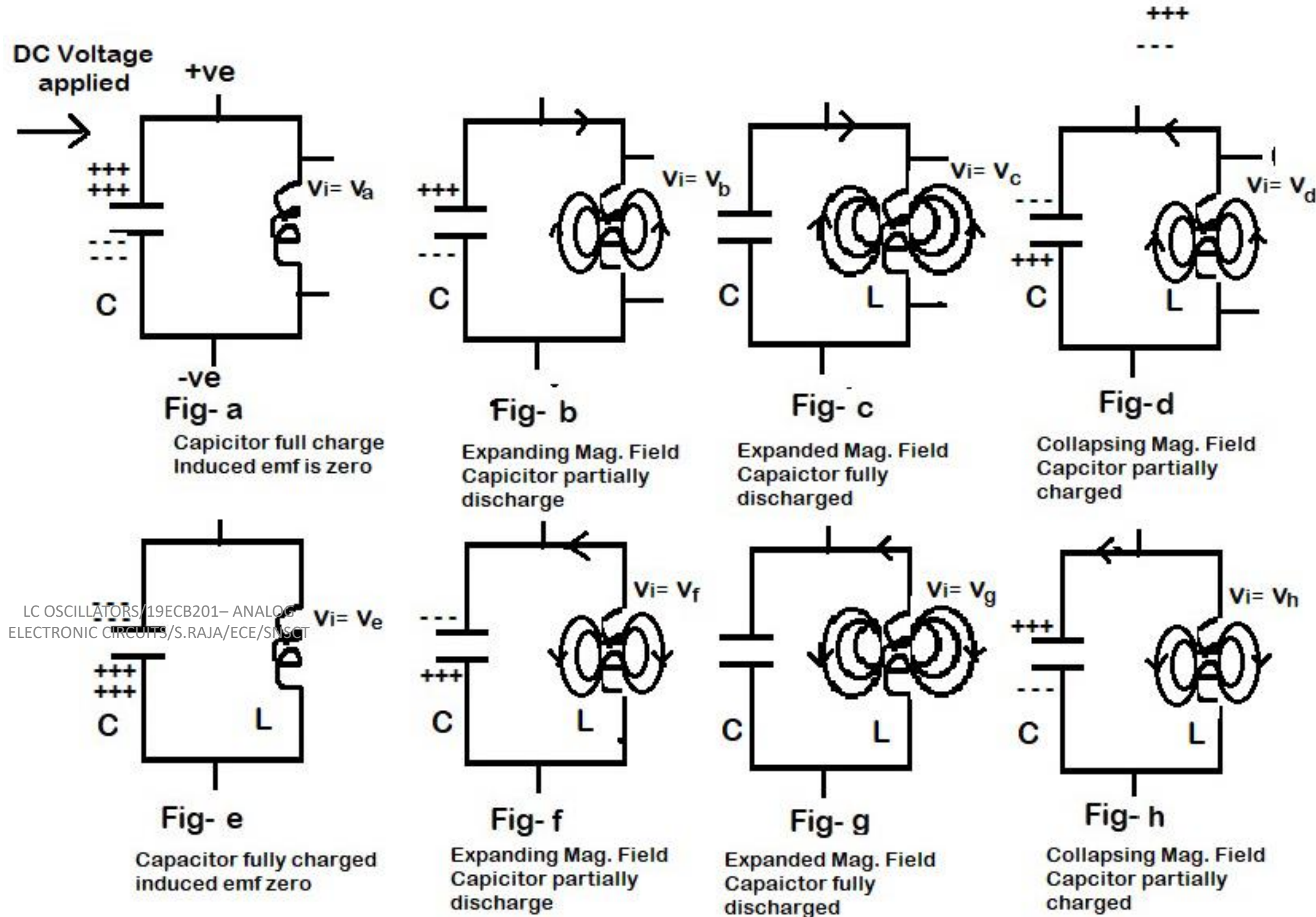



Activity

WHO AM I?

Amplifier

Tuned Amplifier

Oscillator

Differential amplifier

Feedback amplifier

LC Oscillator

Stagger tuned Amp




TYPES OF LC OSCILLATORS



LC oscillators

- Hartley
- Colpitts
- Crystal

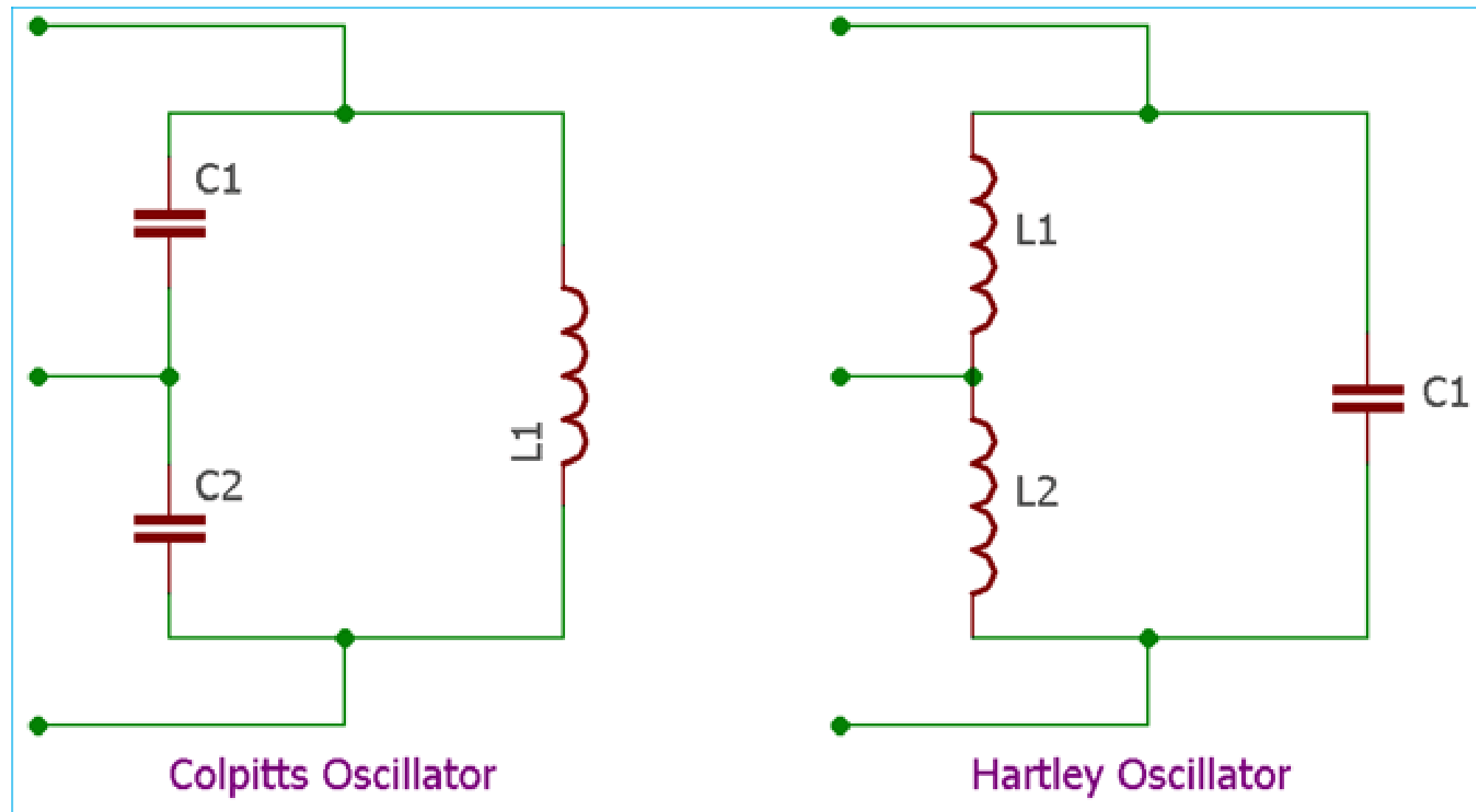LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT






Hartley oscillator



- Hartley Oscillator is a device that generates oscillatory output (sinusoidal).
- It uses **two inductive** reactance and **one capacitive** reactance in its feedback network.
- It consists of an amplifier linked to an oscillatory circuit, also called LC circuit or tank circuit. The function of tank circuit is to tune a certain frequency.
- However they can also be designed to produce oscillations in the **low audio-frequency** range. But for the low-frequency operation, the inductors used will be very large in value, i.e of milli Henrie range and hence very large in physical size.



Hartley oscillator

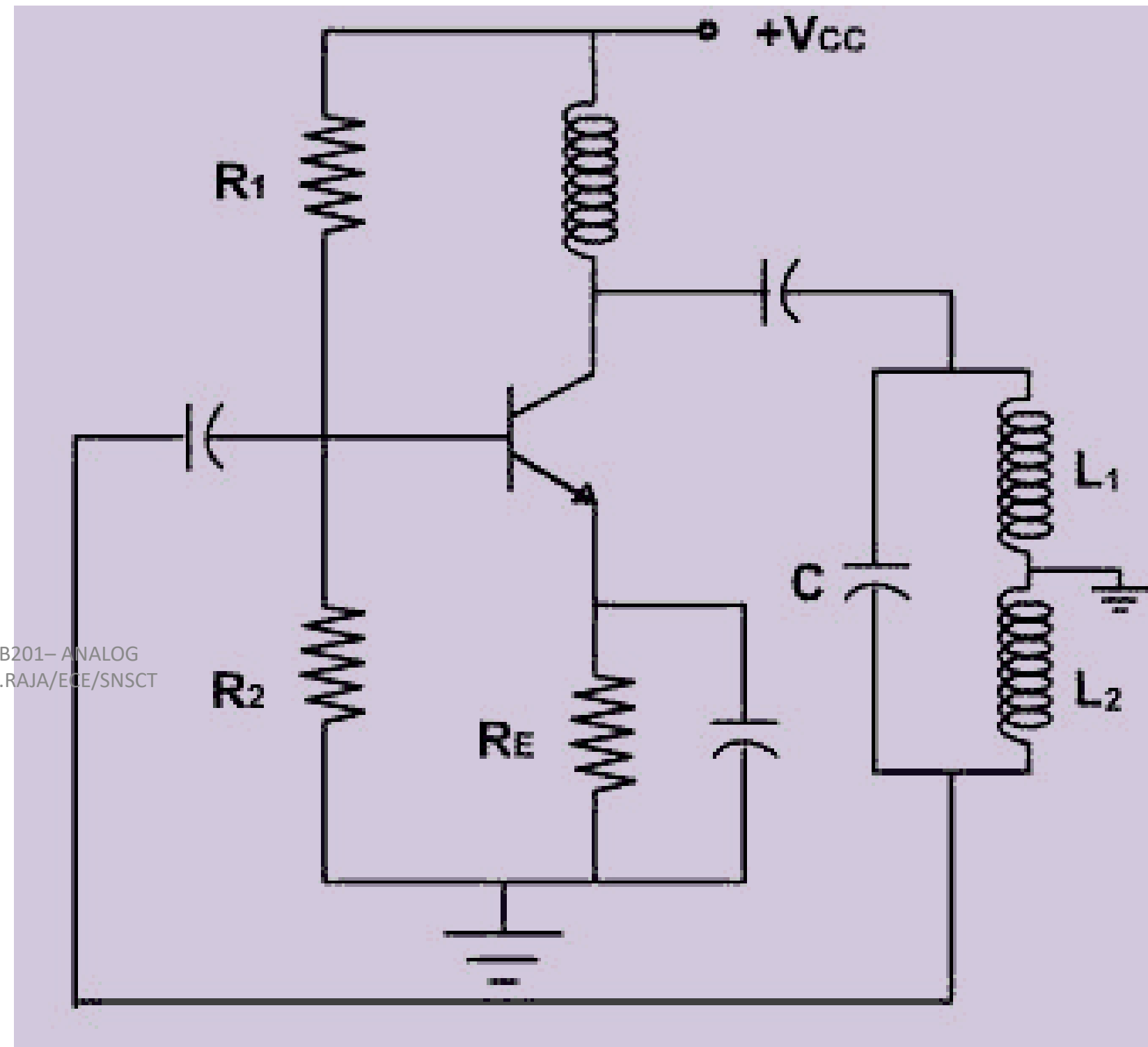

LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT

12/3/2023



Working of Hartley oscillator



- When the collector supply is given, a transient current is produced in the oscillatory or tank circuit. The oscillatory current in the tank circuit produces a.c. voltage across L1.
- As the CE configured transistor provides 180° phase shift, another 180° phase shift is provided by the tank circuit, which makes 360° phase shift between the input and output voltages.
- This makes the feedback positive which is essential for the condition of oscillations. When the loop gain $|\beta A|$ of the amplifier is greater than one, oscillations are sustained in the circuit.

LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT

12/3/2023



Applications



- The Hartley oscillator is to produce a sine wave with the desired frequency
- Hartley oscillators are mainly used as radio receivers. Also note that due to its wide range of frequencies, it is the most popular oscillator
- The Hartley oscillator is Suitable for oscillations in RF (Radio-Frequency) range, up to 30MHZ

LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT



LC Oscillators Summary



- For oscillations to exist an oscillator circuit must contain a reactive (frequency dependant) component either an “Inductor”, (L) or a “Capacitor”, (C) as well as a DC power source.
- In a simple inductor-capacitor, LC circuit, oscillations become damped over time due to component and circuit losses.
- Voltage amplification is required to overcome these circuit losses and provide positive gain.
- The overall gain of the amplifier must be greater than one, unity.
- LC OSCILLATORS/19ECB201- ANALOG ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT Oscillations can be maintained by feeding back some of the output voltage to the
- tuned circuit that is of the correct amplitude and in-phase, (0°).

12/3/2023



ASSESSMENT



1. An inductance of 200mH and a capacitor of 10pF are connected together in parallel to create an LC oscillator tank circuit. Calculate the frequency of oscillation

12/3/2023

LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT



ASSESSMENT



1. An inductance of 200mH and a capacitor of 10pF are connected together in parallel to create an LC oscillator tank circuit.
Calculate the frequency of oscillation

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{200\text{mH} \times 10\text{pF}}} = 112.5 \text{ kHz}$$

LC OSCILLATORS/19ECB201- ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT



THANK YOU

12/3/2023

LC OSCILLATORS/19ECB201– ANALOG
ELECTRONIC CIRCUITS/S.RAJA/ECE/SNSCT