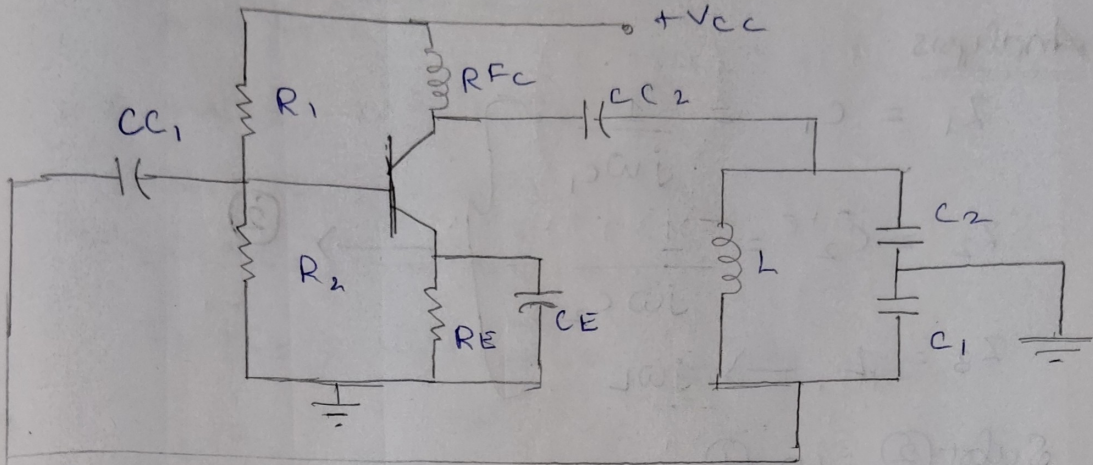


Colpitts oscillator:



The LC oscillator uses two capacitance and one inductance in the feedback network is called Colpitts oscillator.





⇒ Short coupling capacitor

⇒ Bypass capacitor are short circuited

⇒ neglect  $R_1$  &  $R_2$

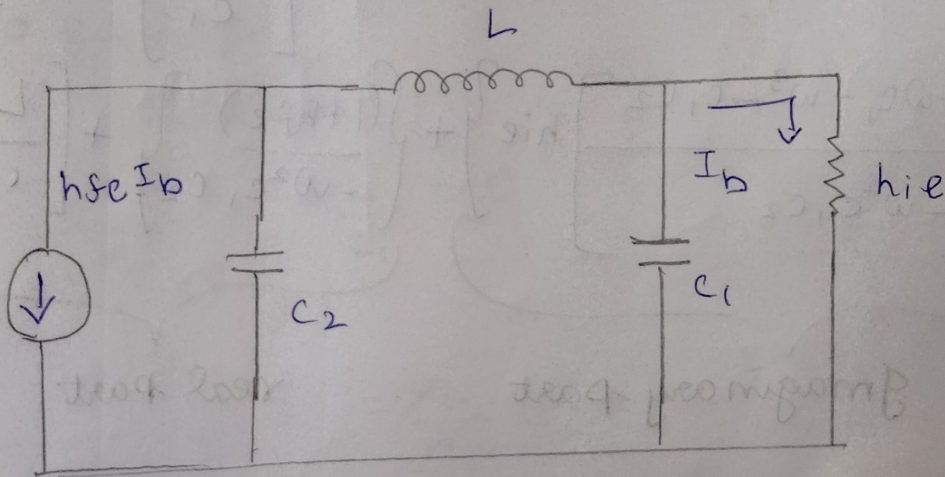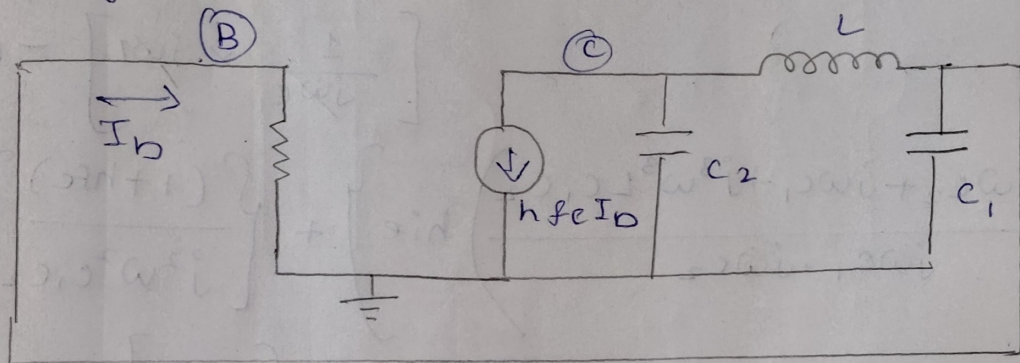

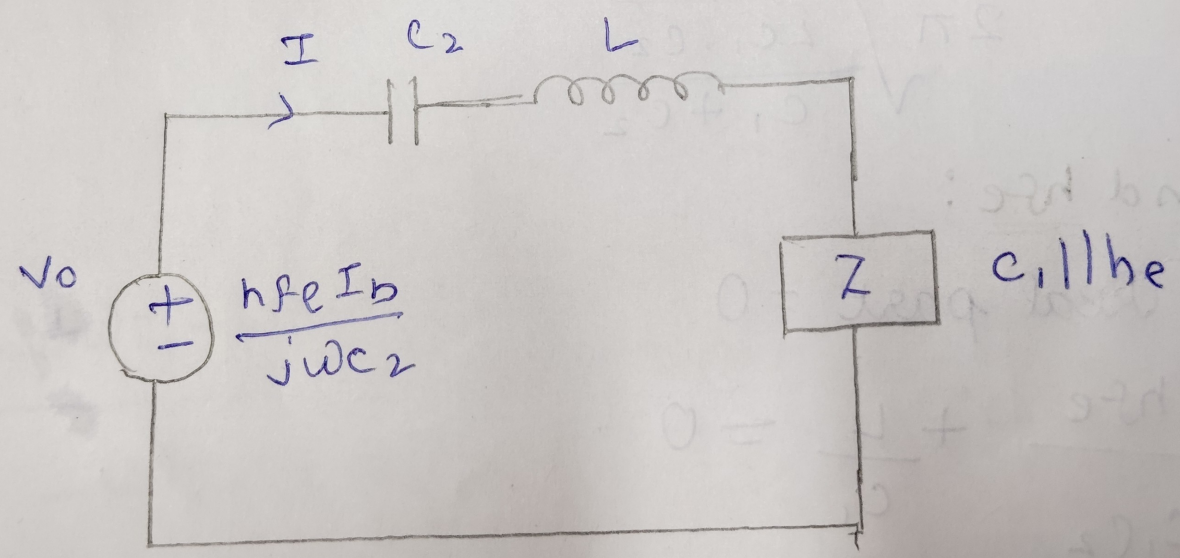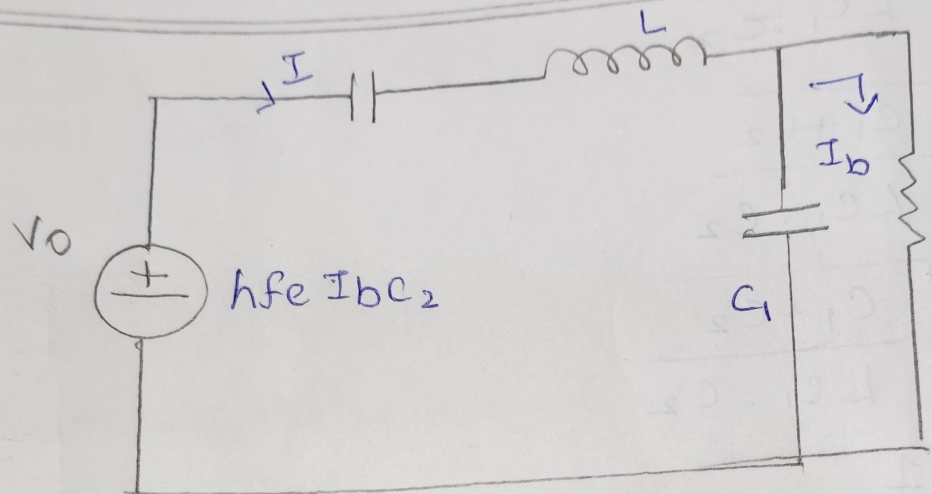(convert current source into volt source)



General form of LC oscillator is

$$(z_1 + z_2 + z_3)h_{ie} + z_1 z_2 (1 + h_{fe}) + z_1 z_3 = 0 \quad \text{--- (1)}$$

Analysis

$$z_1 = C_1 = \frac{1}{j\omega C_1}$$

$$z_2 = C_2 = \frac{1}{j\omega C_2}$$

$$z_3 = L \rightarrow j\omega L$$

--- (2)

Subst (2) in (1)

$$\left\{ \left( \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + j\omega L \right) h_{ie} \right\} + \left\{ \frac{1}{j\omega C_1} \times \frac{1}{j\omega C_2} (1 + h_{fe}) \right\}$$

$$\left\{ \frac{1}{j\omega C_1} \times j\omega L \right\} = 0$$

$$\left\{ \frac{(j\omega C_2 + j\omega C_1 + j^3 \omega^3 L C_1 C_2)}{j\omega C_1 \cdot j\omega C_2} h_{ie} \right\} + \left\{ \frac{(1 + h_{fe})}{j^2 \omega^2 C_1 C_2} \right\}$$

$$+ \left\{ \frac{L}{C_1} \right\} = 0$$

$$\left\{ j \left[ \frac{\omega C_2 + \omega C_1 - \omega^3 L C_1 C_2}{-\omega^2 C_1 C_2} \right] h_{ie} \right\} + \left\{ \frac{(1 + h_{fe})}{-\omega^2 C_1 C_2} \right\} + \left\{ \frac{L}{C_1} \right\} = 0$$

Imaginary part

real part

To find frequency:

Imaginary part = 0

$$\left( \frac{\omega c_1 + \omega c_2 - \omega^3 L c_1 c_2}{-\omega^2 c_1 c_2} \right) hfe = 0$$

$$\omega c_1 + \omega c_2 - \omega^3 L c_1 c_2 = 0$$

$$\omega c_1 + \omega c_2 = \omega^3 L c_1 c_2$$

$$\omega (c_1 + c_2) = \omega^3 L c_1 c_2$$

$$c_1 + c_2 = \frac{\omega^3 L c_1 c_2}{\omega} = \omega^2 L c_1 c_2$$

$$\omega^2 = \frac{c_1 + c_2}{L c_1 c_2}$$

$$\omega = \sqrt{\frac{c_1 + c_2}{L c_1 c_2}}$$

$$2\pi f_r = \sqrt{\frac{c_1 + c_2}{L c_1 c_2}}$$

$$f_r = \frac{1}{2\pi \sqrt{\frac{L c_1 c_2}{c_1 + c_2}}}$$

To find hfe:

Real part = 0

$$\frac{1 + hfe}{-\omega^2 c_1 c_2} + \frac{L}{c_1} = 0$$

$$\frac{1 + hfe}{\omega^2 c_1 c_2} = \frac{L}{c_1}$$

$$(1 + hfe) = \frac{L \cdot \omega^2 c_1 c_2}{c_1}$$

$$(1 + hfe) = L \cdot \omega^2 c_2$$

$$hfe = L \omega^2 c_2 - 1$$

$$h_{fe} = \frac{C_1 + C_2}{C_1} - 1$$

$$\therefore \omega^2 = \frac{C_1 + C_2}{L C_1 C_2}$$

$$h_{fe} = \left( \frac{C_1 + C_2}{C_1} \right) - 1$$

$$h_{fe} \Rightarrow \frac{C_1 + C_2 - C_1}{C_1} = \frac{C_2}{C_1}$$

$$h_{fe} = \frac{C_2}{C_1}$$

