



# SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)



COIMBATORE-35


Accredited by NBA-AICTE and Accredited by NAAC – UGC with A+ Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

UNIT 3
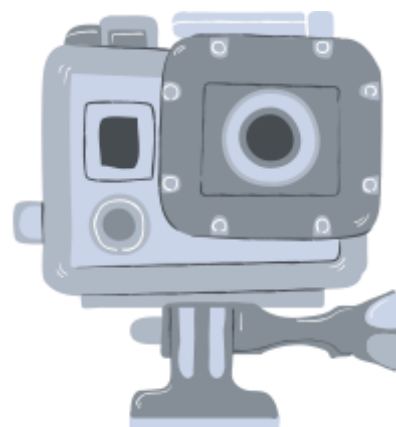
## Fault Analysis – Balanced Faults

19EET302 – Power System 1  
III year / V Semester





# Problem formulation


---

## *Fault Analysis*


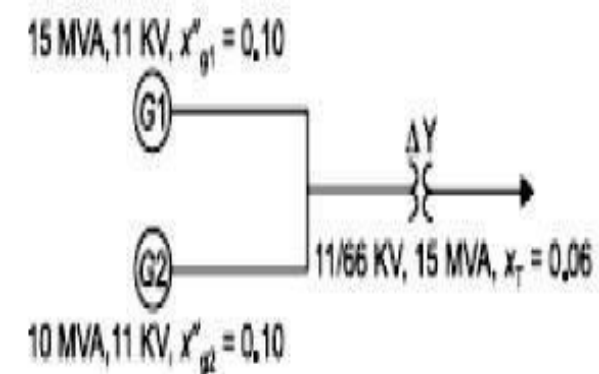
# Problem

- Two generators G1 and G2 are rated 15MVA, 11KV and 10MVA, 11KV respectively. The generators are connected to a transformer as shown in fig. Calculate the sub transient current in each generator when a three phase fault occurs on the high voltage side of the transformer.



**Solution:** Choose a base 15 MVA

$$x''_{g1} = j0.10 \text{ pu}$$

$$x''_{g2} = j0.10 \times \frac{15}{10} = j0.15 \text{ pu}$$



# Solution

$$x_T = j0.06 \text{ pu}$$

$$I_f = \frac{V_o}{j0.12} = \frac{1}{j0.12} = -j8.33 \text{ pu}$$

$$I_{g1} = \frac{j0.15}{j(0.1 + 0.15)} \times (-j8.33) = -j5.0 \text{ pu}$$

$$I_{g2} = \frac{j0.10}{j(0.1 + 0.15)} \times (-j8.33) = -j3.33 \text{ pu}$$

Base current

$$I_B = \frac{15 \times 1000}{\sqrt{3} \times 11} = 787.3 \text{ Amp.}$$

$$\therefore I_{g1} = -j5 \times 787.3 = -j3.936 \text{ KA.}$$

$$I_{g2} = -j3.33 \times 787.3 = -j2.621 \text{ KA.}$$

$$I_f = -j8.33 \times 787.3 = -j6.557 \text{ KA.}$$

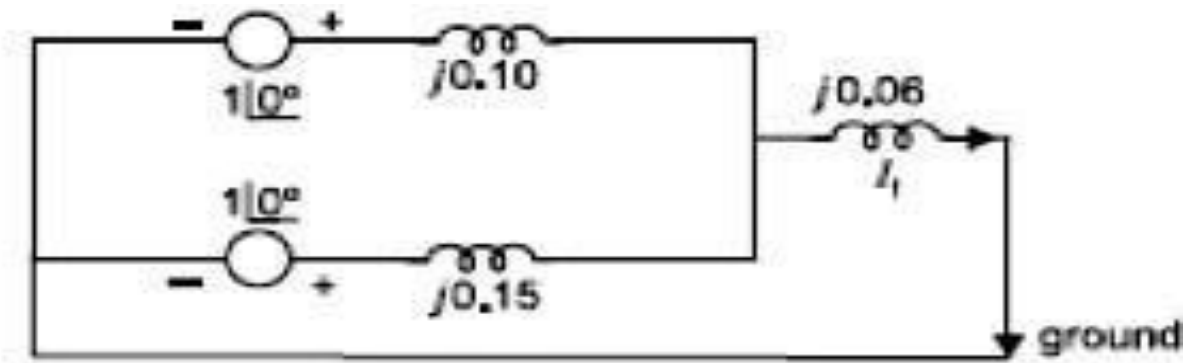


Fig. 8.7(a)

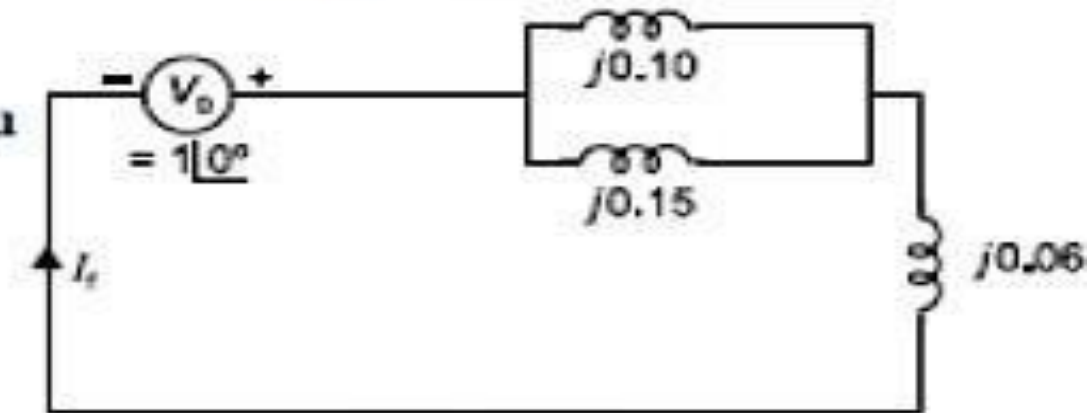


Fig. 8.7(b)


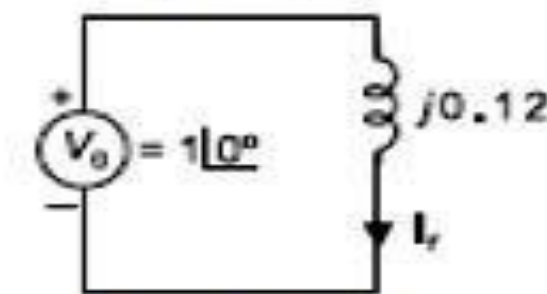


Fig. 8.7(c)

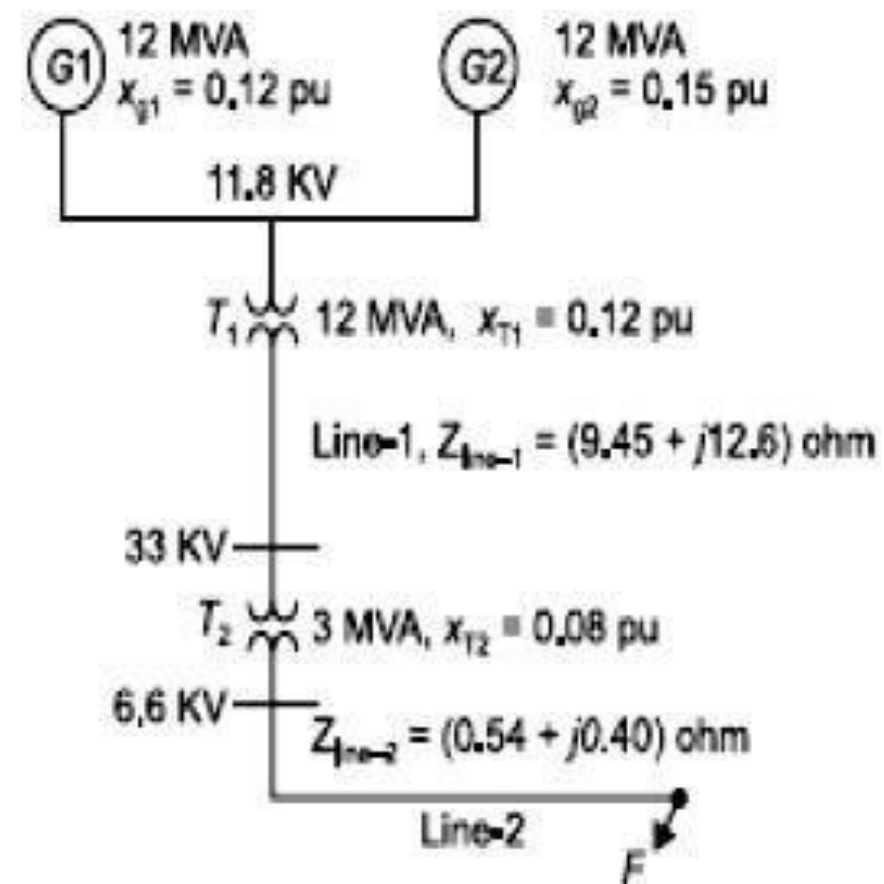

# A Problem

A radial power system network is shown in fig. a three phase balanced fault occurs at F. Determine the fault current and the line voltage at 11.8 KV bus under fault condition.





# Soln

### Solution:

Let Base MVA = 12

Base Voltage = 11.8 KV.

$$x_{g1} = j0.12 \text{ pu}, \quad x_{g2} = j0.15 \text{ pu}$$

$$x_{T1} = j0.12 \text{ pu},$$

$$x_{T2} = j0.08 \times \frac{12}{3} = j0.32 \text{ pu}$$

Base voltage for line-1 is 33 KV.

Base voltage for line-2 is 6.6 KV.

$$Z_{B, \text{line-1}} = \frac{(33)^2}{12} = 90.75 \text{ ohm.}$$

$$Z_{B, \text{line-2}} = \frac{(6.6)^2}{12} = 3.63 \text{ ohm.}$$

$$\therefore Z_{\text{line-1}} = \frac{(9.45 + j12.6)}{90.75} = (0.104 + j0.139) \text{ pu}$$

$$Z_{\text{line-2}} = \frac{(0.54 + j0.40)}{3.63} = (0.148 + j0.11) \text{ pu}$$

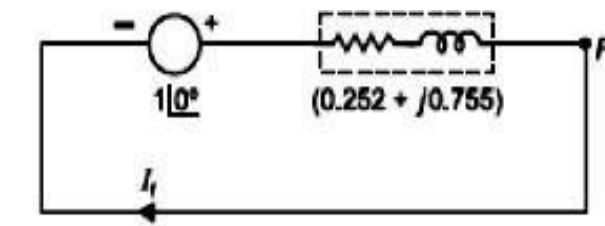
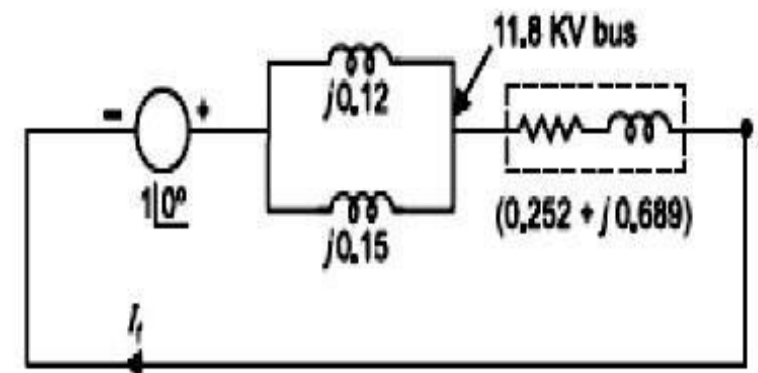
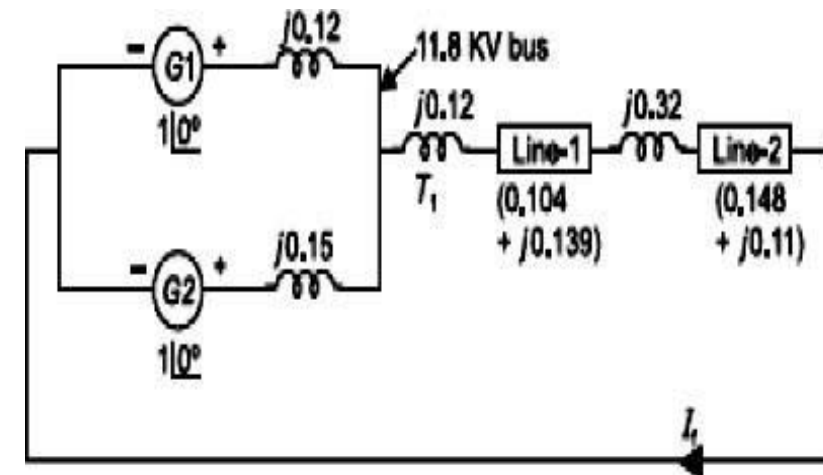


Fig. 8.12(c)

Base current

$$I_B = \frac{12 \times 1000}{\sqrt{3} \times 6.6} = 1049.7 \text{ Amp.}$$

Now

$$I_f = \frac{1 \angle 0^\circ}{(0.252 + j0.755)} = 1.256 \angle -71.5^\circ \text{ pu}$$

$\therefore$

$$I_f = 1.256 \angle -71.5^\circ \times 1049.7$$

$\therefore$

$$I_f = 1318.4 \angle -71.5^\circ \text{ Amp.}$$

Total impedance between F and 11.8 KV bus

$$= (0.252 + j0.689) \text{ pu}$$

Voltage at 11.8 KV bus

$$= 1.256 \angle -71.5^\circ \times (0.252 + j0.689)$$

$$= 0.921 \angle -16^\circ \text{ pu}$$

$$= 0.921 \angle -16^\circ \times 11.8 \text{ KV}$$

$$= 10.86 \angle -16^\circ \text{ KV. Ans.}$$



# Summary

---



## Activity



**KEEP  
LEARNING..  
Thank u**

SEE YOU IN NEXT CLASS