
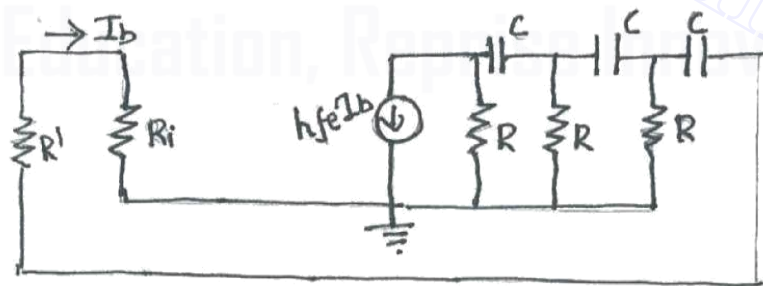


## 16 Marks Questions

- i) Explain the operation of RC phase shift Oscillator and Wein Bridge Oscillator. Derive its frequency of Oscillation.

RC Oscillators :-


- i) RC phase Shift Oscillator :-

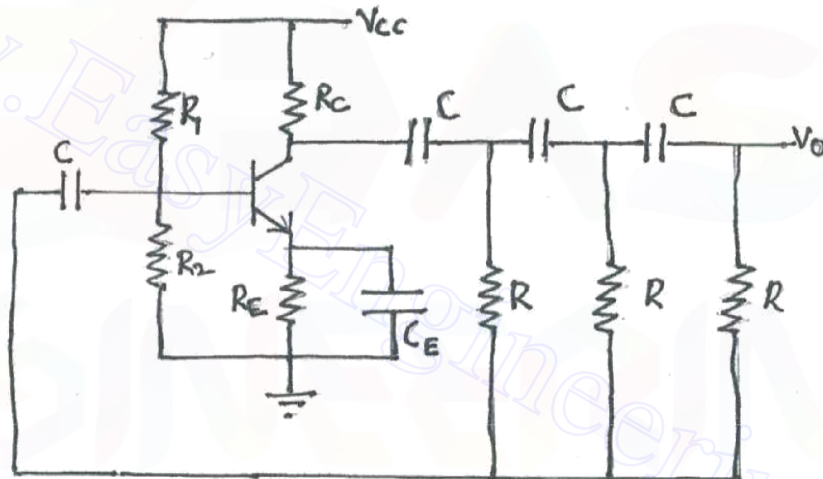

$$R_i = R_1 \parallel R_2 \parallel h_{fe}$$

→ It is a audio frequency or low frequency oscillator. It uses a common emitter amplifier whose output is given to three RC networks. The phase shift produced by the common emitter

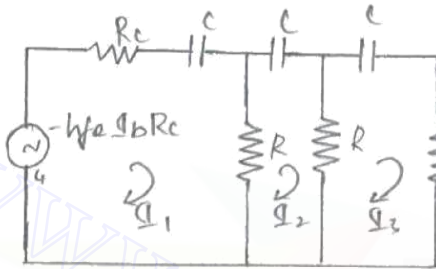emitter amplifier is  $180^\circ$ . Since an Oscillator requires a phase shift of  $360^\circ$  and the additional  $180^\circ$  phase shift is obtained using three RC networks with an individual phase shift of  $60^\circ$  each.



At loop B

$$(I_3 - I_2)R + \frac{I_3}{j\omega C} + I_3 R = 0$$

$$I_3(2R - 1/j\omega C) - I_2 R = 0 \rightarrow \textcircled{1}$$

At loop 2:  $(I_2 - I_1)R + I_2/j\omega C + (I_2 - I_3)R = 0$

$$-I_1 R + I_2(2R + 1/j\omega C) - I_3 R = 0 \rightarrow \textcircled{2}$$

At loop 1:  $(I_1 - I_2)R + I_1/j\omega C + I_1 R_c = -hfe I_b R_c$

$$I_1(R + 1/j\omega C + R_c) - I_2 R = -hfe I_b R_c \Rightarrow hfe I_b R_c - I_2 R + I_1(R + R_c + 1/j\omega C) = 0 \rightarrow$$

$$\begin{vmatrix} 2R + 1/j\omega C & -R & 0 \\ -R & 2R + 1/j\omega C & -R \\ hfe R_c & -R & R + R_c + 1/j\omega C \end{vmatrix} = (2R + 1/j\omega C) \left[ (2R + 1/j\omega C)(R + R_c + 1/j\omega C) - R^2 \right] + R \left[ -R(R + R_c + 1/j\omega C) + R hfe R_c \right]$$

$$= (2R + 1/j\omega C) \left[ 2R^2 + 2RR_c + \frac{2R}{j\omega C} + \frac{R}{j\omega C} + \frac{R_c}{j\omega C} - \frac{1}{\omega^2 C^2} - R^2 \right] + R \left[ -R^2 - RR_c - \frac{R}{j\omega C} + R hfe R_c \right]$$

$$= (2R + 1/j\omega C) \left[ 2R^2 + \frac{3R}{j\omega C} + 2RR_c - \frac{1}{\omega^2 C^2} - R^2 + \frac{R_c}{j\omega C} \right] + \left[ -R^3 - RR_c - \frac{R^2}{j\omega C} + R^2 hfe R_c \right]$$

(55)

$$\begin{aligned}
&= 4R^3 + \frac{6R^2}{j\omega c} + 4R^2 R_c - \frac{2R}{\omega^2 c^2} - 2R^3 + \frac{2RR_c}{j\omega c} - R^3 - R^2 R_c - \frac{R^2}{j\omega c} + R^2 h_{fe} R_c \\
&\quad + \frac{2R^2}{j\omega c} - \frac{3R}{\omega^2 c^2} + \frac{2RR_c}{j\omega c} - \frac{1}{j\omega^3 c^3} - \frac{R^2}{j\omega c} - \frac{R_c}{\omega^2 c^2} \\
&= R^3 + 3R^2 R_c + R^2 h_{fe} R_c - \frac{1}{j\omega^3 c^3} - \frac{5R}{\omega^2 c^2} + \frac{6R^2}{j\omega c} + \frac{4RR_c}{j\omega c} - \frac{R_c}{\omega^2 c^2} \\
&= \left[ R^3 + 3R^2 R_c + R^2 h_{fe} R_c - \frac{5R}{\omega^2 c^2} - \frac{R_c}{\omega^2 c^2} \right] + \left[ \frac{6R^2}{j\omega c} + \frac{4RR_c}{j\omega c} - \frac{1}{j\omega^3 c^3} \right]
\end{aligned}$$

Equating imaginary part to zero  $\rightarrow \textcircled{1}$

i.e.  $\frac{6R^2}{j\omega c} + \frac{4RR_c}{j\omega c} - \frac{1}{j\omega^3 c^3} = 0$ ,  $\frac{6R^2 + 4RR_c}{j\omega c} - \frac{1}{\omega^3 c^3} = 0$

$$\begin{aligned}
\left[ \omega^2 c^2 (6R^2 + 4RR_c) - 1 \right] &= 0 \Rightarrow \omega^2 c^2 (6R^2 + 4RR_c) = 1 \\
\Rightarrow \omega^2 c^2 &= \frac{1}{6R^2 + 4RR_c}
\end{aligned}$$

$$\omega^2 = \frac{1}{c^2 (6R^2 + 4RR_c)} \Rightarrow \frac{1}{c^2 R^2 \left[ 6 + \frac{4R_c}{R} \right]} \rightarrow$$

$$\omega = \frac{1}{RC \sqrt{6 + 4K}} \quad K = R_c/R$$

$$f = \frac{1}{2\pi RC \sqrt{6 + 4K}} \rightarrow \textcircled{2}$$

If  $R_c/R$  is very small

$$f = \frac{1}{2\pi RC \sqrt{6}}$$

(56)

Equating real part to zero

$$R^3 + 3R^2 R_c + R^2 R_c h_{fe} - \frac{5R}{\omega^2 C^2} - \frac{R_c}{\omega^2 C^2} = 0$$

$$R^3 + 3R^2 R_c + R^2 R_c h_{fe} - 5R(6R^2 + 4RR_c) - R_c(6R^2 + 4RR_c) = 0 \text{ from eqn (C)}$$

$$R^3 + 3R^2 R_c + R^2 R_c h_{fe} - 30R^3 - 20R^2 R_c - 6R^2 R_c - 4RR_c^2 = 0$$

$$-29R^3 - 23R^2 R_c + R^2 R_c h_{fe} + 4RR_c^2 = 0$$

$$R^2 R_c h_{fe} = 29R^3 + 23R^2 R_c + 4RR_c^2$$

$$h_{fe} = \frac{29R}{R_c} + 23 + \frac{4R_c}{R} \rightarrow (4)$$

$$\text{Let } k = R_c/R \Rightarrow h_{fe} = \frac{29}{k} + 23 + 4k$$

$$\text{diff w.r.t to 'k' } \cdot \frac{dh_{fe}}{dk} = -\frac{29}{k^2} + 4$$

$$\frac{dh_{fe}}{dk} = 0$$

$$\frac{29}{k^2} = 4 \Rightarrow k = 2.7 \rightarrow (5)$$

$$\text{Substituting } k \text{ value in (4) } h_{fe} = \frac{29}{2.7} + 23 + 4 \times 2.7$$

$$= 44.54$$

$h_{fe} \geq 44.54$  for sustained oscillation

For Barkhausen Criterion  $A\beta = 1$ ,  $\beta = -1/29$

(5)