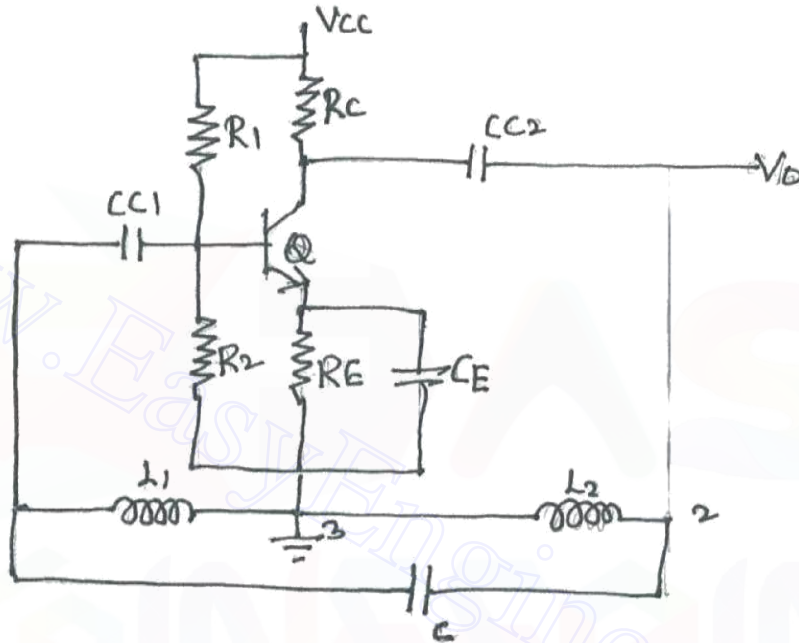


2) Explain the Hartley and Colpits Oscillators and derive its frequency of Oscillation

LC Oscillators:-

i) Hartley Oscillators:-



→ It is an example of LC Oscillator. Z_1, Z_2 are inductor and Z_3 is a capacitor. Resistors R_1, R_2 & R_E provide the necessary dc bias to the transistor. The feedback network consisting of L_1, L_2 and C determines the frequency of Oscillation.

→ C_E is the bypass capacitor, C_{C1} and C_{C2} are coupling capacitors.

(4)

Operation : \rightarrow When the supply voltage $+V_{CC}$ is switched on, a transient current is produced in the tank circuit & consequent damped harmonic oscillation are set up in the circuit

\rightarrow The oscillatory circuit in the tank circuit produces a voltage across L_1 and L_2 . as terminal 3 is earthed at zero potential \rightarrow If terminal 1 is at +ive potential with respect to 3 at any instant terminal 2 will be at a negative potential with respect to 3 at the same instant. Thus the phase difference between terminals 1 & 2 is always 180° .

\rightarrow In the CE mode, the transistor provides a phase shift of 180° . Thus the total phase shift of 360° is achieved that satisfies Barkhausen criterion. Thus the frequency of oscillation is determined by the tank consisting of L_1, C_2 & C . The frequency

of Oscillation is given as $f = \frac{1}{2\pi\sqrt{L_{eq}}}$

$$\text{Where } L_{eq} = L_1 + L_2 + 2M$$

$M \rightarrow$ mutual inductance L_1 & L_2

The condition for sustained Oscillation is $h_{fe} \geq \frac{L_1 + M}{L_2 + M}$

Analysis :-

In this oscillator Z_1 & Z_2 are inductive reactances & Z_3 is capacitive reactance

$$Z_1 = j\omega L_1 + j\omega M, \quad Z_2 = j\omega L_2 + j\omega M$$

$$Z_3 = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

Substituting for Z_1 & Z_2 and Z_3 in general eqn

$$(Z_1 + Z_2 + Z_3)h_{fe} + Z_1 Z_3 + Z_1 Z_2 (1 + h_{fe}) = 0 \rightarrow (1)$$

$$\left[(j\omega L_1 + j\omega L_2 + j\omega M + j\omega M - \frac{j}{\omega C}) \right] h_{fe} + \left[(j\omega L_1 + j\omega M) \times -\frac{j}{\omega C} \right]$$

$$+ (j\omega L_1 + j\omega M)(j\omega L_2 + j\omega M)(1 + h_{fe}) = 0 \rightarrow (2)$$

$$\left[j\omega [L_1 + L_2 + 2M - \frac{1}{\omega^2 C}] h_{fe} + \left[j^2 \omega (L_1 + M) \left(\frac{1}{\omega C} \right) \right] \right]$$

$$+ \left[j^2 \omega^2 (L_1 + M)(L_2 + M)(1 + h_{fe}) \right] = 0$$

(66)

$$j\omega hie \left[(L_1 + L_2 + 2M) - \frac{1}{\omega^2 c} \right] + j^2 \omega \left[(L_1 + M) \left(-\frac{1}{\omega c} \right) - \omega^2 (1 + hie) \right] \\ (L_1 L_2 + L_1 M + L_2 M + M^2) = 0$$

Multiplying and dividing by ω throughout

$$j\omega hie \left[(L_1 + L_2 + 2M) - \frac{1}{\omega^2 c} \right] - \omega^2 (1 + hie) (L_1 + M) (L_2 + M) \\ - \frac{j^2 \omega^2 L_1 - j^2 \omega^2 M}{c \omega^2} = 0$$

$$j\omega hie \left[(L_1 + L_2 + 2M) - \frac{1}{\omega^2 c} \right] - \omega^2 (L_1 + M) \left[(L_2 + M) (1 + hie) - \frac{1}{\omega^2 c} \right] = 0 \\ \rightarrow \textcircled{3}$$

Equating imaginary part eqn $\textcircled{3}$ to zero

$$L_1 + L_2 + 2M - \frac{1}{\omega^2 c} = 0 \rightarrow \textcircled{4} \quad [\because \omega \neq 0 \text{ \& } hie \neq 0]$$

$$\frac{1}{\omega^2 c} = L_1 + L_2 + 2M \quad \omega = \frac{1}{\sqrt{(L_1 + L_2 + 2M) c}} \\ \rightarrow \textcircled{5}$$

$$f = \frac{1}{2\pi \sqrt{(L_1 + L_2 + 2M) c}} \rightarrow \textcircled{6}$$

$$f = \frac{1}{2\pi \sqrt{L_{eq} c}} \rightarrow \textcircled{7} \quad \text{Where } L_{eq} = L_1 + L_2 + 2M$$

The condition for sustained Oscillation is obtained by equating the real part of eqn(3) to zero.

$$\omega^2(L_1+M)\left[(L_2+M)(1+h_{fe})-\frac{1}{\omega^2 C}\right]=0$$

$\therefore \omega^2 \neq 0, L_1+M \neq 0$, we get

$$(L_2+M)(1+h_{fe})-\frac{1}{\omega^2 C}=0, \text{ substituting for } \omega^2 \text{ from eqn (6)}$$


$$(L_2+M)(1+h_{fe})-\frac{(L_1+L_2+2M)C}{C}=0 \Rightarrow L_2+L_2 h_{fe}+M+M h_{fe}-L_1-L_2-2M=0$$

$$h_{fe}(L_2+M)-M-L_1=0 \quad \therefore h_{fe}(L_2+M)=L_1+M$$

$$h_{fe} = \frac{L_1+M}{L_2+M}$$

It is the condition for sustained Oscillation.

Colpitts Oscillator:-

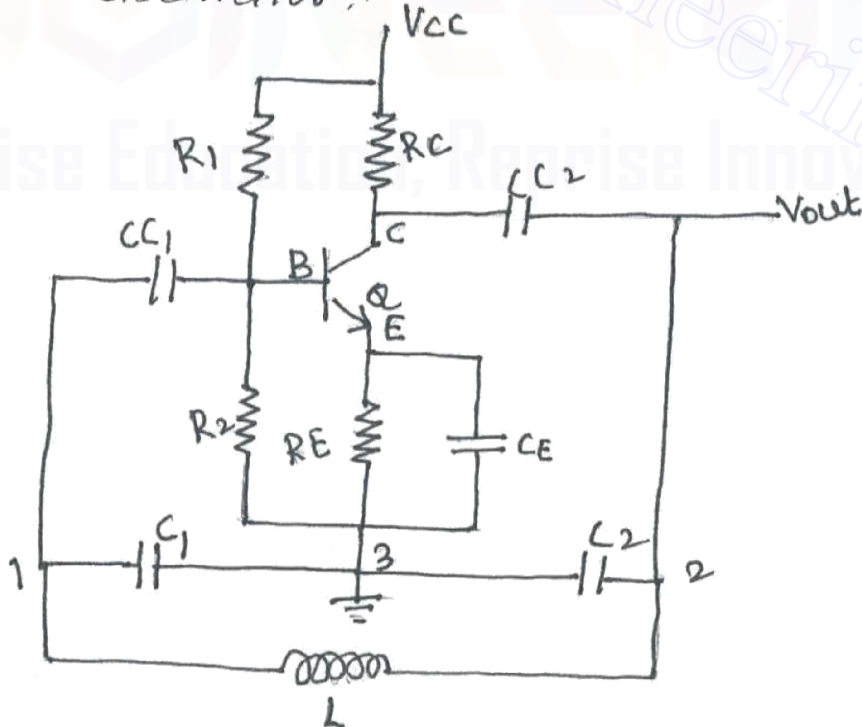

(6B)