

$$\omega^2(L_1 + M) \left[ (L_2 + M)(1 + h_{fe}) - \frac{1}{\omega^2 C} \right] = 0$$

$\therefore \omega^2 \neq 0, L_1 + M \neq 0$ , we get

$$(L_2 + M)(1 + h_{fe}) - \frac{1}{\omega^2 C} = 0, \text{ substituting for } \omega^2 \text{ from eqn (6)}$$


$$(L_2 + M)(1 + h_{fe}) - \frac{(L_1 + L_2 + 2M)C}{C} = 0 \Rightarrow L_2 + L_2 h_{fe} + M + M h_{fe} - L_1 - L_2 - 2M = 0$$

$$h_{fe}(L_2 + M) - M - L_1 = 0 \quad \therefore h_{fe}(L_2 + M) = L_1 + M$$

$$h_{fe} = \frac{L_1 + M}{L_2 + M}$$

It is the condition for sustained Oscillation.

Colpitts Oscillator:-

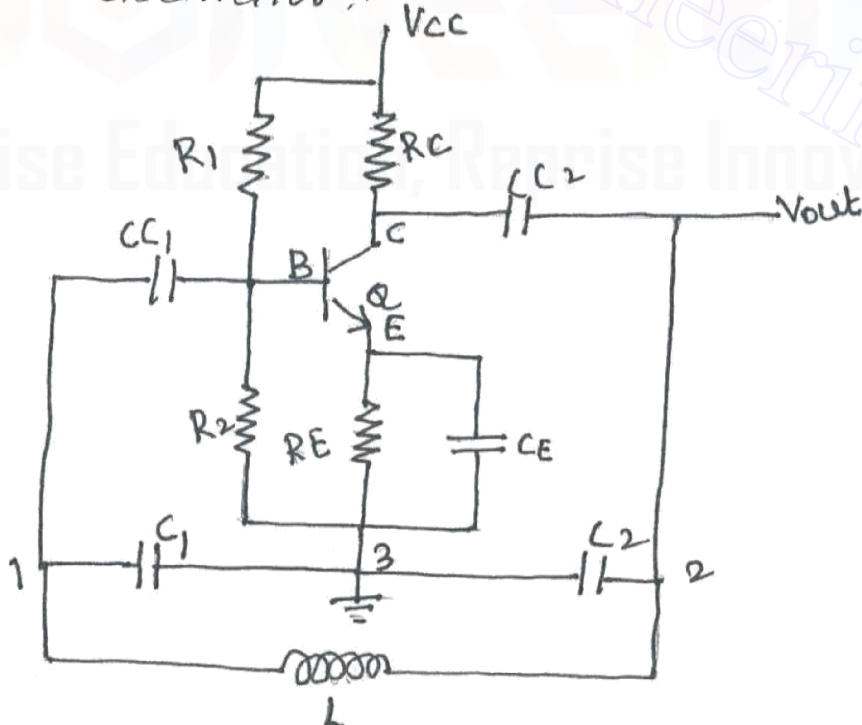

(6B)

→ In Colpits  $Z_1$  &  $Z_2$  are capacitors and  $Z_3$  is an inductor. The resistors  $R_1, R_2$  and  $R_E$  provides the necessary dc bias to the transistors. The bypass capacitor is  $C_E$ . The coupling capacitors are  $C_{C1}$  &  $C_{C2}$ . The feedback network consisting of  $C_1, C_2$  &  $L$  determines the frequency of oscillator. Operation is similar to the Hartley oscillator.

$$f = \frac{1}{2\pi\sqrt{L C_{eq}}} \quad \text{Where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Application :-

- 1) It is used for commercial signal generators for freq 1M to 800 MHz.
- 2) It is used as local oscillator in super heterodyne radio receiver.

Analysis :-

$$Z_1 = \frac{1}{j\omega C_1} = -\frac{j}{\omega C_1}, \quad Z_2 = \frac{1}{j\omega C_2} = -\frac{j}{\omega C_2}$$

$$Z_3 = j\omega L$$

General form :  $(Z_1 + Z_2 + Z_3) \text{net} + Z_1 Z_2 (H/A) + Z_1 Z_3 = 0$   
Substituting  $Z_1, Z_2$  &  $Z_3$  in above eqn

$$hie \left[ \frac{-j}{\omega c_1} - \frac{j}{\omega c_2} + j\omega L \right] + \left( \frac{-j}{\omega c_1} \right) \left( \frac{j}{\omega c_2} \right) (1+h_{fe}) + \left( \frac{-j}{\omega c_1} \right) (j\omega L) = 0$$

$$hie j \left[ \omega L - \frac{1}{\omega c_1} - \frac{1}{\omega c_2} \right] - \frac{(1+h_{fe})}{\omega^2 c_1 c_2} + \frac{\omega L}{\omega c_1} = 0$$

$$jhie \left[ \omega L - \frac{1}{\omega c_1} - \frac{1}{\omega c_2} \right] + \left[ \frac{L}{c_1} - \frac{L(1+h_{fe})}{\omega^2 c_1 c_2} \right] = 0 \rightarrow (2)$$

Equating the imaginary part of eqn to zero

$$\omega L - \frac{1}{\omega c_1} - \frac{1}{\omega c_2} = 0 \rightarrow (3)$$

$$\omega L = \frac{1}{\omega c_1} + \frac{1}{\omega c_2}, \omega L = \frac{1}{\omega} \left[ \frac{1}{c_1} + \frac{1}{c_2} \right]$$

$$\omega^2 = \frac{1}{L} \left[ \frac{c_1 + c_2}{c_1 c_2} \right] \rightarrow (4)$$

$$\omega = \sqrt{\frac{c_1 + c_2}{L c_1 c_2}} \rightarrow (5)$$

$$f = \frac{1}{2\pi} \sqrt{\frac{c_1 + c_2}{L c_1 c_2}}$$

$$f = \frac{1}{2\pi \sqrt{L c_{eq}}} \rightarrow (6)$$

$$\text{Where } c_{eq} = \frac{c_1 c_2}{c_1 + c_2} \rightarrow (7)$$

The condition for sustained oscillation is

(70)

Obtained by equating the real part of eqn(2) to zero

$$\frac{L}{C_1} - \frac{(1+h\mu e)}{\omega^2 C_1 C_2} = 0 \rightarrow \textcircled{8}$$

$$\frac{L}{C_1} = \frac{(1+h\mu e)}{\omega^2 C_1 C_2}$$

$$L = \frac{C_1 (1+h\mu e)}{\omega^2 C_2}$$

Substituting for  $\omega^2$  from eqn (4)

$$L = \frac{(1+h\mu e) L C_1 C_2}{C_2 (C_1 + C_2)}$$

$$L = \frac{(1+h\mu e) L C_1}{C_1 + C_2}$$

$$= C_1 C_2 = (1+h\mu e) C_1$$

$$C_1 \left[ 1 + \frac{C_2}{C_1} \right] = (1+h\mu e) C_1$$

$$h\mu e = \frac{C_2}{C_1} \rightarrow \textcircled{9}$$

This is the condition for sustained oscillation.

(7)