



SNS COLLEGE OF TECHNOLOGY
An Autonomous Institution
Coimbatore-35



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

19ECB201-ANALOG ELECTRONIC CIRCUITS

II YEAR/ III SEMESTER

UNIT 5 – IC MOSFET AMPLIFIERS

TOPIC – IC Amplifiers: IC biasing



IC Biasing

- * In Integrated circuit designs biasing circuits use constant-current sources.
- * Here, the constant d.c. current called reference current is generated at one location & is then replicated at various other locations for biasing the various stages of amplifiers present in the circuit.
- * This process is known as current steering. X 2 MARK



Advantages of current steering process x. 2 Marks

- * The external components such as precision resistors required to generate a predictable & stable reference current, need not be repeated for every amplifier stage.
- * The bias currents of the various stages track each other when there is any change due to power-supply voltage (or) temperature.



THANK YOU