



# **SNS COLLEGE OF TECHNOLOGY**

## **An Autonomous Institution**

### **Coimbatore-35**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB201-ANALOG ELECTRONIC CIRCUITS**

II YEAR/ III SEMESTER

### **UNIT 5 – IC MOSFET AMPLIFIERS**

TOPIC – Amplifier with active loads: Enhancement load



## Amplifiers with Active Load

\* When MOSFET itself is used as a load device, it's referred to as active load.

\* There are 3 types of load devices

1. n-channel enhancement mode device
2. n-channel depletion-mode device
3. p-channel enhancement mode device

\* 2 Mark



# 1. NMOS Amplifier with Enhancement Load

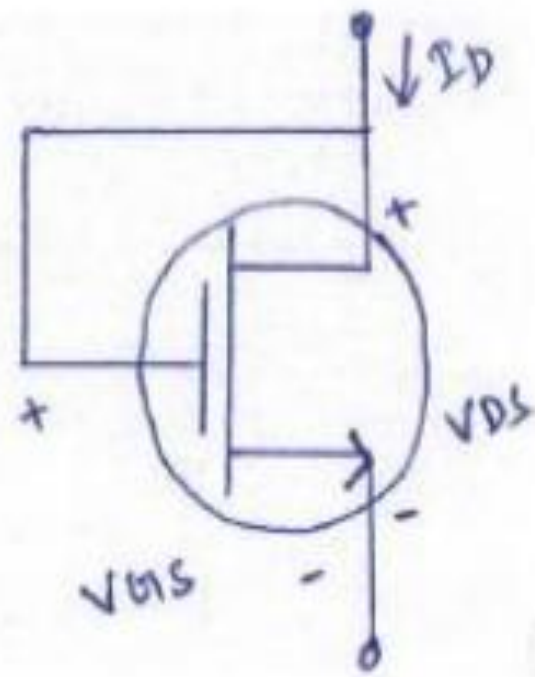


Fig: N-channel enhancement mode MOSFET with gate & drain shorted

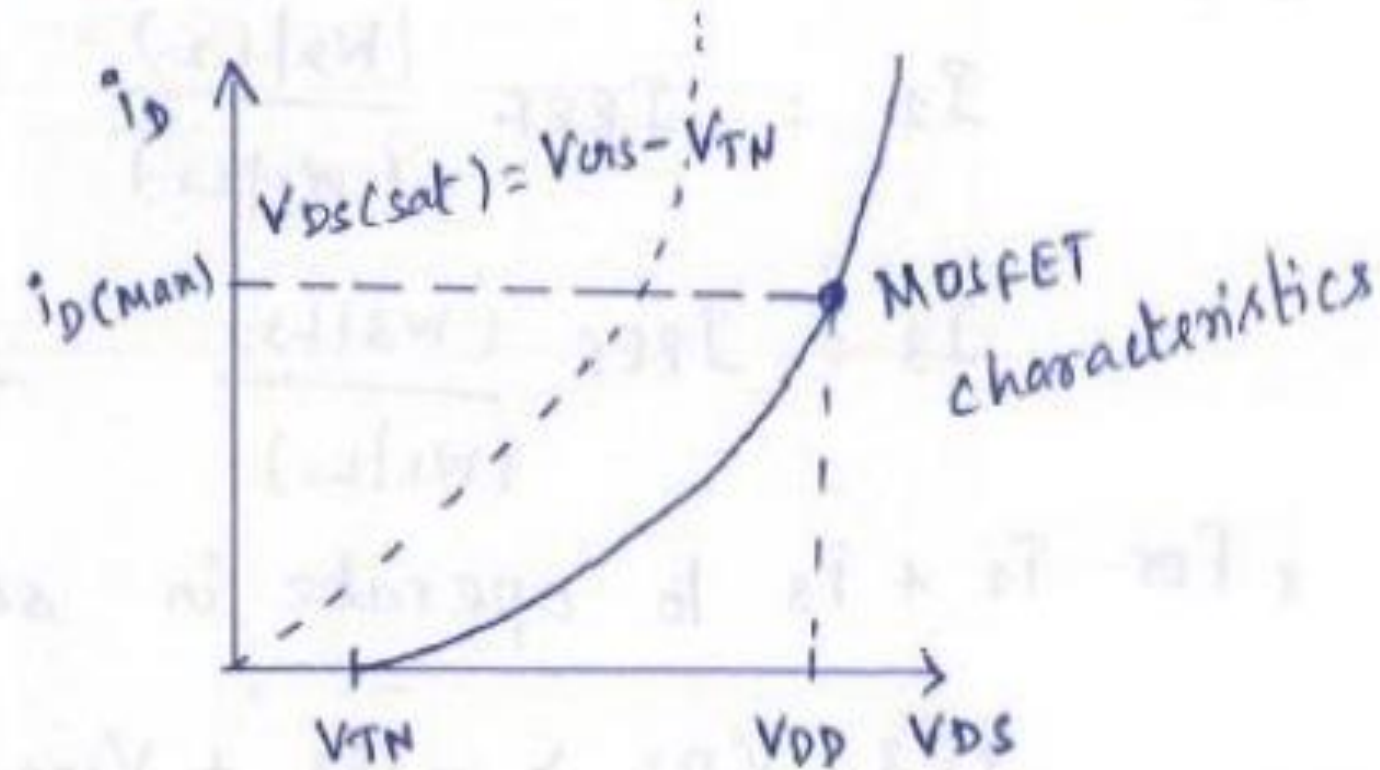


Fig: Current - voltage characteristics for n-channel enhancement load device



\* In this, the MOSFET acts as a non-linear resistor & is called an enhancement load device.

\* Since MOSFET is in enhancement mode  $V_T > 0$ .

\* For this circuit  $V_{DS(sat)} = V_{GS} - V_T$  which means that the MOSFET is always in the saturation region.

\* The I-V characteristics is a plot of equation

$$i_D = k_n (V_{GS} - V_T)^2$$

\* The enhancement load circuit alone can't be used as an amplifier, however, if it's connected in a circuit with another MOSFET, this circuit can be used as an amplifier (or) as an inverter in a digital circuit.

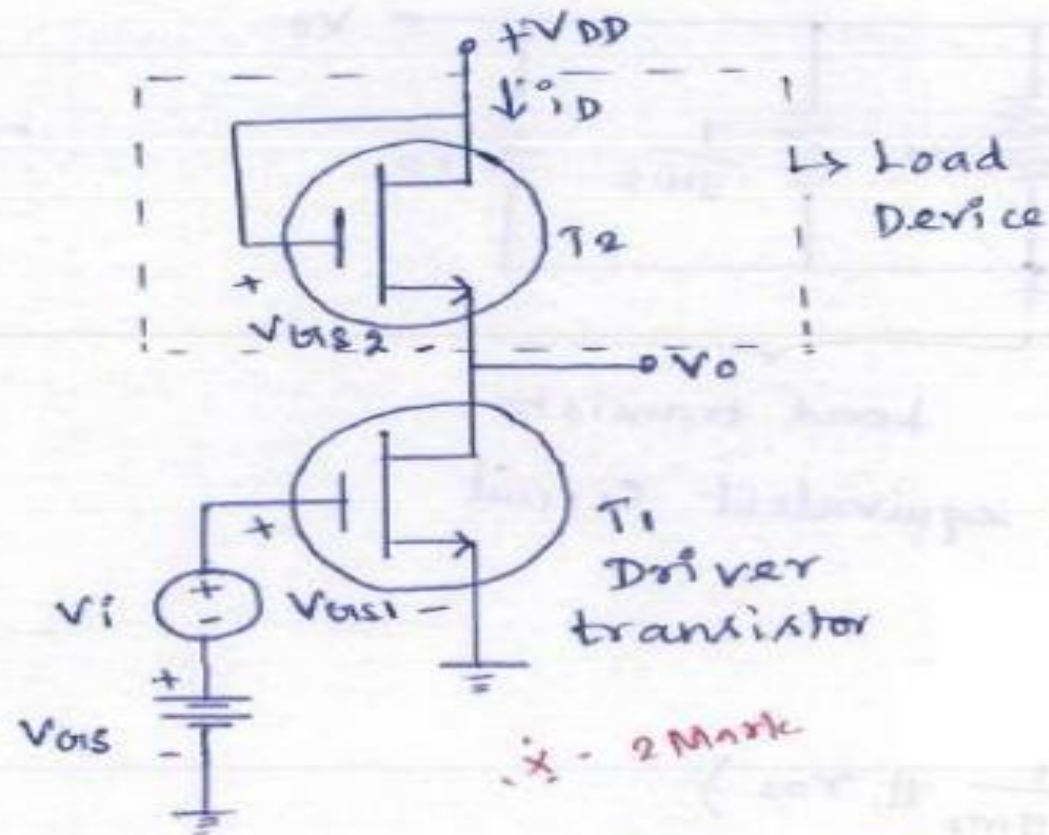


Fig: NMOS amplifier with enhancement load device


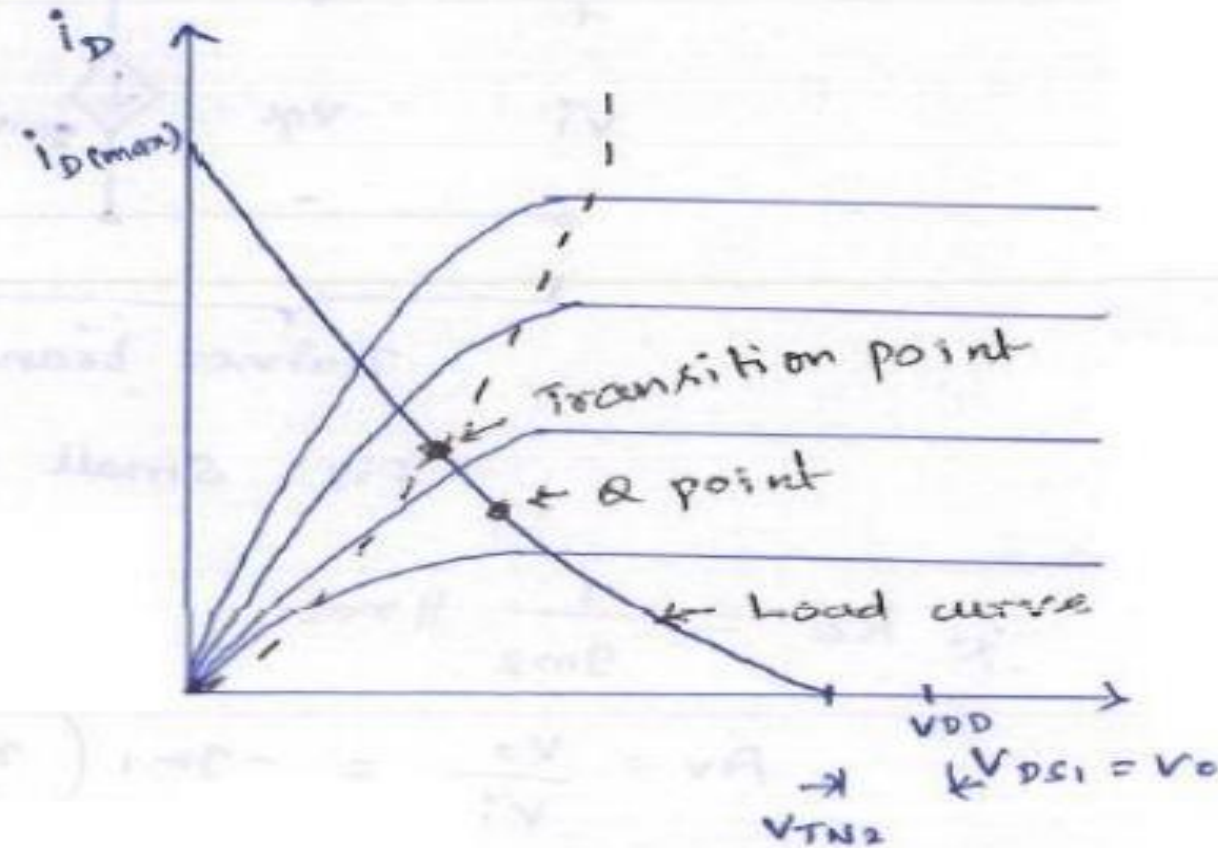


Fig: V-I characteristics

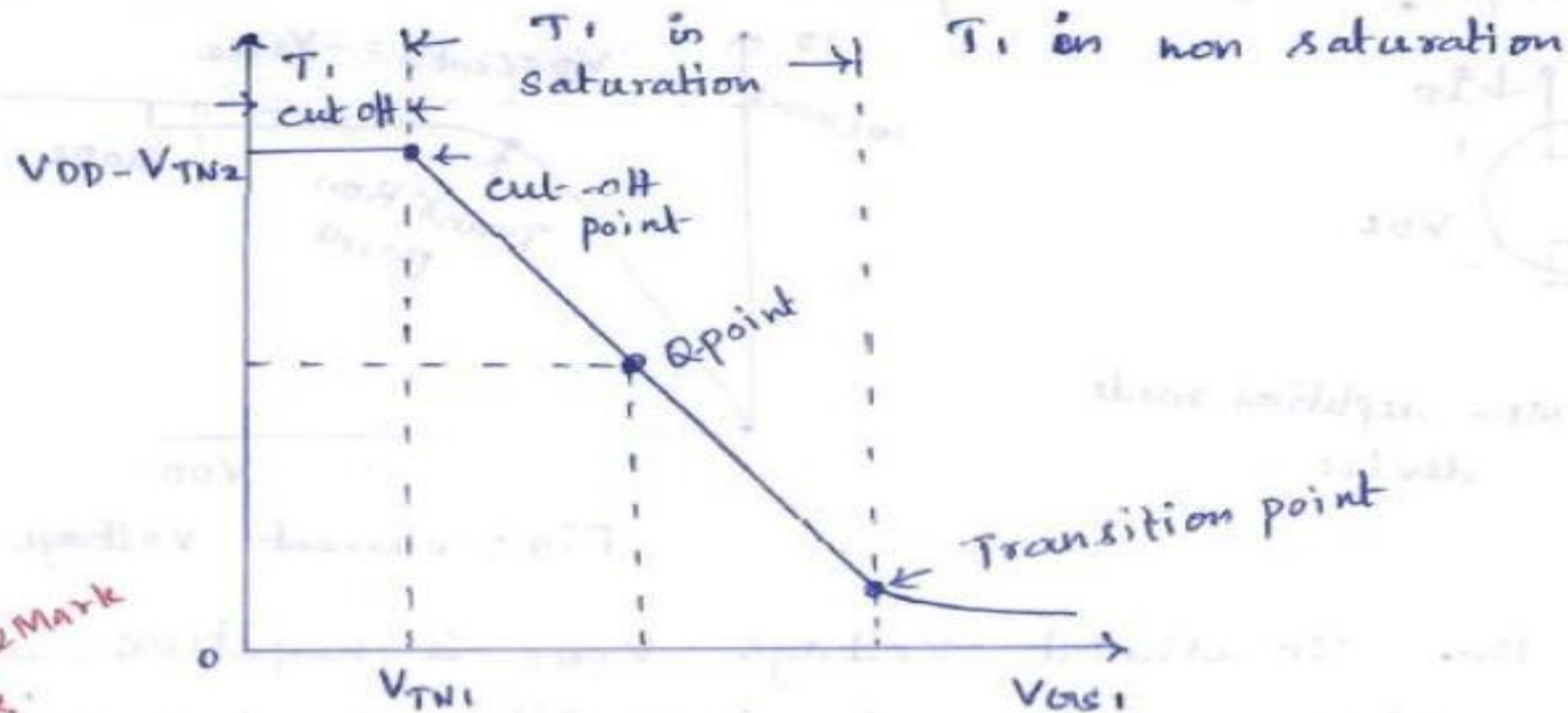- \* Here the MOSFET  $T_2$  is used as a load & MOSFET  $T_1$  is used as a driver transistor.
- \* The load device  $T_2$  is always biased in the saturation region.
- \* The V-I characteristics of the load device is non-linear, the load curve is also non-linear.



\* At  $V_{DD} - V_{TN2}$ , the load curve intersects the voltage axis & the current in the enhancement load goes to zero.



2 Mark

Fig: Voltage Transfer characteristics

\* In the characteristics fig: The Q-point should be in the Saturation region to use circuit as an amplifier.

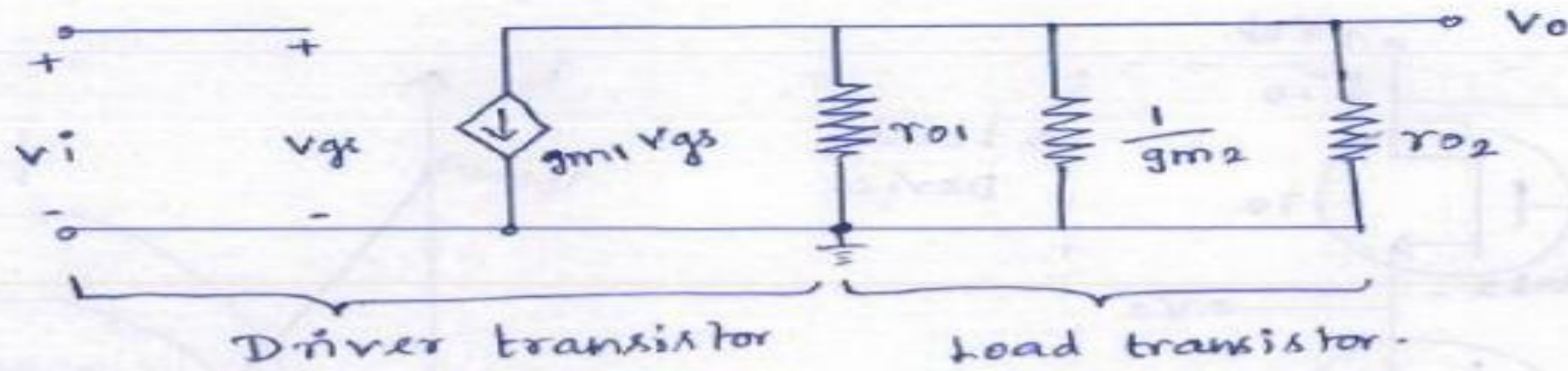


Fig: Small signal equivalent circuit

\*  $R_o = \frac{1}{g_{m2}} \parallel r_{o2}$

$$A_v = \frac{V_o}{V_i} = -g_{m1} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)$$

Since  $\frac{1}{g_{m2}} \ll r_{o2}$  &  $\frac{1}{g_{m1}} \ll r_{o1}$ , the  $A_v$  can be approximated

as

\*  $A_v = \frac{-g_{m1}}{g_{m2}} = -\sqrt{\frac{k_{n1}}{k_{n2}}} = -\sqrt{\frac{(W_1/L_1)}{(W_2/L_2)}}$  => \* This is 2 marks

2 Mark

related to the size of the transistor.

\* To obtain larger voltage gain we can use depletion-mode MOSFET.



**THANK YOU**