



# **SNS COLLEGE OF TECHNOLOGY**

## **An Autonomous Institution**

### **Coimbatore-35**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A+' Grade  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **19ECB201-ANALOG ELECTRONIC CIRCUITS**

II YEAR/ III SEMESTER

### **UNIT 5 – IC MOSFET AMPLIFIERS**

TOPIC – Amplifier with active loads: Depletion load



## NMOS Amplifier with Depletion Load

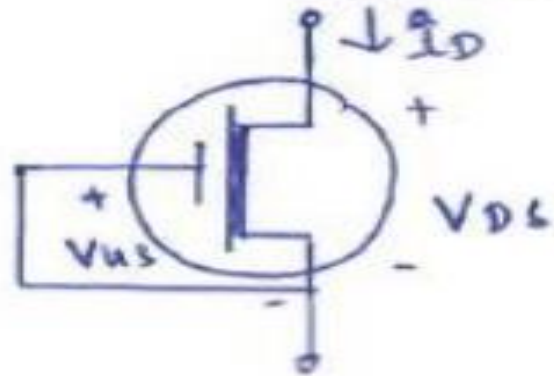


Fig: NMOS depletion mode device


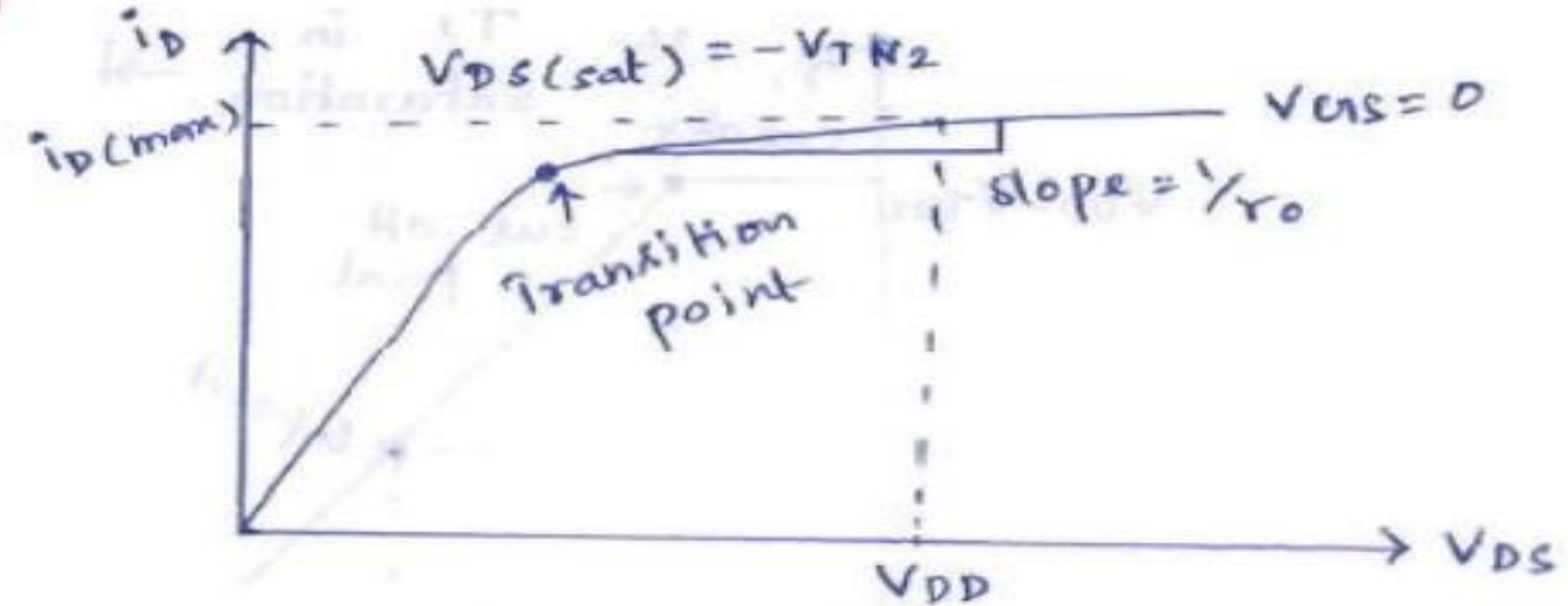


Fig: current-voltage characteristics

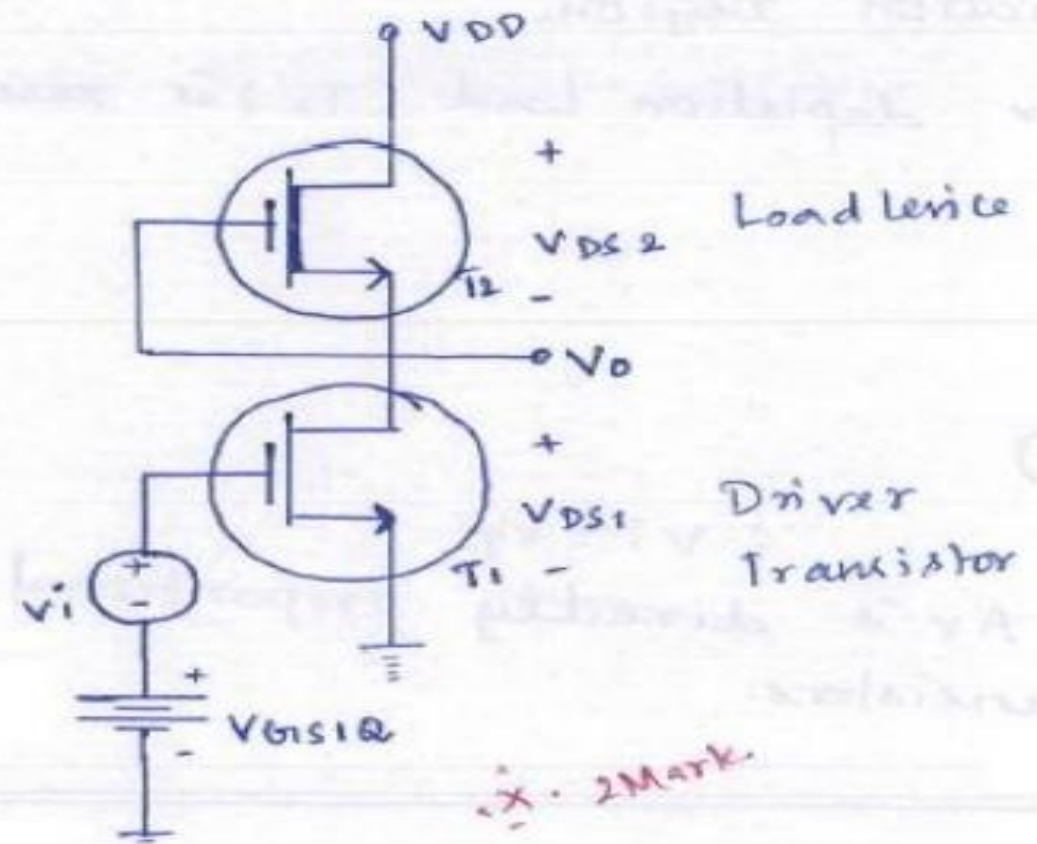- \* Here, the Threshold voltage  $V_{TN2}$  is negative, which means that the value of  $V_{DS}$  at transition point is positive.
- \* Non-zero slope in the saturation region indicates that a finite resistance  $r_o$  exists in this region.



\* X - 2 Mark

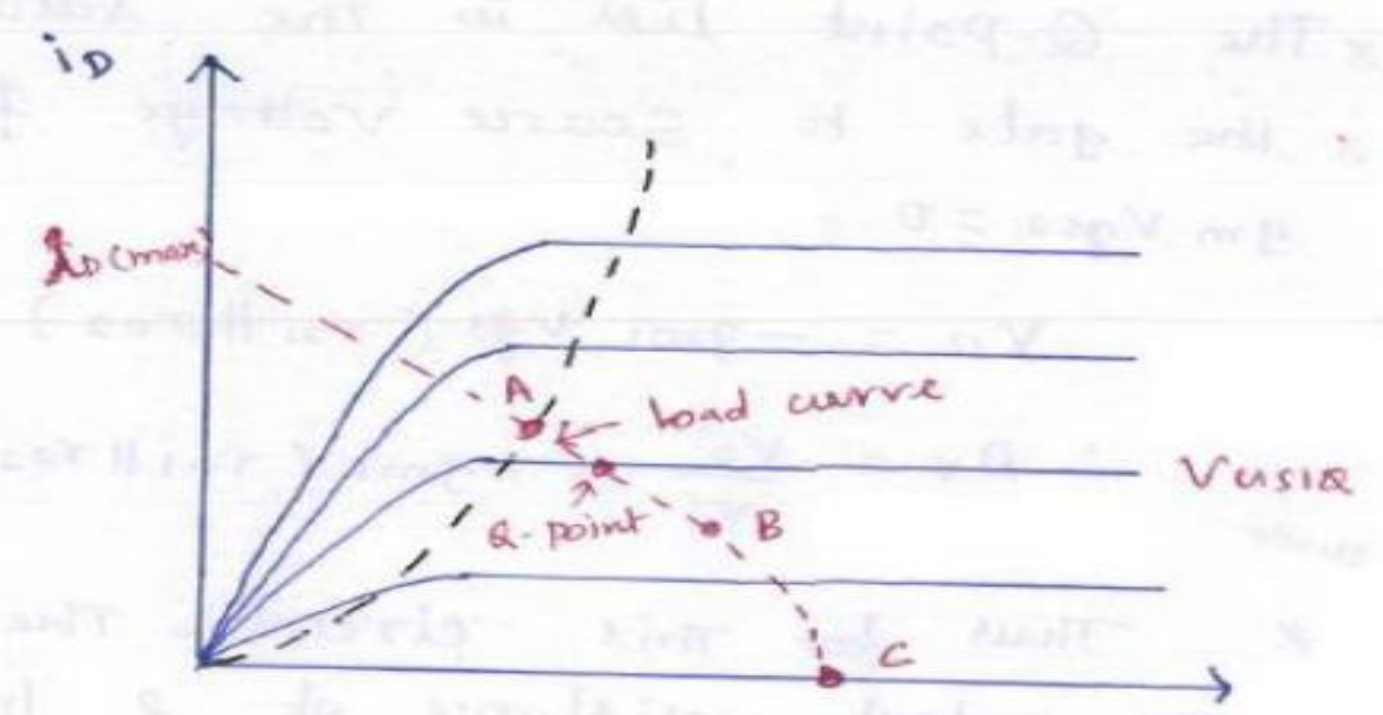


Fig: Driver transistor characteristics

Fig: NMOS amplifier with depletion load device

A - Transition point for  $T_1$   
B - Transition point for  $T_2$

- \* Here,  $T_1$  is used as a driver &  $T_2$  is used as a load.
- \* The I-V characteristics of the load device is non-linear, the load curve is also non-linear.



- \* points A + B are transition points for  $T_1$  +  $T_2$ .
- \* Q-point is approximately midway between 2 transition points.
- \* For amplifier operation, both MOSFET should be biased in Saturation region.

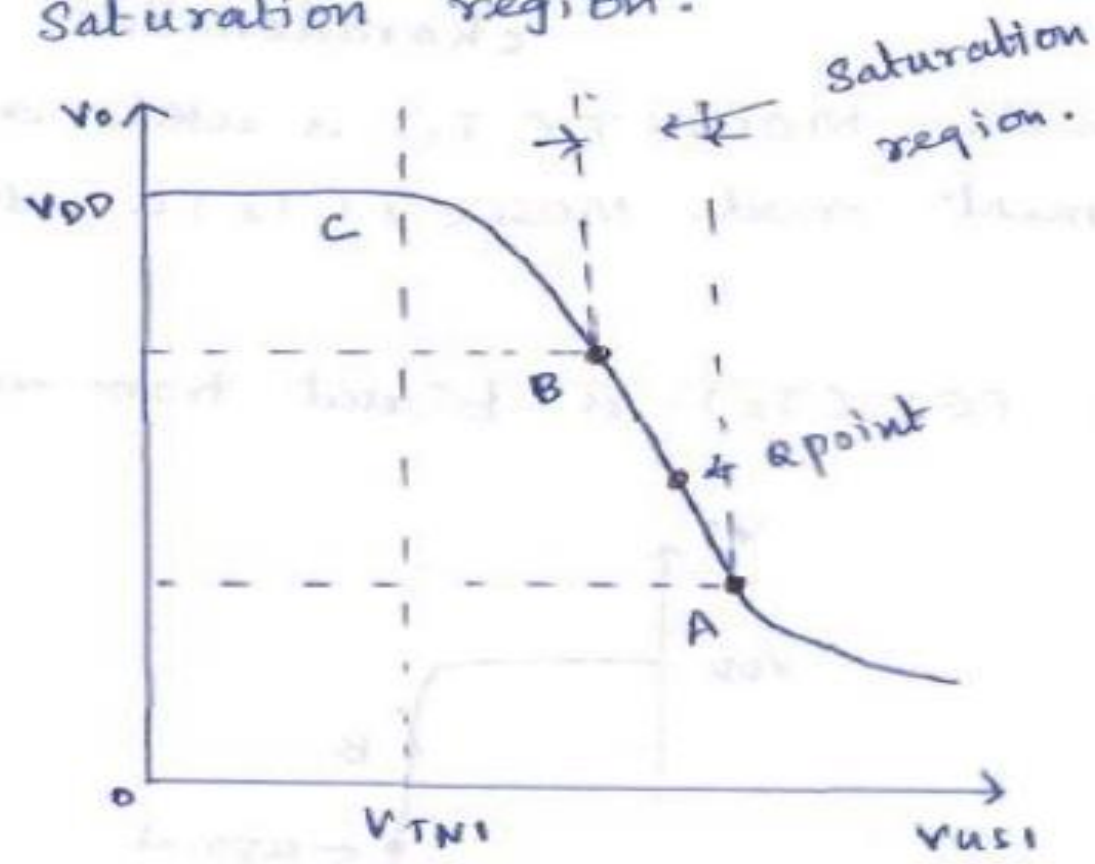


Fig: Voltage Transfer characteristics - X - 2Mark.

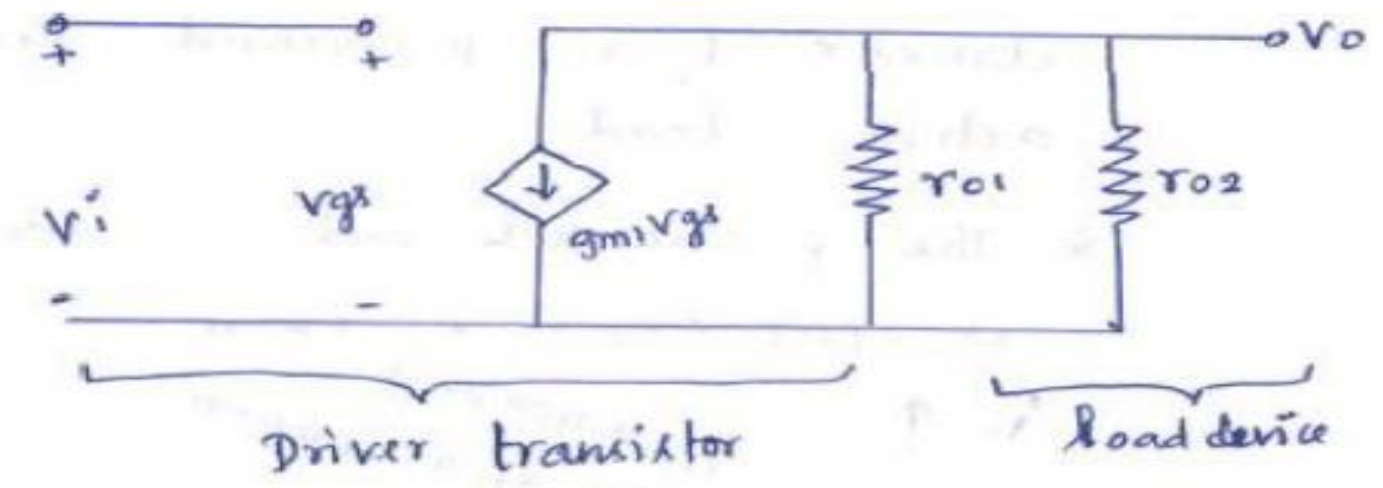


Fig: Small signal equivalent circuit



- \* The Q-point lies in the saturation region.
- \* The gate to source voltage for depletion load ( $T_2$ ) is zero,  
 $g_m V_{gs2} = 0$ .

$$V_o = -g_{m1} V_{gs} (r_{o1} \parallel r_{o2})$$

2 Marks

$$\therefore A_v = \frac{V_o}{V_i} = -g_{m1} (r_{o1} \parallel r_{o2})$$

- \* Thus for this circuit, The  $A_v$  is directly proportional to the output resistance of 2 transistors.







**THANK YOU**