



# **SNS COLLEGE OF TECHNOLOGY**



**(An Autonomous Institution)**

**19EET202 / ANALOG ELECTRONICS**

**II YEAR / III SEMESTER**

**UNIT-4: AMPLIFIERS AND SWITCHING CIRCUITS**

**DIFFERENTIAL AMPLIFIERS**



# What We'll Discuss



## TOPIC OUTLINE


Introduction  
Classification  
Working  
Applications


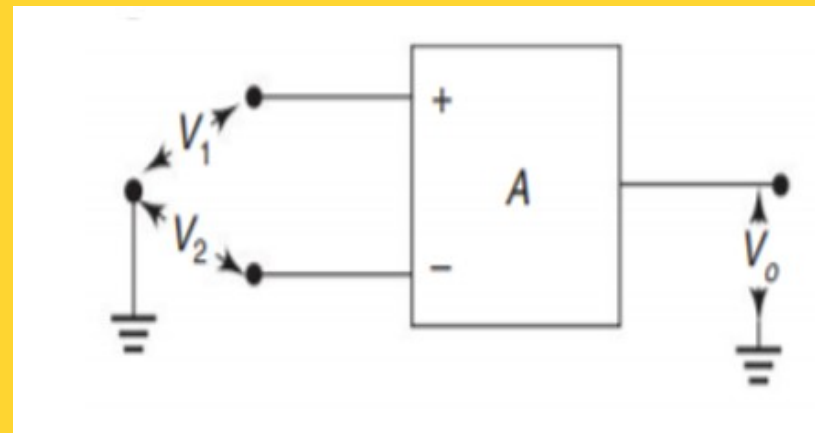
# Introduction



- The function of a differential amplifier is to amplify the difference between two signals.
- The basic block diagram of a differential amplifier consists of two input terminals and one output terminal.





## Differential Amplifiers



- The output signal in a differential amplifier is proportional to the difference between the two input signals.

$$V_o \propto V_1 - V_2$$

- If  $V_1 = V_2$ , the output voltage is zero.
- A non-zero output voltage is obtained if  $V_1$  and  $V_2$  are not equal



# Differential Amplifiers

- The difference-mode input voltage is defined as

$$V_d = (V_1 - V_2)$$



- The common-mode input voltage is defined as

$$V_{cm} = \frac{(V_1 + V_2)}{2}$$



## Working


- A differential mode amplifier has two modes of operations

They are

- • Differential mode operation
- • Common mode operation



# Differential Mode Operation

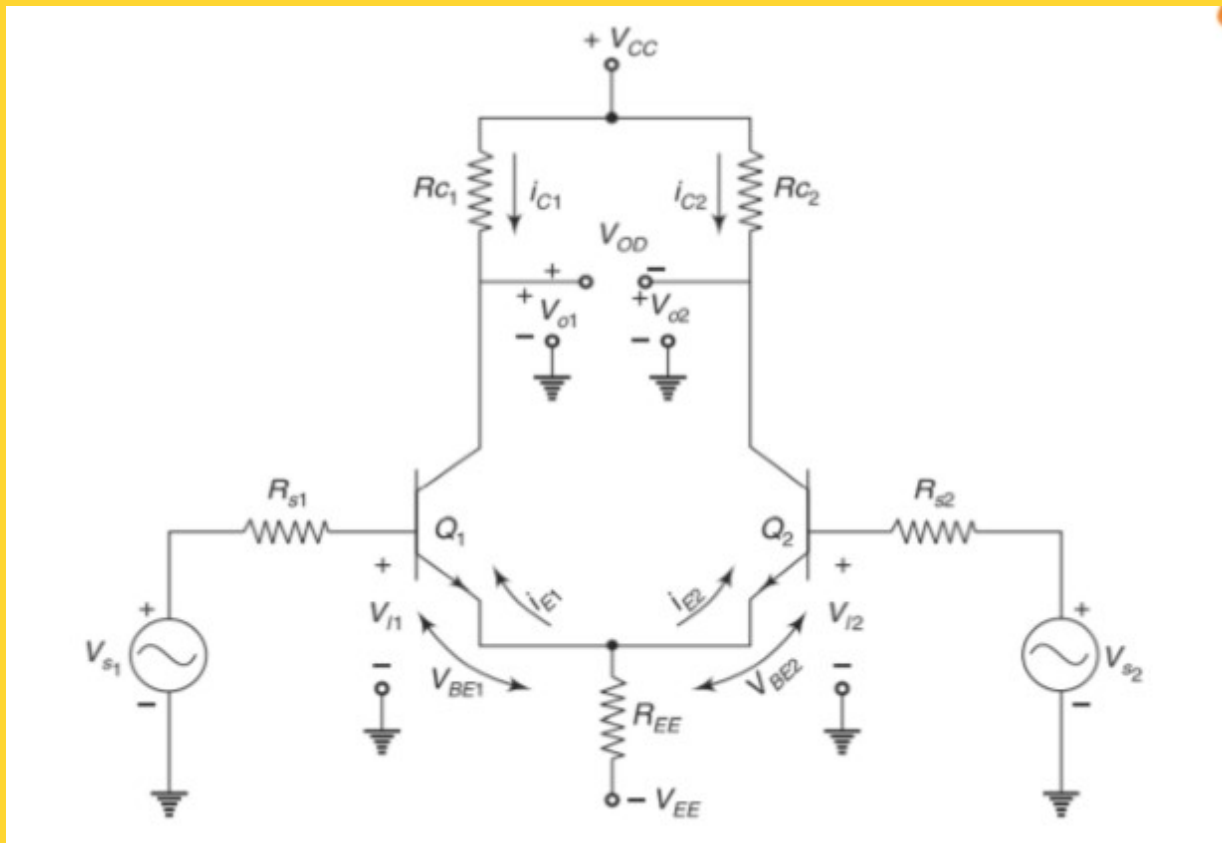



## Output Equations

Output

$$V_o \propto V_1 - V_2$$

$$V_o = A_d (V_1 - V_2)$$

$$V_o = A_d V_d$$

Differential gain  $A_d = V_o/V_d$








## Common Mode Operation

- A differential amplifier is said to be in common mode when same signal is applied to both inputs and the expected output will be zero, ie ideally common mode gain is zero.

$$V_c = \frac{V_1 + V_2}{2}$$

$$V_o = A_c V_c$$

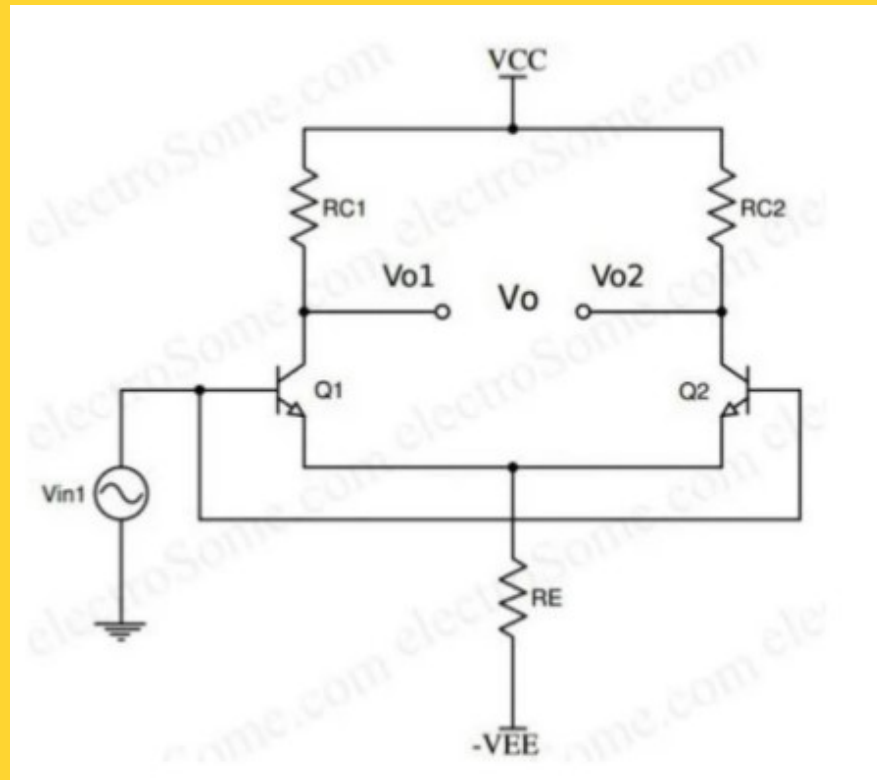



## Common Mode Rejection Ratio (CMRR)

- CMRR is introduced to define the ability of a differential amplifier to reject common mode signal.
- CMRR is defined as the ratio of the differential voltage gain  $A_d$  to common mode gain  $A_c$  and is generally expressed in dB.



$$\text{CMRR} = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$



# Features of Differential Amplifier

- • High differential voltage gain
- • Low common mode gain
- • High CMRR
- • High Input impedance
- • Large bandwidth
- • Low output impedance





# Applications

- Differential amplifiers are vital in numerous electronic systems and devices, including but not limited to:
- **Operational Amplifiers (Op-Amps):** Most operational amplifiers employ a differential input stage, enhancing their performance by offering high input impedance and common-mode noise rejection.
- **Analog-to-Digital Converters (ADCs):** Differential amplifiers are crucial in the design of ADCs. They help in eliminating noise and other common-mode signals before the analog signal is converted into a digital one.
- **Audio Systems:** These systems often utilize differential amplifiers to minimize noise interference and maintain high-quality sound reproduction.





THANK YOU