



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

19EET202 / ANALOG ELECTRONICS

II YEAR / III SEMESTER

UNIT-4: FEEDBACK AMPLIFIERS AND OSCILLATORS

WEIN BRIDGE OSCILLATORS



What We'll Discuss



TOPIC OUTLINE

Introduction

Classification


Working

Applications




Need for Oscillators

- Communication Systems
- Control signal

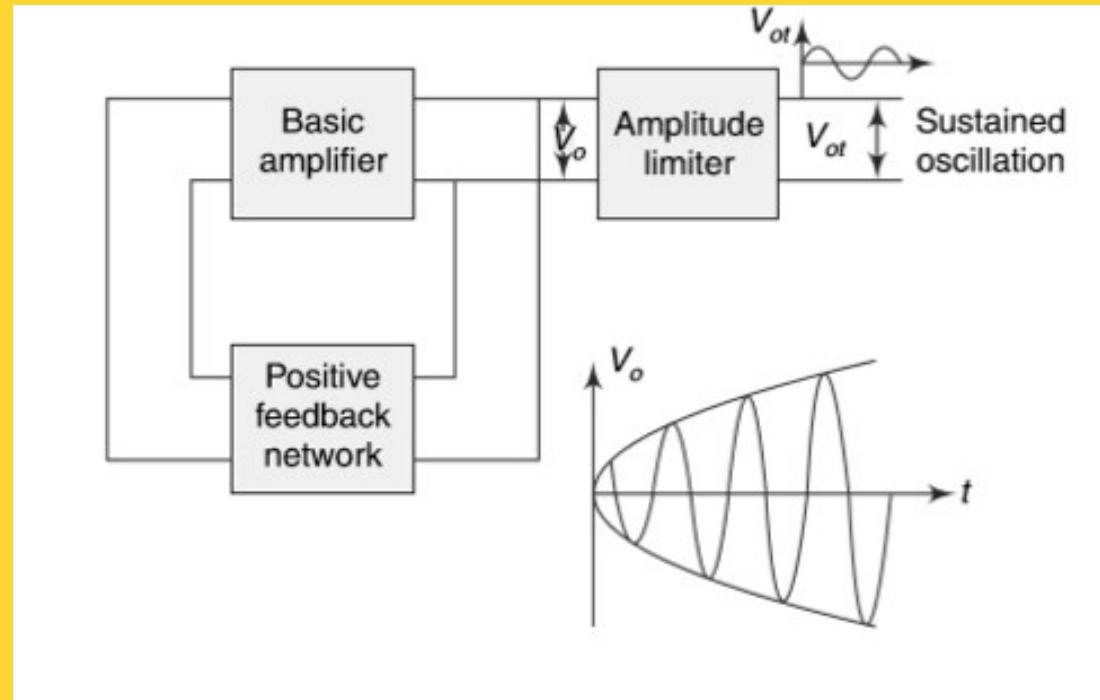




Wein Bridge Oscillator

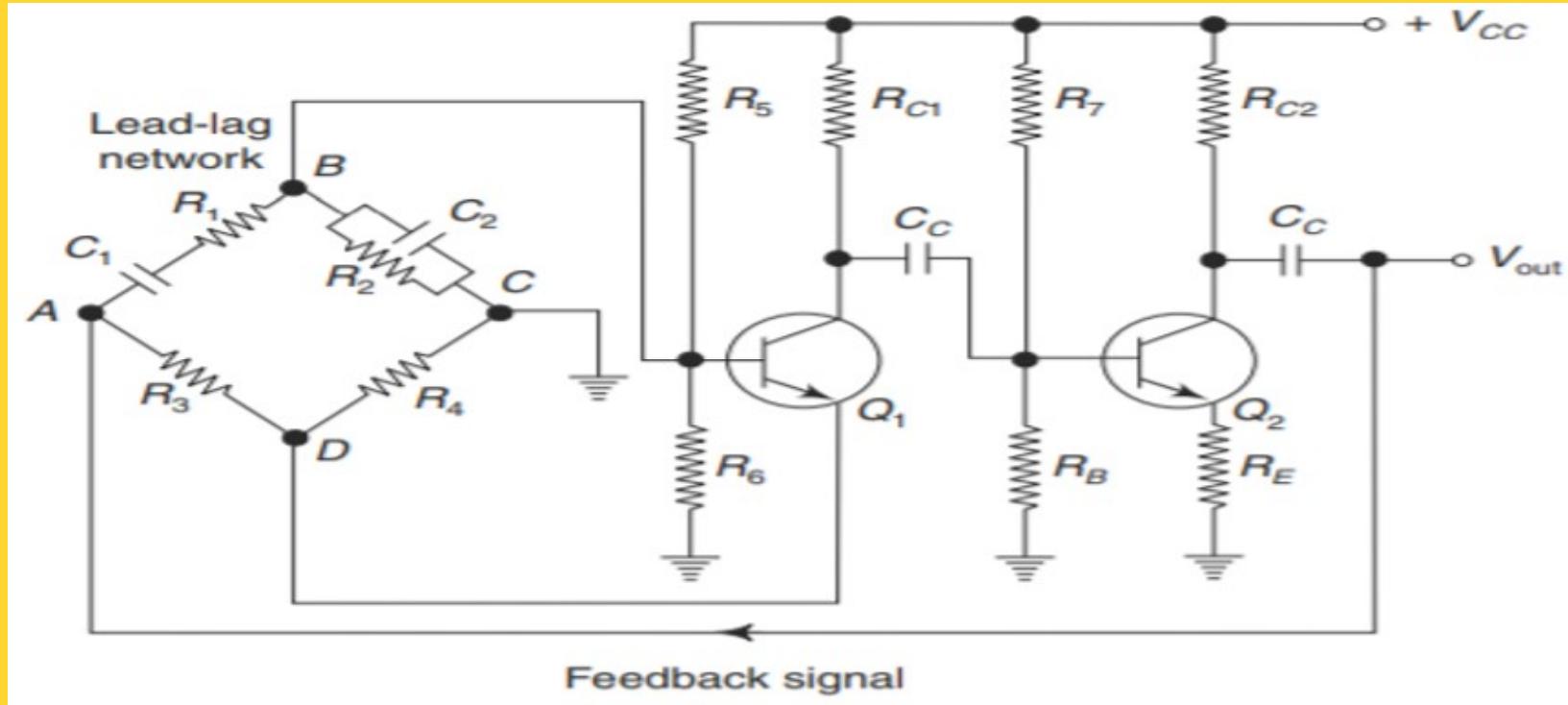



Mechanism of Start of Oscillation

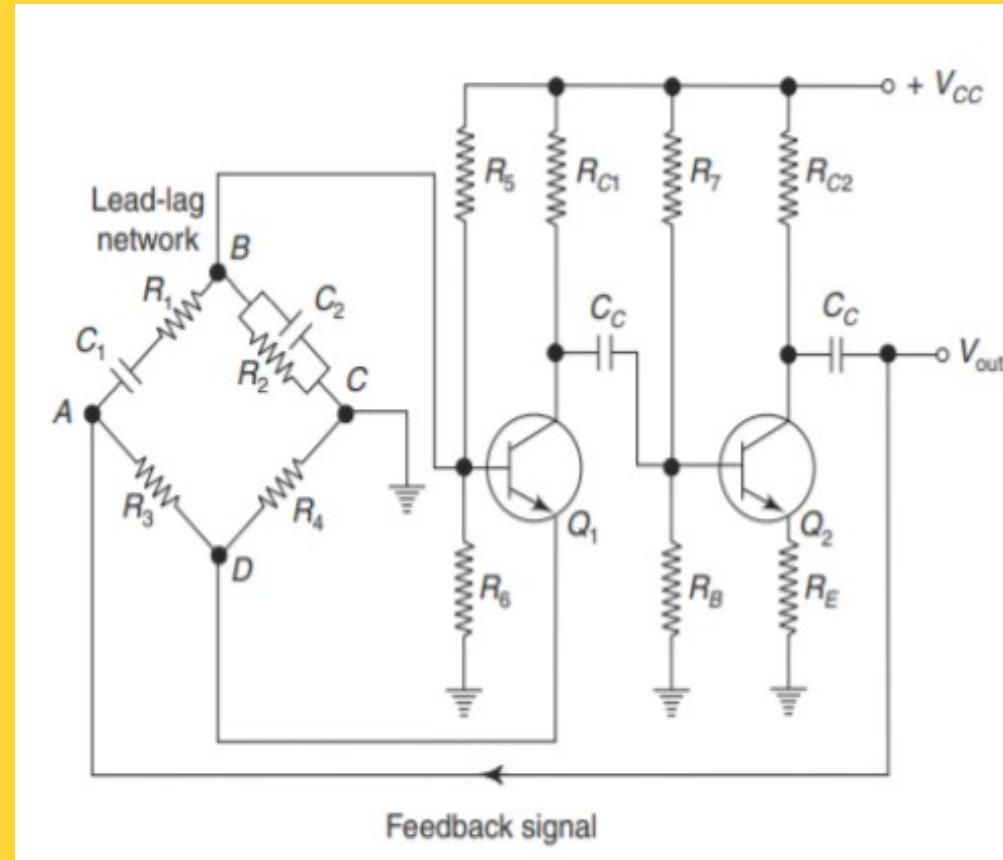
- The feedback network consists of a lead-lag network ($R_1 - C_1$ and $R_2 - C_2$) and a voltage divider ($R_3 - R_4$).





Wein Bridge Oscillator

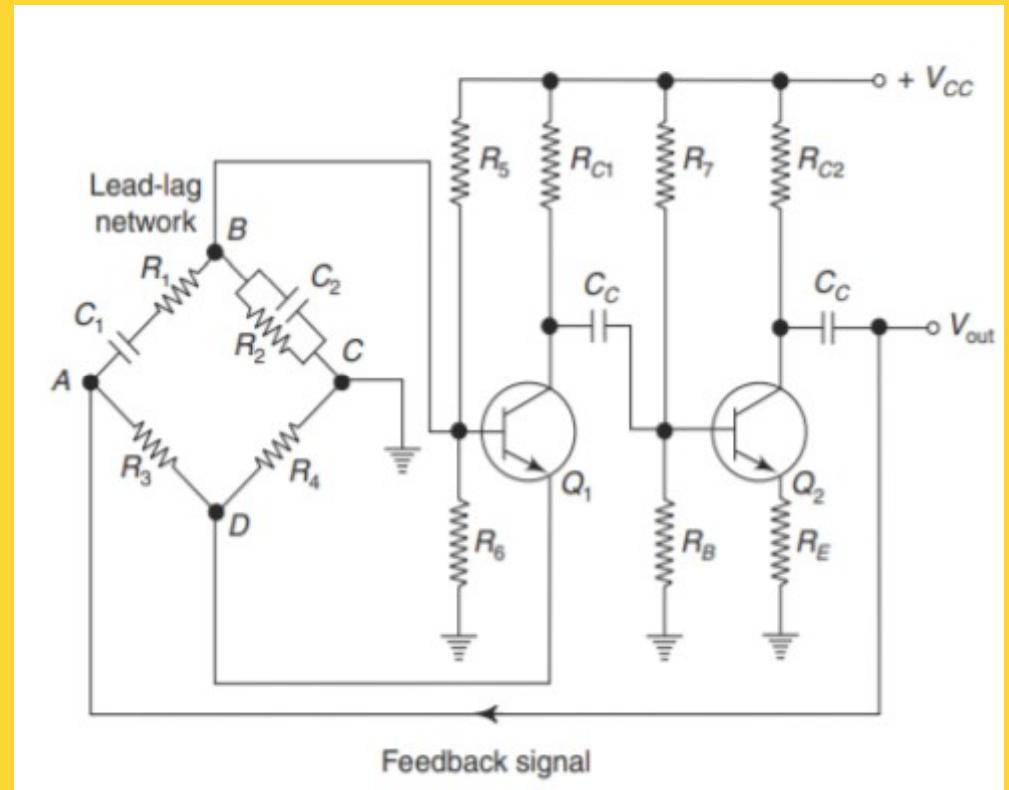- The lead-lag network provides a positive feedback to the input of the first stage and the voltage divider provides a negative feedback to the emitter of Q1.





Frequency of Oscillation



$$f_o = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$= \frac{1}{2\pi R C}$, if $R_1 = R_2 = R$ and $C_1 = C_2 = C$.



Problem-I

In an RC phase shift oscillator, if $R_1 = R_2 = R_3 = 200 \text{ k}\Omega$ and $C_1 = C_2 = C_3 = 100 \text{ pF}$. Find the frequency of oscillations.



The frequency of an *RC* phase shift oscillator is given by

$$\begin{aligned}f_o &= \frac{1}{2\pi RC\sqrt{6}} \\&= \frac{1}{2\pi \times 200 \times 10^3 \times 100 \times 10^{-12} \sqrt{6}} \\&= 3.248 \text{ kHz}\end{aligned}$$



Problem-II

In a Wien-bridge oscillator, if the value of R is $100 \text{ k}\Omega$, and frequency of oscillation is 10 kHz , find the value of capacitor C .



Solution The operating frequency of a Wien-bridge oscillator is given by

$$f_o = \frac{1}{2\pi RC}$$

Therefore,

$$\begin{aligned} C &= \frac{1}{2\pi R f_o} \\ &= \frac{1}{2\pi \times 100 \times 10^3 \times 10 \times 10^3} = 159 \text{ pF} \end{aligned}$$



Fréquency of Oscillation

- For calculating the frequency of oscillation Equate the imaginary part of the basic equation to zero



$$f_o = \frac{\omega_o}{2\pi},$$

$$\left[L_1 + L_2 + 2M - \frac{1}{\omega_o^2 C} \right] = 0$$

$$f_o = \frac{\omega_o}{2\pi} = \frac{1}{2\pi\sqrt{(L_1 + L_2 + 2M)C}}$$



Assessment 1



Determine the frequency of oscillations when a RC phase-shift oscillator has $R = 10 \text{ k}\Omega$, $C = 0.01 \mu\text{F}$ and $R_C = 2.2 \text{ k}\Omega$. Also, find the minimum current gain needed for this purpose.



Reference

Electronic Devices and Circuits By Salivahanan





THANK YOU