



# **SNS COLLEGE OF TECHNOLOGY**



**(An Autonomous Institution)**

**19EET202 / ANALOG ELECTRONICS**

**II YEAR / III SEMESTER**

**UNIT-4: FEEDBACK AMPLIFIERS AND OSCILLATORS**

**COLPITTS OSCILLATOR**



# What We'll Discuss



## TOPIC OUTLINE


Introduction  
Classification  
Working  
Applications



# Need for Oscillators



- Communication Systems
- Control signal

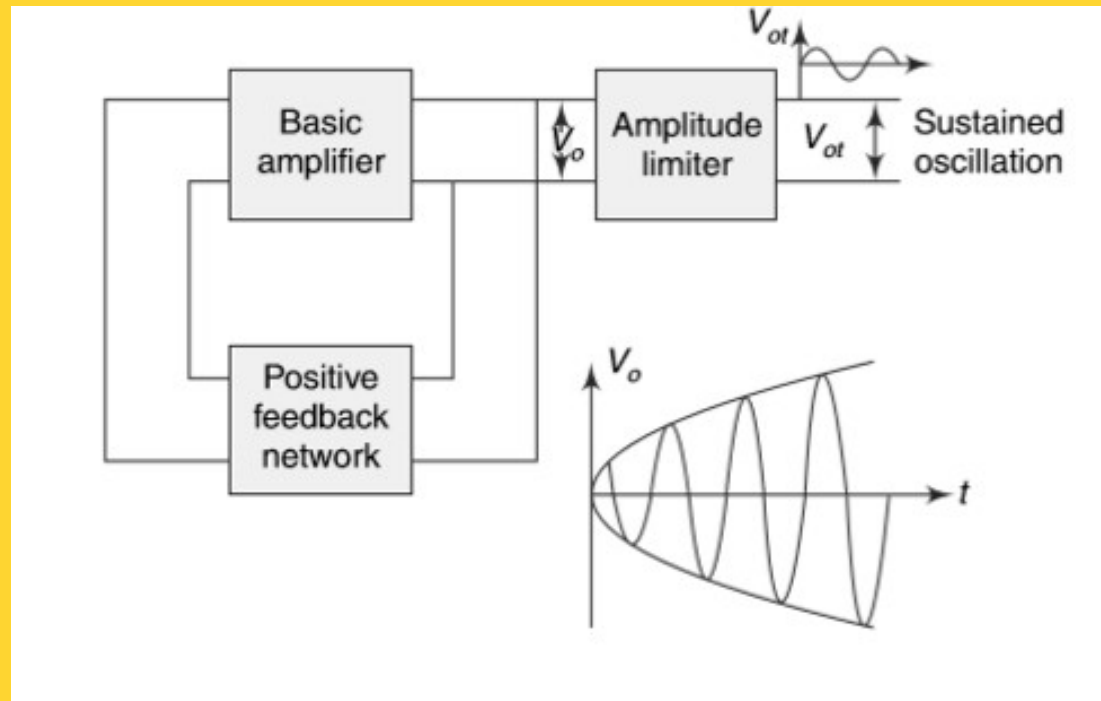



## Colpitts Oscillator Circuit

- NPN transistor
- Conditions for oscillations
- Positive- Feed back

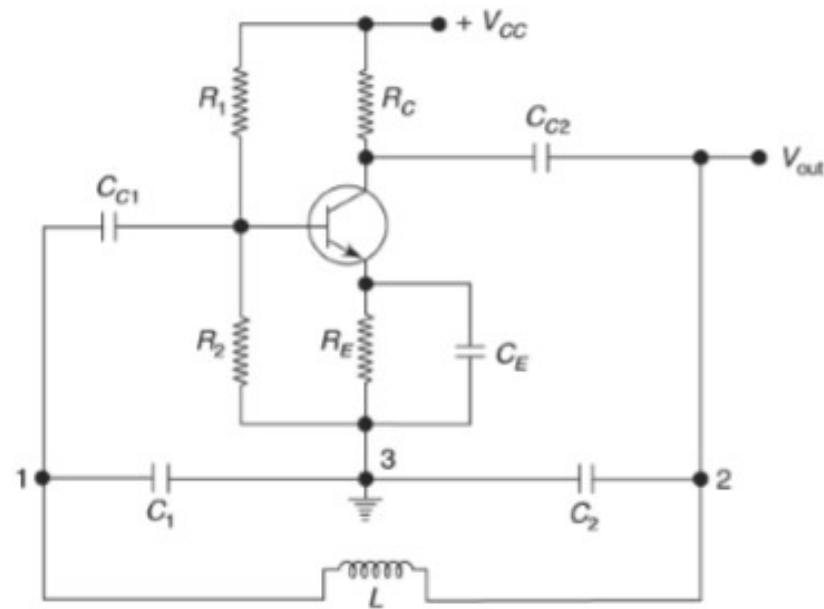


Fig. 15-5 Colpitts oscillator



# Differential Amplifiers

- The difference-mode input voltage is defined as

$$V_d = (V_1 - V_2)$$



- The common-mode input voltage is defined as

$$V_{cm} = \frac{(V_1 + V_2)}{2}$$



## Mechanism of Start of Oscillation


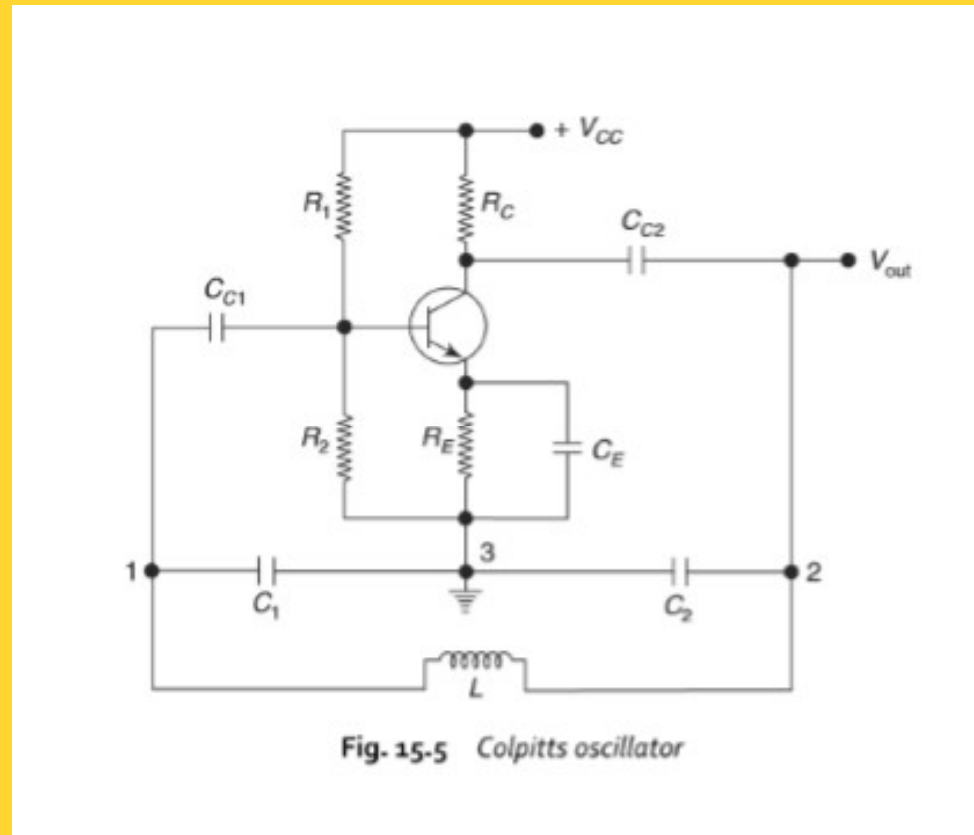


Fig. 15-5 Colpitts oscillator

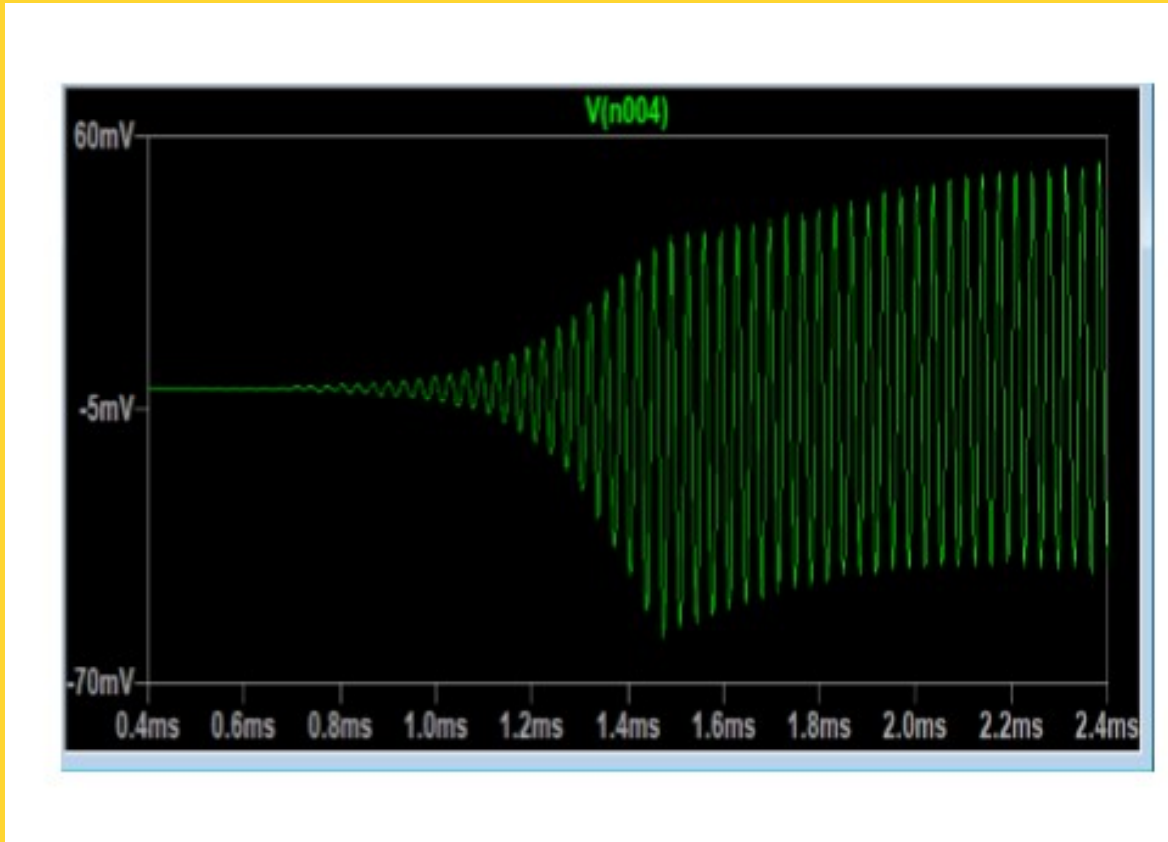

# Amplitude Limiting





# Frequency of Oscillation

$$Z_1 = \frac{1}{j\omega C_1} = -\frac{j}{\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2} = -\frac{j}{\omega C_2}$$

$$Z_3 = j\omega L$$

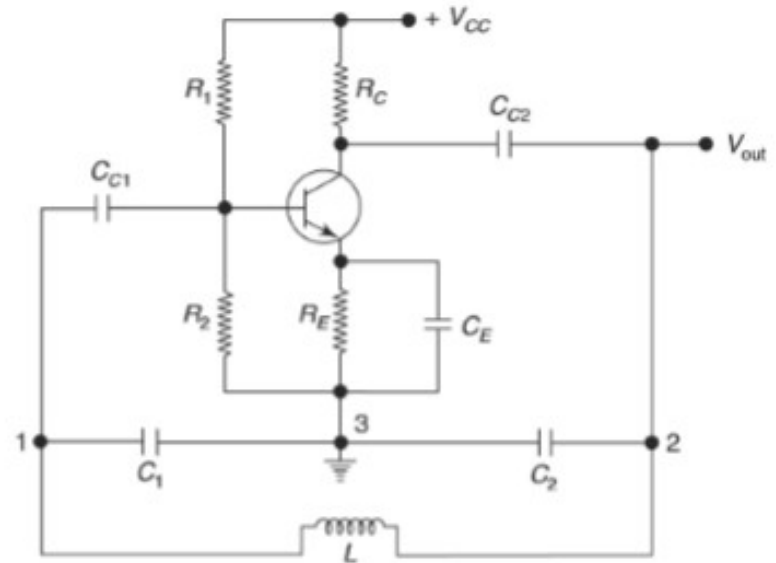


Fig. 15.5 Colpitts oscillator








# Frequency of Oscillation

General Equation of Oscillation

$$h_{ie}(Z_1 + Z_2 + Z_3) + Z_1Z_2(1 + h_{fe}) + Z_1Z_3 = 0$$
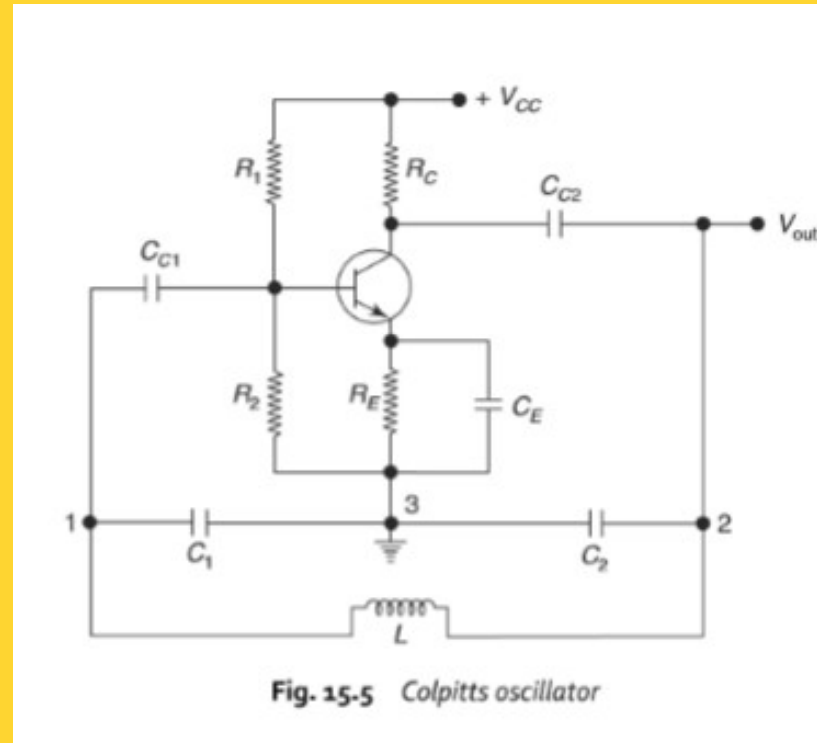
$$-jh_{ie}\left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L\right) + \left(\frac{1 + h_{fe}}{\omega^2 C_1 C_2} - \frac{L}{C_1}\right) = 0$$





# Fréquency of Oscillation

- For calculating the frequency of oscillation
- Equate the imaginary part of the basic equation to zero

$$f_o = \frac{\omega_o}{2\pi}$$

$$f_o = \frac{\omega_o}{2\pi} = \frac{1}{2\pi} \sqrt{\frac{C_1 + C_2}{LC_1C_2}}$$

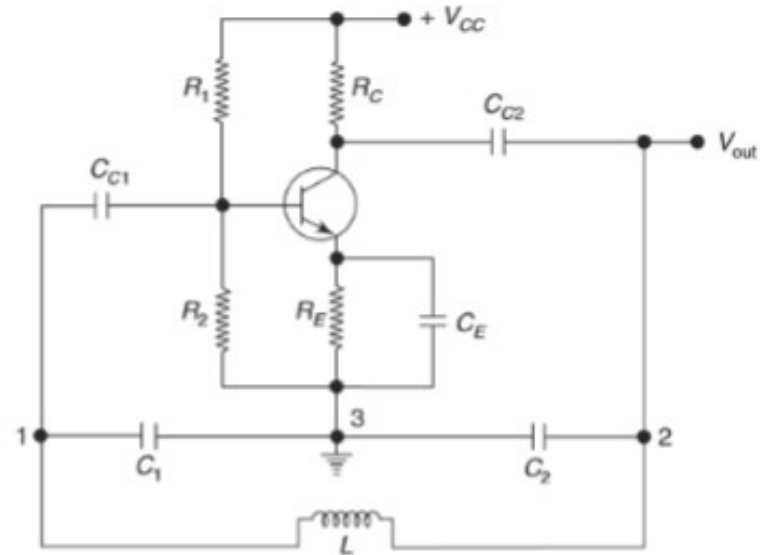


Fig. 15-5 Colpitts oscillator



# Conditions for Maintenance of Oscillation



For obtaining the conditions for maintenance of oscillation equate the real part of the basic equation to zero



$$h_{fe} = \frac{C_2}{C_1}$$



## Assessment

- In the Colpitts oscillator,  $C_1=0.02$  micro Farads and  $C_2=0.02$  micro Farads. If the frequency of oscillation is 10 KHz, find the value of the inductor?





THANK YOU