



SNS COLLEGE OF TECHNOLOGY
(Autonomous)
Coimbatore-35
Department of EEE



**16EE205 / INDUCTION AND SYNCHRONOUS
MACHINES**


Unit – IV (A)
**Starting of Three phase
Induction motor**

Need for Starting – Types of Starters

At starting when the rotor is at standstill, the squirrel cage rotor is just like a short circuited secondary.


Therefore the current in the rotor circuit will be high and consequently the stator also will draw a high current from the supply lines if full line voltage were applied at start.

1.D.O.L Starter

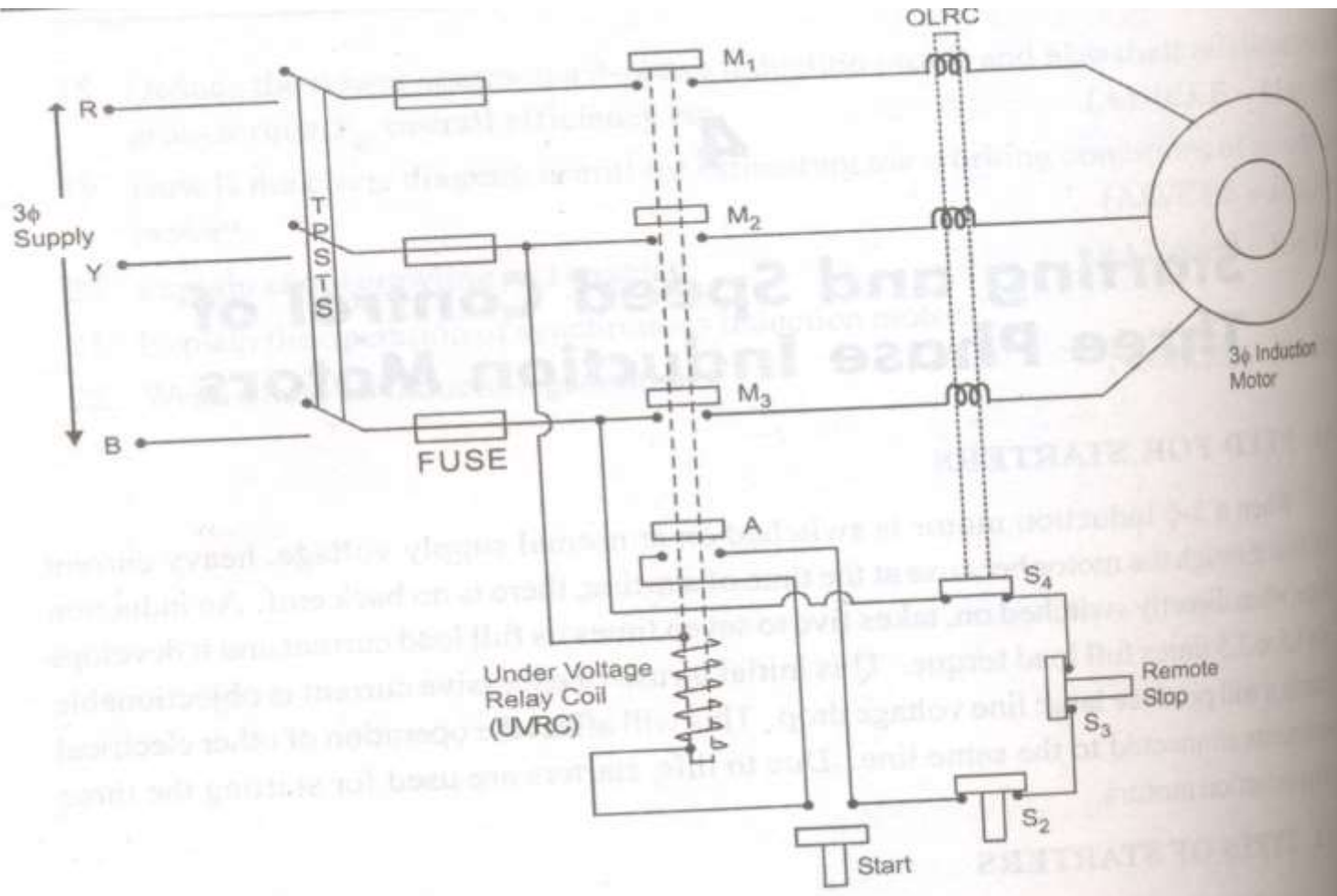

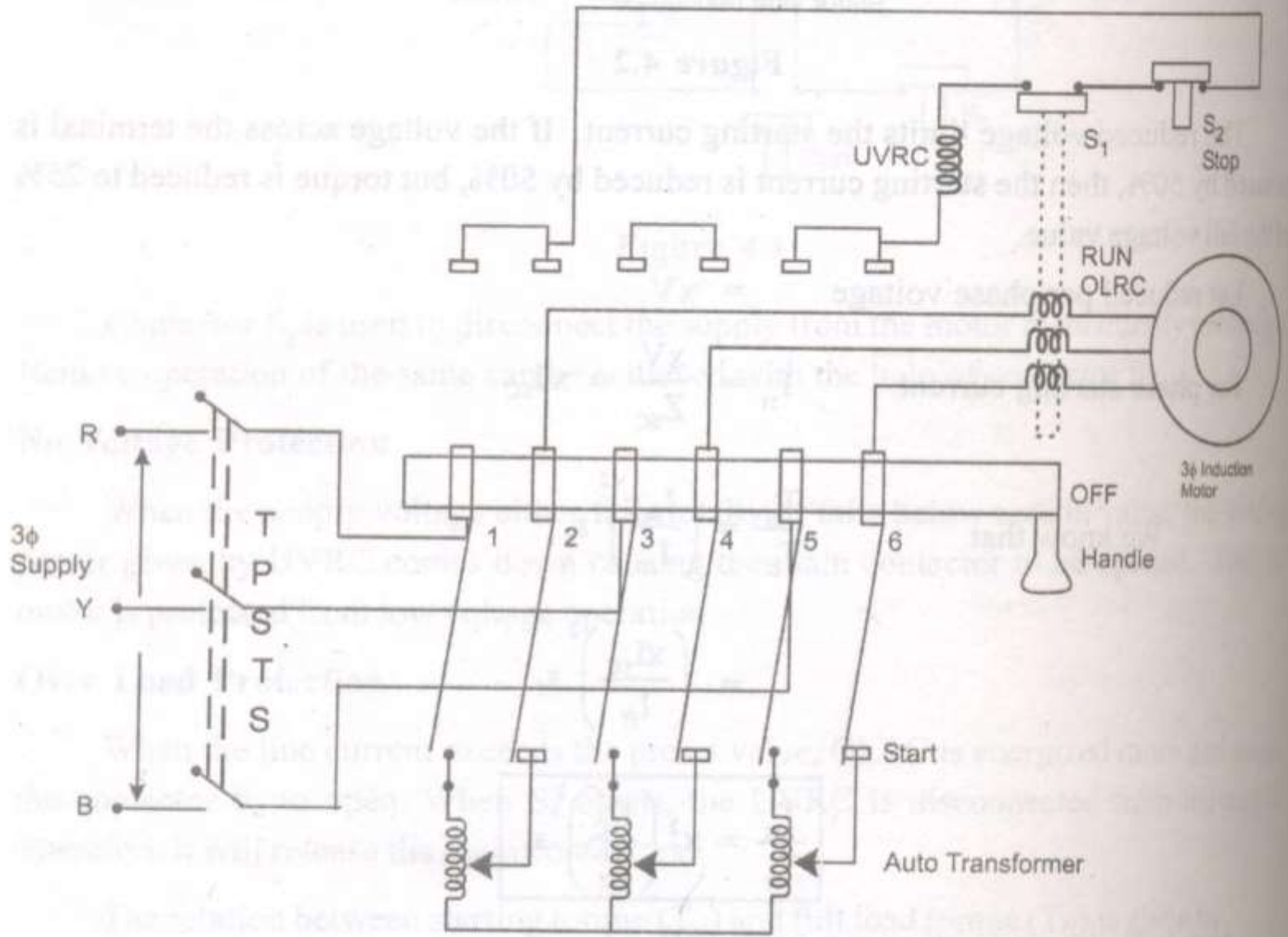2.Auto –Transformer Starter

- ▶ A three phase auto transformer can be used to reduce the voltage applied to the stator
- ▶ The advantage of this method is that the voltage is reduced by transformation and not by dropping the excess in resistor
- ▶ Hence the input current and power from the supply are also reduced compared to stator resistor starting.



Auto -Transformer Starter

The ratio of starting torque (T_{st}) to full load torque (T_f):

$$\frac{T_{st}}{T_f} = X^2 \left(\frac{I_{st}}{I_f} \right)^2 S_f$$


I_{st} = starting current and I_f = full load current

X = Transformer tapping as p.u. of rated voltage

S_f = Full load slip

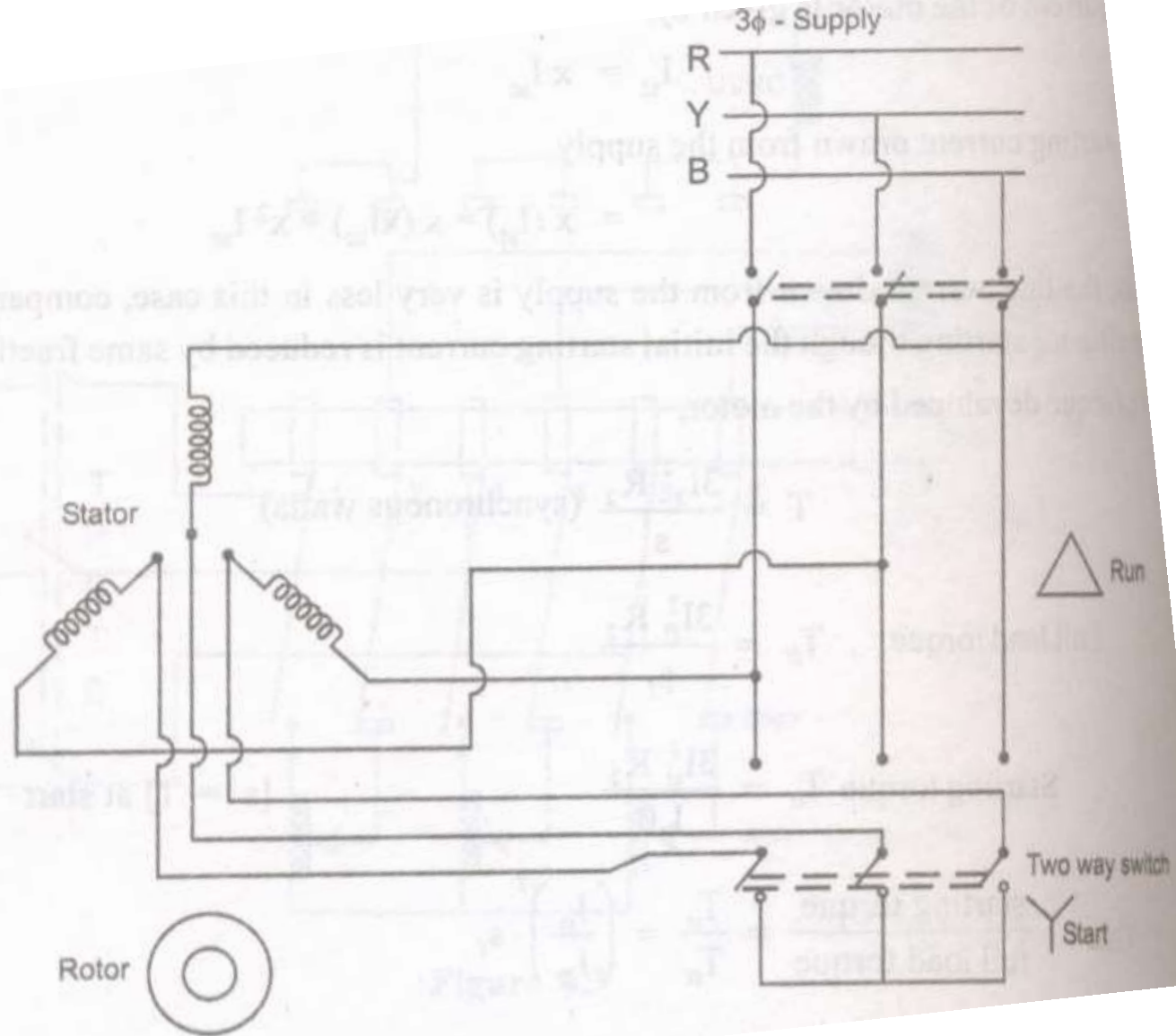3. Star-Delta Starter

- ▶ This method applicable for motors designed to run normally with delta connected stator windings
- ▶ At starting, the stator windings connected in star
- ▶ After the motor has reached nearly the steady state speed, the windings are connected in delta
- ▶ Over load and single phasing protection are provided



Star-Delta Starter

- ▶ At starting the stator phase voltage reduced by $1/\sqrt{3}$ times the voltage.
- ▶ Phase current reduced by $1/\sqrt{3}$ times the current with the direct online starting.
- ▶ Line current reduce by 3 times.

4. Rotor Resistance Starter

- ▶ Applicable to slip ring induction motors
- ▶ Rated voltage applied to the stator
- ▶ balanced three phase resistors connected in series with the rotor through slip rings
- ▶ Resistance kept at maximum at starting
- ▶ starting current reduced
- ▶ starting torque increased
- ▶ after starting resistance can be cut out

