Design Synchronous Decade Counter Using T flip flop

ASSESSMENTS

1.What is BCD Counter?
2.Design synchronous decade counter using T flip flop.
3.Difference between synchronous and Asynchronous counter .

THANK YOU