



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore – 641 107

AN AUTONOMOUS INSTITUTION

Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai



VI Semester

B.E-Electrical & Electronics Engineering

19EE605 – PROTECTION AND SWITCHGEAR

Topic Name : Nature and causes of faults

Duration: 10 min

No. of Questions 02

1. Write the inference which fault occurred from the picture_____

K2

(a) Line to Line (b) Line to Ground (c) Line to Line to Ground (d) Ground to Ground



2. Write the inference from the picture by fault_____

K2

