



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore - 641 107

AN AUTONOMOUS INSTITUTION

Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai



VI Semester B.E-Electrical & Electronics Engineering 19EE605 - PROTECTION AND SWITCHGEAR


Topic Name : Type of faults

Duration: 10 min

No. of Questions 04

K1

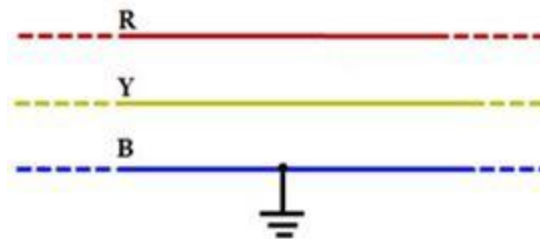
1. Write what are the faults occurred in the below mentioned pictures. _____



(a) Line to Line (b) Line to Ground (c) Line to Line to Ground (d) Ground to Ground


K1

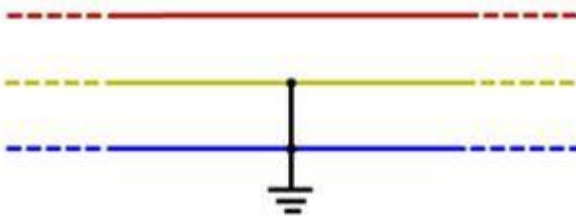2. What are the faults occurred in the below mentioned pictures. _____



(a) Line to Line (b) Line to Ground (c) Line to Line to Ground (d) Ground to Ground

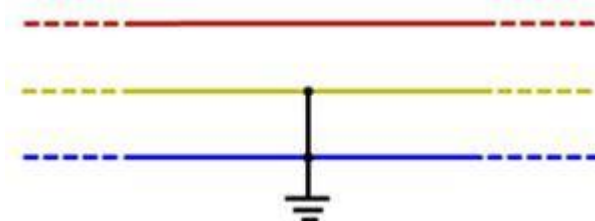3. What are the faults occurred in the below mentioned pictures. _____



K1



SNS COLLEGE OF ENGINEERING

Kurumbapalayam (Po), Coimbatore - 641 107

AN AUTONOMOUS INSTITUTION


Approved by AICTE, New Delhi and Affiliated to Anna University, Chennai



VI Semester

B.E-Electrical & Electronics Engineering

19EE605 - PROTECTION AND SWITCHGEAR

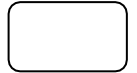

(a) Line to Line (b) Line to Ground (c) Line to Line to Ground (d) Ground to Ground